

# SYNCHRONOUS-LOGIC OPTIMIZATION

© *Giovanni De Micheli*

Stanford University

# Outline

---

© GDM

- Structural optimization methods:
  - Peripheral retiming
  - Synchronous-logic transformations.
  - Synchronous *don't cares* .
- Relations between state-based models and structural models.

## Peripheral retiming









© GDM

---

- Alternate retiming and comb. synthesis.
- Move register position to periphery:
  - Maximize the scope of combinational logic.
  - Borrow and release synchronous delays.
- Optimize combinational logic.
- Return borrowed synchronous delays.

# Example

© GDM

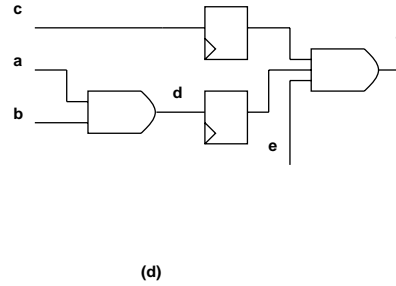       

## Assumption for peripheral retiming

© GDM

- The network graph is acyclic.
- There are no two paths from an input to an output vertex with different weights.
- There exists integer vectors
  - $\mathbf{a} \in \mathbb{Z}^{|V^I|}$  and  $\mathbf{b} \in \mathbb{Z}^{|V^O|}$ , such that
  - $w(v_i, \dots, v_j) = a_i + b_j$  for all paths  $(v_i, \dots, v_j)$  with  $v_i \in V^I, v_j \in V^O$ .
- Remarks:
  - Applicable to pipelined networks.
  - Extensible to circuits with feedback by using partitioning.

## Logic transformations and peripheral retiming


---

© GDM


- Apply combinational logic transformations.
- Requirement:
  - No negative weight on I/O paths to guarantee that circuit can be retimed again.
- Reject some transformations.

# Example


© GDM

 

(a)

 

(b)

 

(c)

## Algebraic synchronous logic transformations

---



© GDM

- Combine transformations with retiming.
- Transform combinational logic expressions:
  - *Within* register boundaries.
  - *Across* register boundaries.
- Extension of *algebraic* transformations.



## Example of synchronous elimination

© GDM

  


$$c = ab; \quad x = d + c \oplus 1$$

$$x = d + a \oplus 1 b \oplus 1$$

# Example of synchronous substitution

© GDM

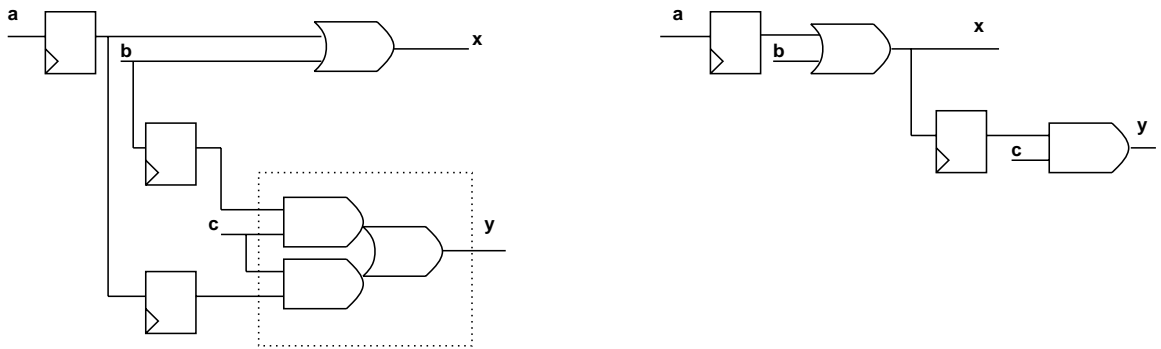

$$x = a @ 1 + b; \quad y = a @ 2c + b @ 1c$$

$$x = a @ 1 + b; \quad y = x @ 1c$$

## Boolean synchronous logic transformations

---

© GDM

- Boolean function minimization:
  - Functions of delayed variables.
  - *Explicit synchronous don't care* conditions.
  - Extension of combinational methods.
- Boolean relation minimization:
  - Problem generalization.
  - *Implicit don't care* conditions.

## Extension of classic *don't care* conditions to the synchronous domain

---

© GDM

- *Controllability don't care* sets:
  - Conditions that cannot occur:
    - \* Due to *external* connections.
    - \* Due to *internal* connections.
- *Observability don't care* sets:
  - Conditions such that a variable is not observed at present or in the future.
    - \* At some *external* port.
    - \* At some *internal* gate.

## Explicit *don't care* representation


---

© GDM

- Synchronous literal: literal with time label.
- Synchronous product: product of sync. literals.
- *Don't care* sets:
  - Sums of synchronous products.
  - Time invariant component.
  - Time dependent component.

## Example

© GDM

 

- Initialization:

- $(b^{(-4)}, b^{(-3)}, b^{(-2)}) = (1, 0, 1)$ .

- Transient *don't care* condition:

- $v^{(-3)} \neq v^{(-1)}$ .

- Time-invariant *don't care* condition:

- $u^{(n)}v^{(n+1)}$ .

## Synchronous logic optimization using explicit *don't care* sets.


---

© GDM

- Compute local *don't care* sets:
  - Extensions of *controllability*, *observability* algorithms for combinational circuits.
- Optimize functions w.r. to local *don't care* sets:
  - Rename time-labeled variables.
  - Use two-level minimizers.

## Example

© GDM

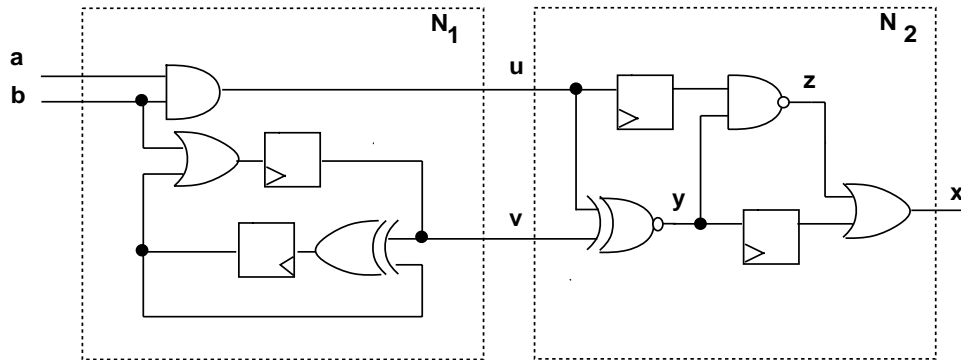

- Replace *EXNOR* gate by an *AND* gate.

– Perturbation:

$$* \delta^{(n)} = (u^{(n)}v^{(n)} + u'^{(n)}v'^{(n)}) \oplus (u^{(n)}v^{(n)}) = u'^{(n)}v'^{(n)}$$

- Compute local *don't care* set:

–  $\widetilde{DC}_y$  contains  $u'^{(n-1)}u'^{(n)} + u^{(n-1)}v'^{(n)}$ .


- Perturbation is bounded by *don't care* set:

– Replacement feasible !



# Example

© GDM

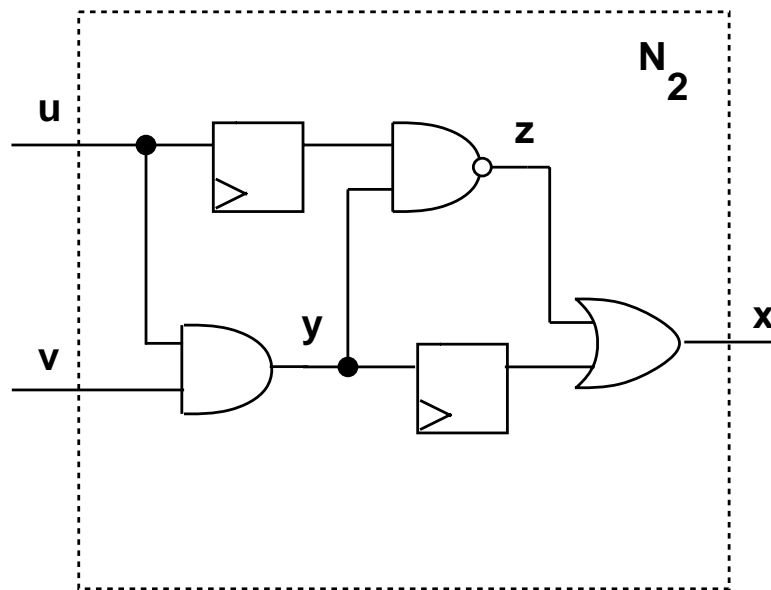

## Implicit *don't care* conditions

---


© GDM

- Explicit *don't care* sets do not represent all degrees of freedom for optimization.
- There are some feasible simplifications that require a more complex model.
  - Synchronous Boolean relation models.
  - Implicit *don't care* condition representations.
- Specialized algorithms.

# Example


## Path reconvergence with unequal delays

© GDM

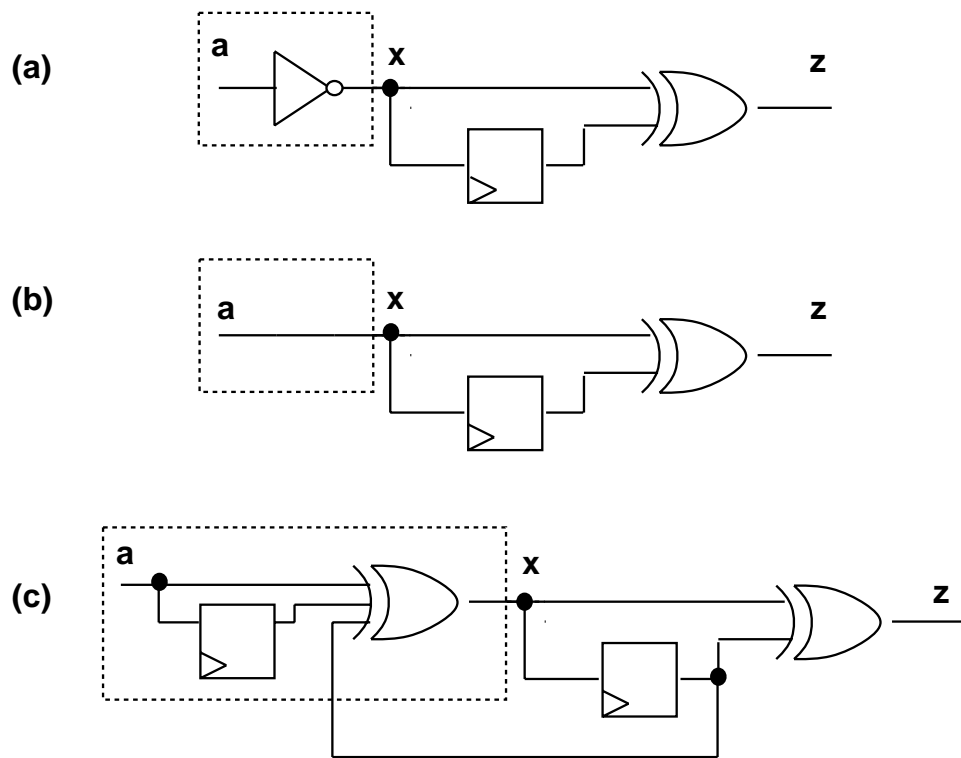

## Example of implicit representation

© GDM

 

- Equating terminal behavior:

$$- F = x'_n \oplus x'_{n-1} = y_n \oplus y_{n-1}$$

$$- (x'_n \oplus x'_{n-1}) \overline{\oplus} (y_n \oplus y_{n-1}) = 1$$

- Example of solutions:

$$- y_n = x_n$$

$$- y_n = x'_n$$

$$- y_n = x_n \oplus x_{n-1} \oplus y_{n-1}$$

## Relating the structural to the state-based models.


---

© GDM


- State encoding:
  - Maps the state-based representation into a structural one.
- State extraction:
  - Recovers the state information from a structural model.
- Remark:
  - A circuit with  $n$  register may have  $2^n$  states.
  - Unreachable states.

# State Extraction

© GDM

 

(a)

 

(b)

- State variables:  $p, q$ .
- Initial state:  $p = 0, q = 0$ .
- Four possible states.

# State Extraction

© GDM

- Reachability analysis.
  - Given a state  
determine which states are reachable  
for some inputs.
  - Given a state subset  
determine the reachable state subset.
  - Start from initial state.
  - Stop when convergence is reached.
- Notation:
  - A state (or state subset) is an  
expression over the state variables.

## Reachability analysis


© GDM

- State transition function:  $\mathbf{f}$
- Initial state:  $r_0$ .
- States reachable from  $r_0$ :
  - Image of  $r_0$  under  $\mathbf{f}$ .
- States reachable from set  $r_k$ :
  - Image of  $r_k$  under  $\mathbf{f}$ .
- Iteration:
  - $r_{k+1} = r_k \cup (\text{image of } r_k \text{ under } \mathbf{f})$ .
- Convergence:
  - $r_{k+1} = r_k$  for some  $k$ .




## Example

© GDM

 

(a)

 

(b)

- Initial state  $r_0 = p'q'$ .

- The state transition function  $\mathbf{f} = \begin{bmatrix} x'p'q' + pq \\ xp' + pq' \end{bmatrix}$ .

## Example

© GDM

- Image of  $p'q'$  under  $\mathbf{f}$ :

- When  $(p = 0; q = 0)$ ,  $\mathbf{f}$  reduces to  $\begin{bmatrix} x' \\ x \end{bmatrix}$

- Range is  $\begin{bmatrix} 0 \\ 1 \end{bmatrix}$  and  $\begin{bmatrix} 1 \\ 0 \end{bmatrix}$

- States reachable from the reset state:

- $(p = 1; q = 0)$  and  $(p = 0; q = 1)$ .

- $r_1 = p'q' + pq' + p'q = p' + q'$ .

- States reachable from  $r_1$ :  $\begin{bmatrix} 0 \\ 0 \end{bmatrix}$ ,  $\begin{bmatrix} 0 \\ 1 \end{bmatrix}$ ,  $\begin{bmatrix} 1 \\ 0 \end{bmatrix}$

- Convergence:  $s_0 = p'q'$ ;  $s_1 = pq'$ ;  $s_2 = p'q$ .

## Completing the extraction


---

© GDM


- Determine state set (vertex set).
- Determine transitions (edge set) and I/O labels.
  - Inverse image computation.
  - Look at conditions that lead you into a given state.

# Example

© GDM

 

(a)

 

(b)

- Transitions into  $s_0 = p'q'$ .

- Patterns that make  $\mathbf{f} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$

- $(x'p'q' + pq)'(xp' + pq) = x'p'q$

- Transition from state  $s_2 = p'q$  under input  $x'$ .

## Remarks

---

© GDM

- Extraction is performed efficiently with BDDs.
- Model the transition relation  $\chi(\mathbf{i}, \mathbf{x}, \mathbf{y})$  with BDD.
  - Links possible triples of
    - \* (input, state, next-state).
- Image of  $r_k$  (where  $r_k$  depends on  $\mathbf{x}$ ).
  - $\mathcal{S}_{\mathbf{i}, \mathbf{x}}(\chi(\mathbf{i}, \mathbf{x}, \mathbf{y}) \cdot r_k(\mathbf{x}))$ .

# Summary

## Optimization of synchronous circuits

---

© GDM

- State-based models:
  - Classic FSM optimization.
- Structural models:
  - Retiming.
  - Peripheral retiming.
  - Algebraic and Boolean transformations.
- Still area of active research.