

# TIMING ISSUES IN MULTI-LEVEL LOGIC OPTIMIZATION

© *Giovanni De Micheli*

Stanford University

# Outline

---

© GDM

- Timing verification.
  - Delay modeling.
  - Critical paths.
  - The false path problem.
- Algorithms for timing optimization.

# Timing verification and optimization

© GDM

- Verification:
  - Check that a circuit runs at speed:
    - \* Satisfies I/O delay constraints.
    - \* Satisfies cycle-time constraints.
  
- Optimization:
  - *Minimum area*
    - \* subject to *delay* constraints.
  - *Minimum delay*
    - \* (subject to *area* constraints).

# Delay modeling

---

© GDM

- Gate delay modeling:
  - Straightforward for bound networks.
  - Approximations for unbound networks.
  
- Network delay modeling:
  - Compute signal propagation:
    - \* Topological methods.
    - \* Logic/topological methods.

# Gate delay modeling unbound networks

---

© GDM

- Virtual gates:
  - Logic expressions.
- Stage delay model:
  - Unit delay per vertex.
- Refined models:
  - Depending on fanout.


## Network delay modeling

© GDM

- For each vertex  $v_i$ .
- *Propagation delay*  $d_i$ .
  - I/O propagation delays are usually zero.
- *Data-ready time*  $t_i$ .
  - Input data-ready times denote when inputs are available.
  - Computed elsewhere by *forward traversal*:
  - $$t_i = d_i + \max_{j|(v_j, v_i) \in E} t_j$$

# Example

© GDM

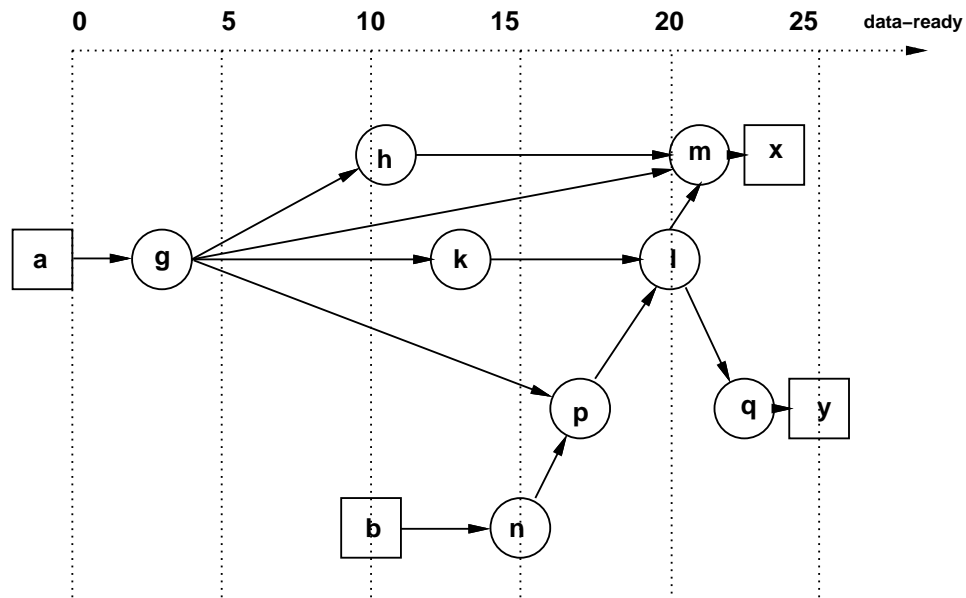

- Propagation delays:

- $d_g = 3; d_h = 8; d_m = 1; d_k = 10; d_l = 3;$

- $d_n = 5; d_p = 2; d_q = 2; d_x = 2; d_y = 3;$

## Network delay modeling


© GDM

- For each vertex  $v_i$ .
- *Required data-ready time*  $\bar{t}_x$ .
  - Specified at the primary outputs.
  - Computed elsewhere by *backward traversal*:
    - $\bar{t}_i = \min_{j|(v_i, v_j) \in E} \bar{t}_j - d_j$
- *Slack*  $s_i$ .
  - Difference between required and actual data-ready times  $s_i = \bar{t}_i - t_i$ .



# Example

© GDM

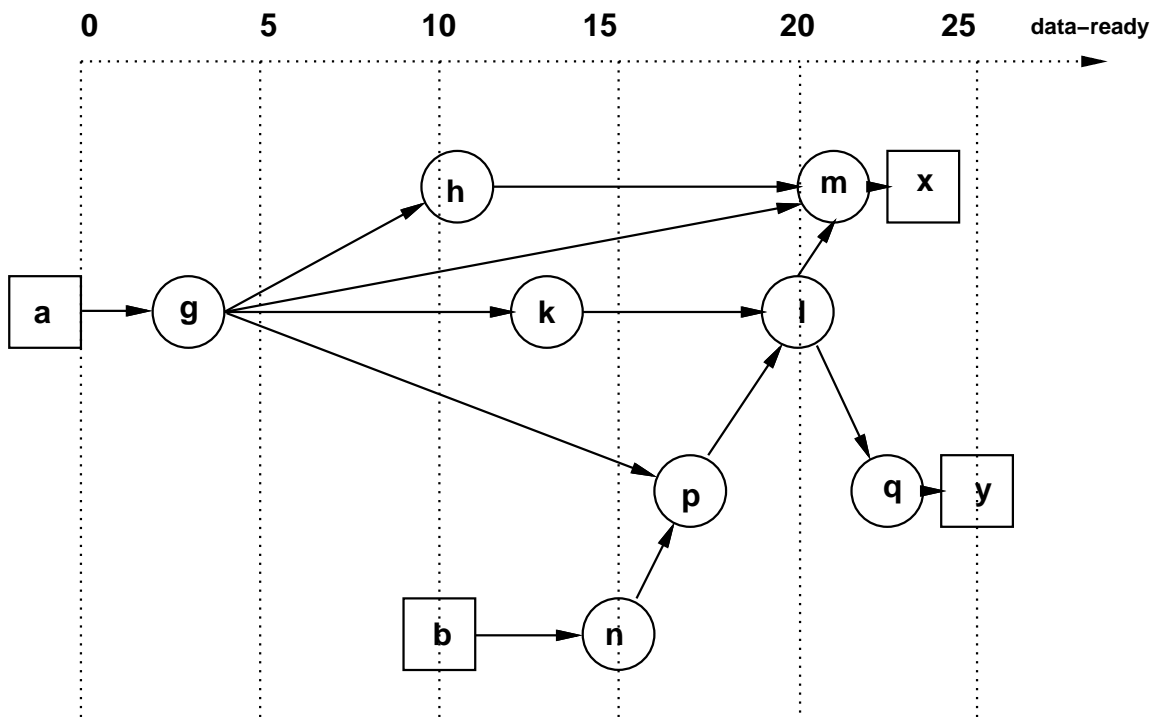

- Required data-ready times:

–  $\bar{t}_x = 25$  and  $\bar{t}_y = 25$ .

## Example

© GDM

- $s_x = 2; s_y = 0$
- $\bar{t}_m = 25 - 2 = 23; s_m = 23 - 21 = 2;$
- $\bar{t}_q = 25 - 3 = 22; s_q = 22 - 22 = 0;$
- $\bar{t}_l = \min\{23 - 1; 22 - 2\} = 20; s_l = 20 - 20 = 0;$
- $\bar{t}_h = 23 - 1 = 22; s_h = 22 - 11 = 11;$
- $\bar{t}_k = 20 - 3 = 17; s_k = 17 - 13 = 4;$
- $\bar{t}_p = 20 - 3 = 17; s_p = 17 - 17 = 0;$
- $\bar{t}_n = 17 - 2 = 15; s_n = 15 - 15 = 0;$
- $\bar{t}_b = 15 - 5 = 10; s_b = 10 - 10 = 0;$
- $\bar{t}_g = \min\{22 - 11; 17 - 10; 17 - 2\} = 7; s_g = 7 - 3 = 4;$
- $\bar{t}_a = 7 - 3 = 4; s_a = 4 - 0 = 4.$


## Topological critical path

© GDM

- Assume topologic computation of:
  - Data-ready by forward traversal.
  - Required data-ready by backward traversal.
- *Topological critical path*:
  - Input/output path with zero slacks.
  - Any increase in the vertex propagation delay affects the output data-ready time.
- A topological critical path may be *false*.
  - No event can propagate along that path.


# Example

© GDM

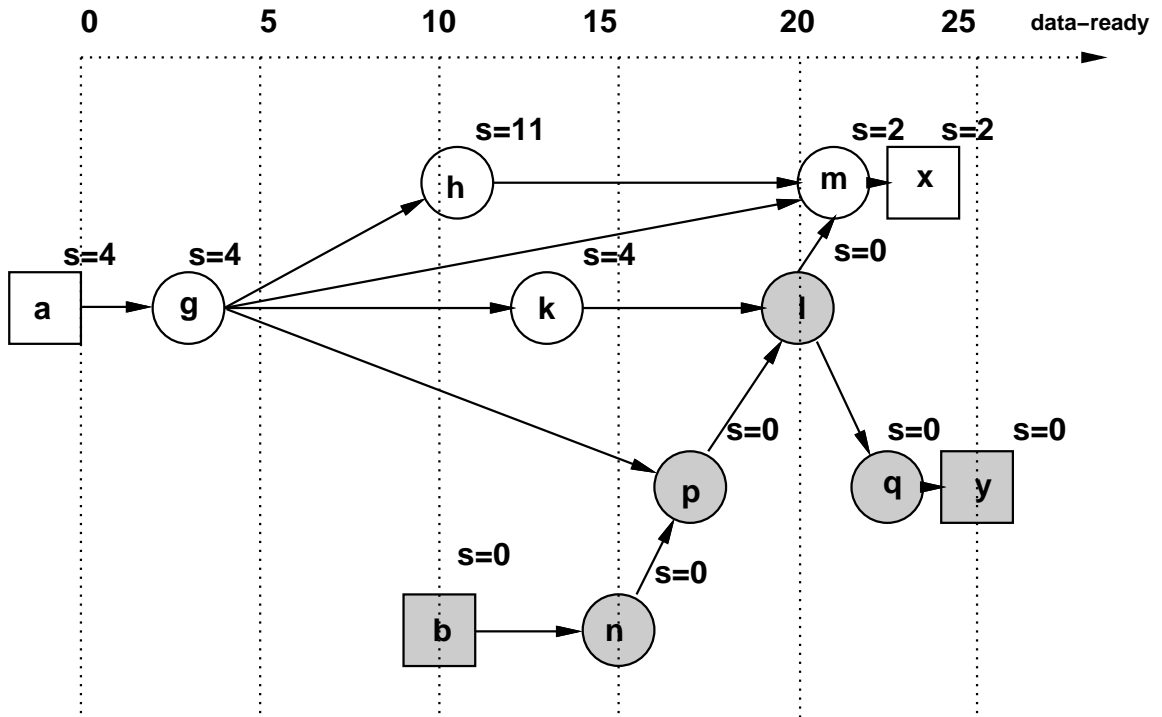

## Example

© GDM

 

- All gates have unit delay.
- All inputs ready at time 0.
- Longest topological path:  $(v_a, v_c, v_d, v_y, v_z)$ .
  - Path delay: 4 units.
- Critical true path:  $(v_a, v_c, v_d, v_y)$ .
  - Path delay: 3 units.

## Sensitizable paths

---

© GDM

- A path in a logic network is *sensitizable* if an event can propagate from its tail to its head.
- A *critical path* is a sensitizable path of maximum weight.
- Only sensitizable paths should be considered.
- Non-sensitizable paths are *false* and can be discarded.

## Sensitizable paths

© GDM

---

- *Path*:
  - Ordered set of vertices.
- *Inputs* to a vertex:
  - Direct predecessors.
- *Side-inputs* of a vertex:
  - Inputs not on the path.

## Dynamic sensitization condition

---


© GDM

- Path:  $P = (v_{x_0}, v_{x_1}, \dots, v_{x_m})$ .
- An event propagates along  $P$  if
  - $\partial f_{x_i} / \partial x_{i-1} = 1 \quad \forall i = 1, 2, \dots, m$ .
- Remark:
  - Boolean differences are function of the side-inputs and values on the side-inputs may change.
  - Boolean differences must be true *at the time that the event propagates*.



## Example

© GDM

 

- Path:  $(v_a, v_c, v_d, v_y, v_z)$ 
  - $\partial f_y / \partial d = e = 1$  at time 2.
  - $\partial f_z / \partial y = e' = 1$  at time 3.
- Not dynamically sensitizable because  $e$  settles at time 1.

## Static sensitization


---

© GDM

- Simpler, weaker model.
- We neglect the requirement on *when* the Boolean differences must be true to propagate an event.
- There is an assignment of primary inputs  $\mathbf{c}$  such that  $\partial f_{x_i}(\mathbf{c})/\partial x_{i-1} = 1 \forall i = 1, 2, \dots, m$ .
- May lead to *underestimate* delays.

## Example


© GDM

 

- Not statically sensitizable.

## Example

© GDM

 

- All gates have unit propagation delay.

## Example

---

© GDM

- Topological critical paths:
  - $\{(v_a, v_d, v_g, v_o); (v_b, v_d, v_g, v_o)\}$
  - Path delay: 3.
  - Not statically sensitizable.
- Other path:
  - $(v_a, v_e, v_o)$
  - Path delay: 2.
- Assume:
  - $c = 0$  and  $a, b$  dropping from 1 to 0.
  - Event propagates to output !!!

## Modes for delay computation

© GDM

- *Transition mode:*
  - Variables assumed to hold previous values.
    - \* Model circuit node capacitances.
  - Need *two* input vectors to test.
- *Floating mode:*
  - Circuit is assumed to be memoryless.
  - Need *only one* test vector.
  - Variables have unknown value until set by input test vector.

## Modes for delay computation

© GDM

---

- *Floating mode* delay computation is simpler than *transition mode* computation.
- *Floating mode* is a pessimistic approach.
- *Floating mode* is more robust:
  - *Transition mode* may not have the *monotone speed-up* property.

## Monotone speed-up property

---




© GDM

- Propagation delays are upper bounds.
  - What happens if gates are *faster* than expected?
- We must insure that speeding-up a gate does not slow-down the circuit.
  - Topological critical paths are robust.
  - What about dynamically sensitizable paths in transition mode?



# Example

© GDM

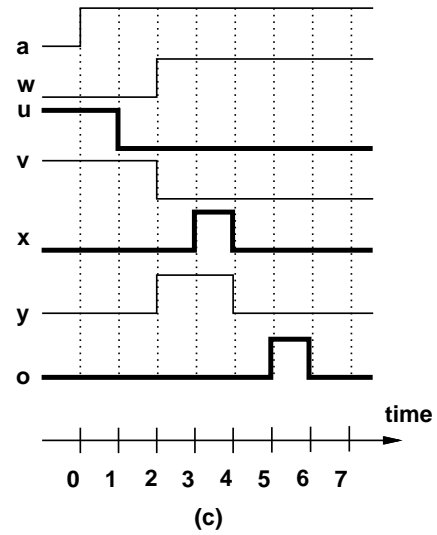 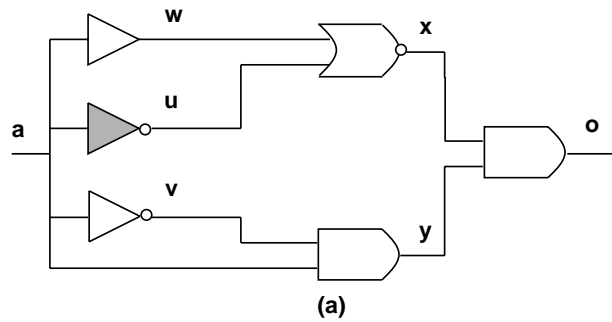

- Propagation delays: 2 units.
- Shaded gate: 3 units and 1 unit.

## Static co-sensitization

---

© GDM

- Assumption:
  - Circuit modeled by *AND*, *OR*, *INV* gates.
  - *INV* are irrelevant to the analysis.
  - Floating mode.
- Controlling values:
  - 0 for *AND* gate.
  - 1 for *OR* gate.
- Gate has *controlled value*.

## Static co-sensitization

© GDM

- Path:  $P = (v_{x_0}, v_{x_1}, \dots, v_{x_m})$ .
- A vector *statically co-sensitizes* a path to 1 (or to 0) if
  - $x_m = 1$  or (0) and
  - $v_{x_{i-1}}$  has a controlling value whenever  $v_{x_i}$  has a controlled value.
- Necessary condition for a path to be true.

## False path detection test


---

© GDM

- For all input vectors, one of the following is true:
  - (1) A gate is controlled and
    - \* the path provides a non-controlling value
    - \* a side-input provides a controlling value.
  - (2) A gate is controlled and
    - \* the path and a side-input have controlling values
    - \* the side-input presents the controlling value first.
  - (3) A gate is not controlled and
    - \* a side-input presents the non-controlling value last.

## Example

© GDM

 

- Path:  $(v_a, v_c, v_d, v_y, v_z)$ .
- For  $a = 0, b = 0$ 
  - condition (1) occurs at the OR gate.
- For  $a = 0, b = 1$ 
  - condition (2) occurs at the AND gate.
- For  $a = 1, b = 0$ 
  - condition (2) occurs at the OR gate.
- For  $a = 1, b = 1$ 
  - condition (1) occurs at the AND gate.

## Important problems

---

© GDM

- Check if circuit works at speed  $\bar{t}$ .
  - Verify that all true paths are faster than  $\bar{t}$ .
  - Show that all paths slower than  $\bar{t}$  are false.
- Compute groups of false paths.
- Compute critical true path:
  - Binary search for values of  $\bar{t}$ .
  - Show that all paths slower than  $\bar{t}$  are false.

## Algorithms for delay minimization

---

© GDM

- Alternate:
  - Critical path computation.
  - Logic transformation on critical vertices.
  
- Consider *quasi critical paths*:
  - Paths with near-critical delay.
  - Small slacks.

## Algorithms for delay minimization

© GDM

```
REDUCE_DELAY(  $G_n(V, E)$  ,  $\epsilon$ ){  
  repeat {  
    Compute critical paths and critical delay  $\tau$ ;  
    Set output required data-ready times to  $\tau$ ;  
    Compute slacks;  
     $U$  = vertex subset with slack lower than  $\epsilon$ ;  
     $W$  = select vertices in  $U$ ;  
    Apply transformations to vertices  $W$ ;  
  }until (no transformation can reduce  $\tau$  );  
}
```



## Transformations for delay reduction

© GDM

---

- Reduce propagation delay.
- Reduce dependencies from critical inputs.
- *Favorable* transformation:
  - Reduces local data-ready time.
  - Any data-ready time increase at other vertices is bounded by the local slack.

## Example



---

© GDM

- Unit gate delay.
- Transformation:
  - Elimination.
- Always favorable.
- Obtain several area/delay trade-off points.

# Example

© GDM

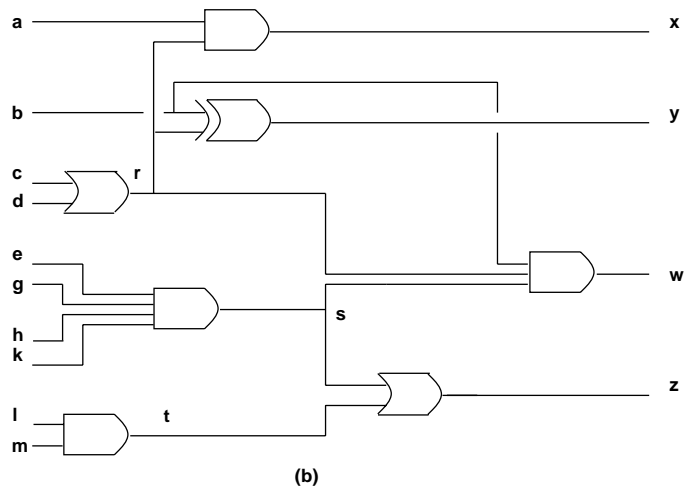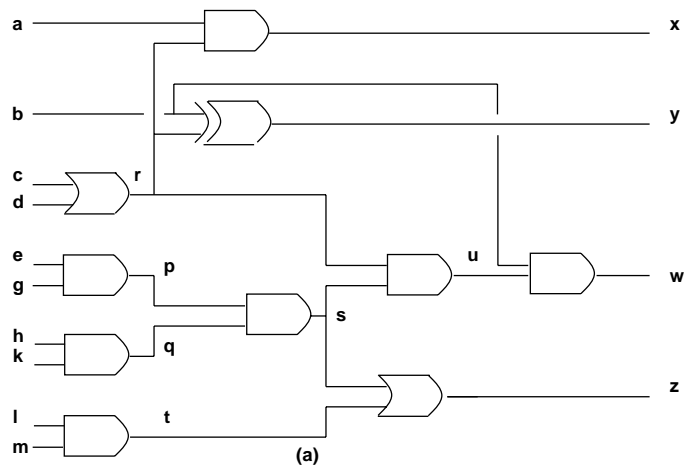

- Iteration 1: eliminate  $v_p, v_q$ . (No literal increase.)
- Iteration 2: eliminate  $v_u$ . (No literal increase.)
- Iteration 3: eliminate  $v_r, v_s, v_t$ . (Literals increase.)

## More refined delay models


---

© GDM



- Elimination:
  - Reduces one stage.
  - Yields more complex and slower gates.
  - May slow other paths.
- Substitution:
  - Adds one dependency.
  - Loads and slows a gate.
  - May slow other paths.

# Example


© GDM

 



(a)

  

(b)

 




(c)

  

(d)

# Example

© GDM

   

- NAND delay = 2. INVERTER delay = 1.
- All input data-ready are 0, except  $t_d = 3$ .

## Speed-up algorithm

© GDM

- Determine a subnetwork  $W$  of depth  $d$ .
- Collapse subnetwork by elimination.
- Duplicate vertices with successors outside  $W$ :
  - Record *area penalty*.
- Resynthesize  $W$  by timing-driven decomposition.
- Heuristics:
  - Choice of  $W$ .
  - Monitor *area penalty* and *potential speed-up*.

## Algorithms for minimal-area synthesis under delay constraints

---

© GDM

- Make network *timing feasible*.
  - May not be possible.
- *Minimize area* while preserving timing feasibility.
  - Use area optimization algorithms.
  - Monitor delays and slacks.
  - Reject transformations yielding negative slacks.



## Making a network timing feasible.

---



© GDM

- Naive approach:
  - Mark vertices with negative slacks.
  - Apply transformations to marked vertices.
- Refined approach.
  - Transform multiple I/O delay constraints into single constraint by delay padding.
  - Apply algorithms for CP minimization.
  - Stop when constraints are satisfied.

# Example

$$\bar{t} = [2332]^T$$

© GDM

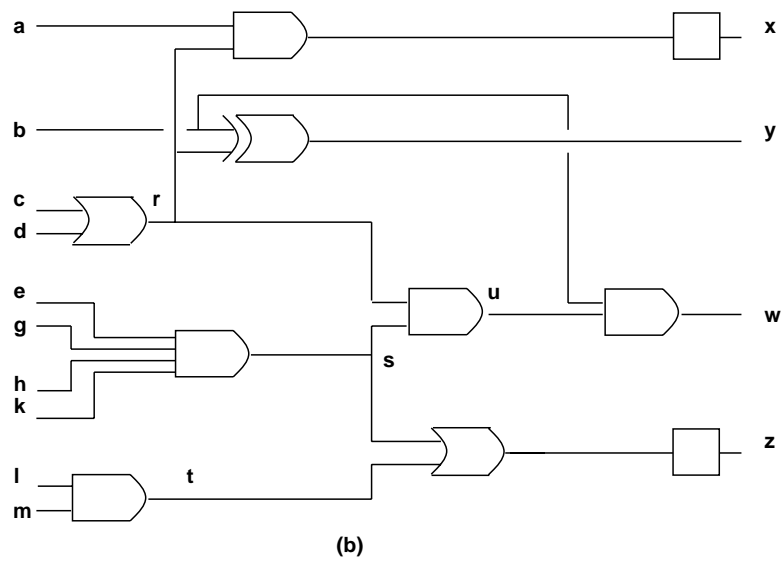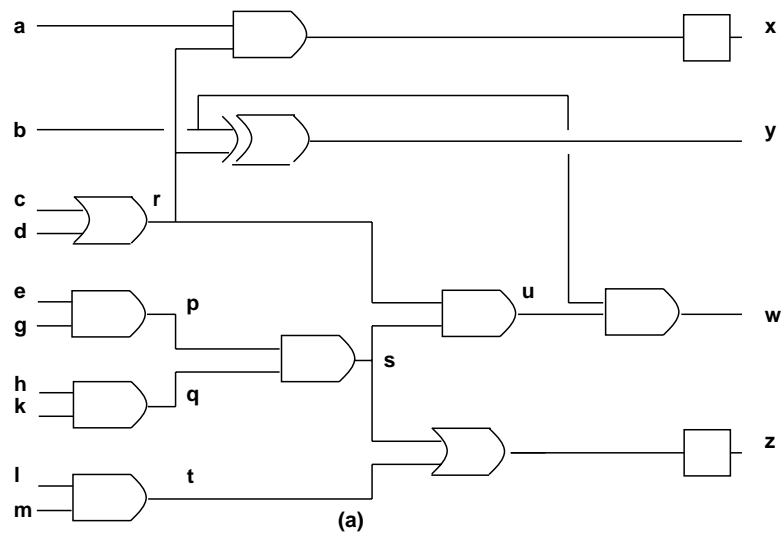

# Summary

---

© GDM

- Timing optimization is crucial for achieving competitive logic design.
- Timing optimization problems are hard:
  - Detection of critical paths.
    - \* Elimination of false paths.
  - Network transformations.