

# BOOLEAN METHODS

©Giovanni De Micheli

Stanford University

## Boolean methods

© GDM

- Exploit Boolean properties.
  - *Don't care* conditions.
- Minimization of the local functions.
- Slower algorithms, better quality results.


## External *don't care* conditions

© GDM

- *Controllability don't care* set  $CDC_{in}$ :
  - Input patterns never produced by the environment at the network's input.
- *Observability don't care* set  $ODC_{out}$ :
  - Input patterns representing conditions when an output is not observed by the environment.
  - Relative to each output.
  - Vector notation used:  $ODC_{out}$ .

## Example

© GDM

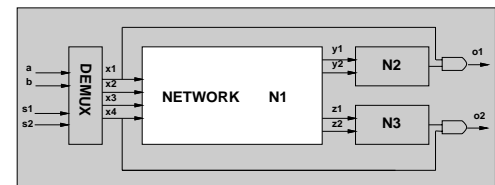

- Inputs driven by a de-multiplexer.
- $CDC_{in} = x'_1x'_2x'_3x'_4 + x_1x_2 + x_1x_3 + x_1x_4 + x_2x_3 + x_2x_4 + x_3x_4$ .
- Outputs observed when  $\begin{bmatrix} x_1 \\ x_4 \end{bmatrix} = \mathbf{1}$

$$ODC_{out} = \begin{bmatrix} x'_1 \\ x'_1 \\ x'_4 \\ x'_4 \end{bmatrix}$$


**Example**  
**overall external don't care set**

© GDM

$$DC_{ext} = CDC_{in} + ODC_{out} = \begin{bmatrix} x'_1 + x_2 + x_3 + x_4 \\ x'_1 + x_2 + x_3 + x_4 \\ x'_4 + x_2 + x_3 + x_1 \\ x'_4 + x_2 + x_3 + x_1 \end{bmatrix}$$

**Internal don't care conditions**

© GDM

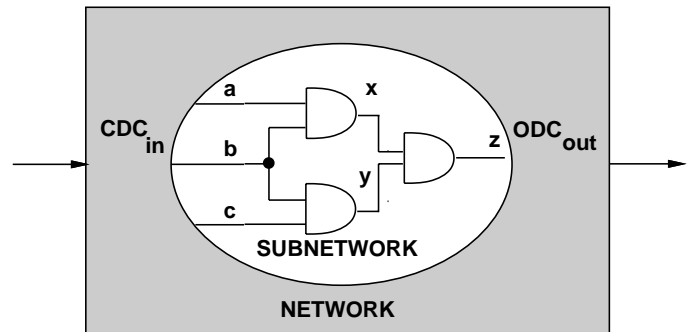


**Internal don't care conditions**

© GDM

- Induced by the network structure.
- *Controllability don't care* conditions:
  - Patterns never produced at the inputs of a subnetwork.
- *Observability don't care* conditions:
  - Patterns such that the outputs of a subnetwork are not observed.

**Example**

© GDM

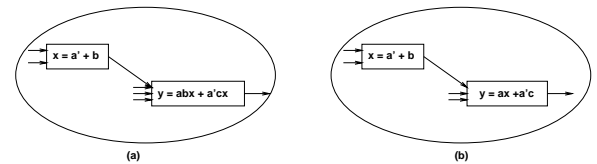

- CDC of  $v_y$  includes  $ab'x + a'x'$ .
- Minimize  $f_y$  to obtain:  $\tilde{f}_y = ax + a'c$ .

## Satisfiability *don't care* conditions

© GDM

- Invariant of the network:
  - $x = f_x \rightarrow x \neq f_x \subseteq SDC$ .
- $SDC = \sum_{v_x \in V^G} x \oplus f_x$
- Useful to compute controllability *don't cares*.

## CDC computation

© GDM

- Network traversal algorithm:
  - Consider different *cuts* moving from input to output.
- Initial CDC is  $CDC_{in}$ .
- Move *cut* forward.
  - Consider SDC contributions of predecessors.
  - Remove unneeded variables by *consensus*.

## CDC computation


© GDM

```

CONTROLLABILITY( $G_n(V, E)$ ,  $CDC_{in}$ ) {
   $C = V^I$ ;
   $CDC_{cut} = CDC_{in}$ ;
  foreach vertex  $v_x \in V$  in topological order {
     $C = C \cup v_x$ ;
     $CDC_{cut} = CDC_{cut} + f_x \oplus x$ ;
     $D = \{v \in C \text{ s.t. all dir. succ. of } v \text{ are in } C\}$ 
    foreach vertex  $v_y \in D$ 
       $CDC_{cut} = \mathcal{C}_y(CDC_{cut})$ ;
     $C = C - D$ ;
  };
   $CDC_{out} = CDC_{cut}$ ;
}
    
```

## Example

© GDM

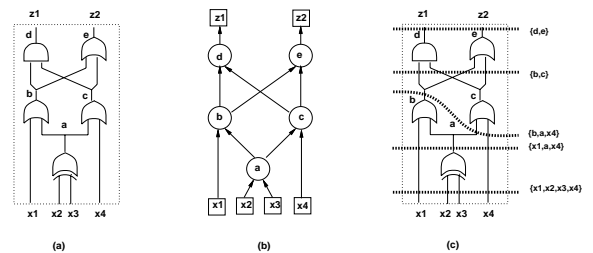

### Example

© GDM

- Assume  $CDC_{in} = x'_1 x'_4$ .
- Select vertex  $v_a$ :
  - Contribution to  $CDC_{cut}$ :  $a \oplus (x_2 \oplus x_3)$ .
  - Drop variables  $D = \{x_2, x_3\}$  by consensus:
  - $CDC_{cut} = x'_1 x'_4$ .
- Select vertex  $v_b$ :
  - Contribution to  $CDC_{cut}$ :  $b \oplus (x_1 + a)$ .
  - \*  $CDC_{cut} = x'_1 x'_4 + b \oplus (x_1 + a)$ .
  - Drop variable  $x_1$  by consensus:
  - \*  $CDC_{cut} = b' x'_4 + b' a$ .
- ...
- $CDC_{out} = e' = z'_2$ .

### CDC computation by image computation

© GDM

- Network behavior at  $cut$ :  $\mathbf{f}$ .
- $CDC_{cut}$  is just the complement of the *image* of  $(CDC_{in})'$  with respect to  $\mathbf{f}$ .
- $CDC_{cut}$  is just the complement of the *range* of  $\mathbf{f}$  when  $CDC_{in} = \emptyset$ .
- Range can be computed recursively.
  - Terminal case: scalar function.
  - \* Range of  $y = f(\mathbf{x})$  is  $y + y'$  (any value) unless  $f$  (or  $f'$ ) is a tautology and the range is  $y$  (or  $y'$ ).

### Example

© GDM


#### RANGE VECTORS



- $range(\mathbf{f}) = d \ range((b + c)|_{d=bc=1}) + d' \ range((b + c)|_{d=bc=0})$
- When  $d = 1$ , then  $bc = 1 \rightarrow b + c = 1$  is TAUTOLOGY.
- If I choose 1 as top entry in output vector:
  - the bottom entry is also 1.
  - $\begin{bmatrix} 1 \\ ? \end{bmatrix} \rightarrow \begin{bmatrix} 1 \\ 1 \end{bmatrix}$
- When  $d = 0$ , then  $bc = 0 \rightarrow b + c = \{0, 1\}$ .
- If I choose 0 as top entry in output vector:
  - the bottom entry can be 0 or 1.
- $range(\mathbf{f}) = de + d'(e + e') = de + d' = d' + e$

### Example


© GDM

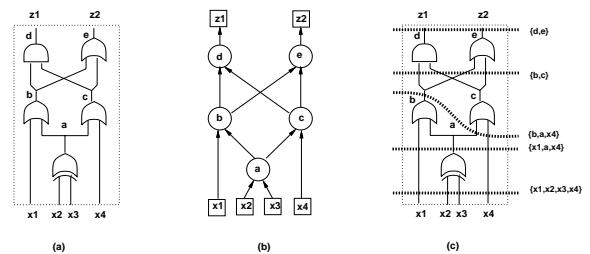

$$\mathbf{f} = \begin{bmatrix} f^1 \\ f^2 \end{bmatrix} = \begin{bmatrix} (x_1 + a)(x_4 + a) \\ (x_1 + a) + (x_4 + a) \end{bmatrix} = \begin{bmatrix} x_1 x_4 + a \\ x_1 + x_4 + a \end{bmatrix}$$

### Example

© GDM

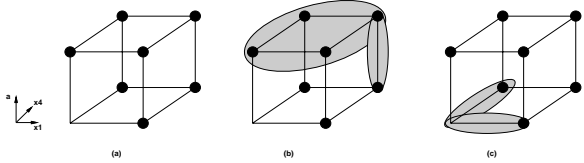

$$\begin{aligned}
 \text{range}(\mathbf{f}) &= \\
 &= d \text{ range}(f^2|_{(x_1, x_4+a)=1}) + \\
 &\quad d' \text{ range}(f^2|_{(x_1, x_4+a)=0}) \\
 &= d \text{ range}(x_1 + x_4 + a|_{(x_1, x_4+a)=1}) + \\
 &\quad d' \text{ range}(x_1 + x_4 + a|_{(x_1, x_4+a)=0}) \\
 &= d \text{ range}(1) + d' \text{ range}(a'(x_1 \oplus x_4)) \\
 &= de + d'(e + e') \\
 &= e + d'
 \end{aligned}$$

- $CDC_{out} = (e + d')' = de' = z_1 z_2'$ .


### Perturbation method

© GDM

- Modify network by adding an extra input  $\delta$ .
- Extra input can flip polarity of a signal  $x$ .
- Replace local function  $f_x$  by  $f_x \oplus \delta$ .
- Perturbed terminal behavior:  $\mathbf{f}^x(\delta)$ .

### Example

© GDM

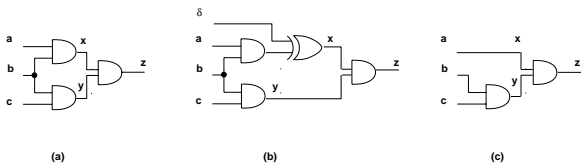

### Observability *don't care* conditions

© GDM

- Conditions under which a change in polarity of a signal  $x$  is not perceived at the outputs.
- Complement of the Boolean difference:
  - $\partial f / \partial x = f|_{x=1} \oplus f|_{x=0}$ .
- Equivalence of perturbed function:  $\mathbf{f}^x(0) \oplus \overline{\mathbf{f}^x(1)}$ .

## Observability *don't care* computation

© GDM

- Problem:
  - Outputs are not expressed as function of all variables.
  - If network is flattened to obtain  $f$ , it may explode in size.
- Requirement:
  - Local rules for ODC computation.
  - Network traversal.

## Single-output network with tree structure


© GDM

- Traverse network tree.
- At root:
  - $ODC_{out}$  is given.
- At internal vertices:
  - $ODC_x = (\partial f_y / \partial x)' + ODC_y$
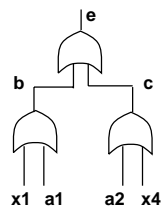
## Example

© GDM


$$\begin{aligned} e &= b + c \\ b &= x_1 + a_1 \\ c &= x_4 + a_2 \end{aligned}$$



- Assume  $ODC_{out} = ODC_e = 0$ .
- $ODC_b = (\partial f_e / \partial b)' = (b + c)|_{b=1} \oplus (b + c)|_{b=0} = c$ .
- $ODC_c = (\partial f_e / \partial c)' = b$ .
- $ODC_{x_1} = ODC_b + (\partial f_b / \partial x_1)' = c + a_1$ .
- ...

## General networks


© GDM

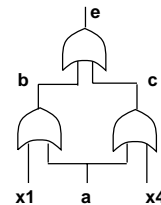

- Fanout reconvergence.
- For each vertex with two (or more) fanout stems:
  - The contribution of the ODC along the stems cannot be added *tout court*.
  - Interplay of different paths.
- More elaborate analysis.

## Two-way fanout stem

© GDM

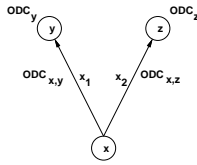

- Compute ODC sets associated with edges.
- Combine ODCs at vertex.
- Formula derivation:
  - Assume two equal perturbations on the edges.
  - $\mathbf{ODC}_x = \mathbf{f}^{x_1, x_2}(1, 1) \bar{\oplus} \mathbf{f}^{x_1, x_2}(0, 0)$

## ODC formula derivation

© GDM

$$\begin{aligned}
 \mathbf{ODC}_x &= \mathbf{f}^{x_1, x_2}(1, 1) \bar{\oplus} \mathbf{f}^{x_1, x_2}(0, 0) \\
 &= \mathbf{f}^{x_1, x_2}(1, 1) \bar{\oplus} \mathbf{f}^{x_1, x_2}(0, 0) \\
 &\quad \bar{\oplus} (\mathbf{f}^{x_1, x_2}(0, 1) \bar{\oplus} \mathbf{f}^{x_1, x_2}(0, 1)) \\
 &= (\mathbf{f}^{x_1, x_2}(1, 1) \bar{\oplus} \mathbf{f}^{x_1, x_2}(0, 1)) \\
 &\quad \bar{\oplus} (\mathbf{f}^{x_1, x_2}(0, 1) \bar{\oplus} \mathbf{f}^{x_1, x_2}(0, 0)) \\
 &= \mathbf{ODC}_{x, y} |_{\delta_2=1} \bar{\oplus} \mathbf{ODC}_{x, z} |_{\delta_1=0} \\
 &= \mathbf{ODC}_{x, y} |_{x_2=x'} \bar{\oplus} \mathbf{ODC}_{x, z} |_{x_1=x} \\
 &= \mathbf{ODC}_{x, y} |_{x=x'} \bar{\oplus} \mathbf{ODC}_{x, z}
 \end{aligned}$$

- Because  $x = x_1 = x_2$ .

## Multi-way stems Theorem

© GDM

- Let  $v_x \in V$  be any internal or input vertex.
- Let  $\{x_i, i = 1, 2, \dots, p\}$  be the edge vars corresponding to  $\{(x, y_i) ; i = 1, 2, \dots, p\}$ .
- Let  $\mathbf{ODC}_{x, y_i}$ ,  $i = 1, 2, \dots, p$  the edge ODCs.
- $\mathbf{ODC}_x = \bar{\oplus}_{i=1}^p \mathbf{ODC}_{x, y_i} |_{x_{i+1}=\dots=x_p=x'}$

## Observability *don't care* algorithm


© GDM

```

OBSERVABILITY( $G_n(V, E)$ ,  $\mathbf{ODC}_{out}$ ) {
  foreach vertex  $v_x \in V$  in reverse topological order {
    for ( $i = 1$  to  $p$ )
       $\mathbf{ODC}_{x, y_i} = (\partial f_{y_i} / \partial x)' \mathbf{1} + \mathbf{ODC}_{y_i}$ ;
     $\mathbf{ODC}_x = \bar{\oplus}_{i=1}^p \mathbf{ODC}_{x, y_i} |_{x_{i+1}=\dots=x_p=x'}$ ;
  }
}
    
```

## Example

© GDM

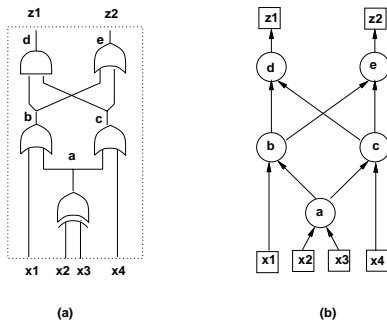

$$\begin{aligned} \text{ODC}_d &= \begin{pmatrix} 0 \\ 1 \end{pmatrix} ; \text{ODC}_e = \begin{pmatrix} 1 \\ 0 \end{pmatrix} ; \text{ODC}_c = \begin{pmatrix} b \\ c \end{pmatrix} ; \text{ODC}_b = \begin{pmatrix} c' \\ c \end{pmatrix} \\ \text{ODC}_{a,b} &= \begin{pmatrix} c' + x_1 \\ c + x_1 \end{pmatrix} = \begin{pmatrix} a'x'_4 + x_1 \\ a + x_4 + x_1 \end{pmatrix} \\ \text{ODC}_{a,c} &= \begin{pmatrix} b' + x_4 \\ b + x_4 \end{pmatrix} = \begin{pmatrix} a'x'_1 + x_4 \\ a + x_1 + x_4 \end{pmatrix} \\ \text{ODC}_a &= \text{ODC}_{a,b|a=d} \oplus \text{ODC}_{a,c} = \begin{pmatrix} ax'_4 + x_1 \\ a' + x_4 + x_1 \end{pmatrix} \oplus \begin{pmatrix} a'x'_1 + x_4 \\ a + x_1 + x_4 \end{pmatrix} = \\ &= \begin{pmatrix} x_1x_4 \\ x_1 + x_4 \end{pmatrix} \end{aligned}$$

## Transformations with *don't cares*

© GDM

- Boolean simplification:
  - Use standard minimizer (Espresso).
  - Minimize the number of literals.
- Boolean substitution:
  - Simplify a function by adding an extra input.
  - Equivalent to simplification with global *don't care* conditions.

## Example

### Boolean substitution

© GDM

- Substitute  $q = a + cd$  into  $f_h = a + bcd + e$  to get  $f_h = a + bq + e$ .
- SDC set:  $q \oplus (a + cd) = q'a + q'cd + qa'(cd)'$ .
- Simplify  $f_h = a + bcd + e$  with  $q'a + q'cd + qa'(cd)'$  as *don't care*.
- Simplification yields  $f_h = a + bq + e$ .
- One literal less by changing the support of  $f_h$ .

## Single-vertex optimization

© GDM

```

SIMPLIFY_SV(  $G_n(V, E)$  ){
  repeat {
     $v_x$  = selected vertex ;
    Compute the local don't care set  $DC_x$ ;
    Optimize the function  $f_x$  ;
  }until (no more reduction is possible)
}
    
```




## Optimization and perturbations

© GDM

- Replace  $f_x$  by  $g_x$ .
- Perturbation  $\delta_x = f_x \oplus g_x$ .
- Condition for feasible replacement:
  - Perturbation bounded by local *don't care* set
  - $\delta_x \subseteq \mathbf{DC}_{ext} + \mathbf{ODC}_x$
  - If  $x$  not a primary input consider also CDC set.

## Example

© GDM

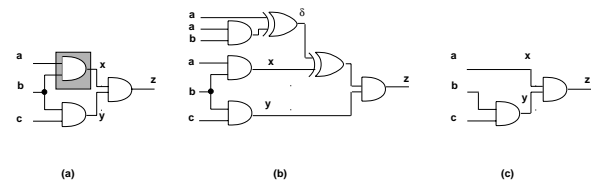

- No external *don't care* set.
- Replace AND by wire:  $g_x = a$
- Analysis:
  - $\delta = f_x \oplus g_x = ab \oplus a = ab'$ .
  - $\mathbf{ODC}_x = y' = b' + c'$ .
  - $\delta = ab' \subseteq \mathbf{DC}_x = b' + c' \Rightarrow$  feasible!

## Degrees of freedom

© GDM

- Fully represented by *don't care* conditions:
  - External *don't cares*.
  - Internal observability and controllability.
- *Don't cares* represent an *upper bound* on the perturbation.
- Approximations:
  - Use smaller *don't care* sets to speed-up the computation.


## Multiple-vertex optimization

© GDM

- Simplify more than one local function at a time.
- Potentially better (more general) approach.
- Analysis:
  - Multiple perturbations.
- Condition for feasible replacement:
  - *Upper and lower bounds* on the perturbation.
  - Boolean relation model.

### Example


© GDM

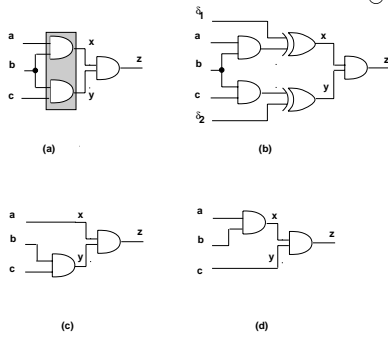

- The two perturbations are related.
- Cannot change simultaneously:
  - $ab \rightarrow a$ .
  - $cb \rightarrow c$ .

### Multiple-vertex optimization Boolean relation model

© GDM

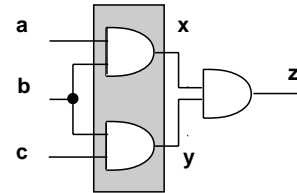

a	b	c	x, y
0	0	0	{ 00, 01, 10 }
0	0	1	{ 00, 01, 10 }
0	1	0	{ 00, 01, 10 }
0	1	1	{ 00, 01, 10 }
1	0	0	{ 00, 01, 10 }
1	0	1	{ 00, 01, 10 }
1	1	0	{ 00, 01, 10 }
1	1	1	{ 11 }

### Multiple-vertex optimization Boolean relation model

© GDM

- Compute Boolean relation:
  - Flatten the network. Analyze patterns.
  - Derive equivalence relation from ODCs.
- Use relation minimizer.

- Example of minimum function:
 

a	b	c	x, y
1	*	*	10
*	1	1	01

### Multiple-vertex optimization Boolean relation model

© GDM

```

SIMPLIFY_MVR( Gn(V, E) ){
  repeat {
    U = selected vertex subset;
    foreach vertex vx ∈ U
      Compute OCDx;
      Determine the equiv. classes of the Boolean relation
        of the subnetwork induced by U;
      Find an optimal function compatible with the relation
        using a relation minimizer;
    }until (no more reduction is possible);
}
    
```

**Multiple-vertex optimization**  
compatible *don't cares*

© GDM

- Determine *compatible don't cares* :
  - CODCs: subset of ODCs.
  - Decouple dependencies.
  - Reduced degrees of freedom.
- Using compatible ODCs, only *upper bounds* on the perturbation need to be satisfied.


**Example**  
**two perturbations**

© GDM

- First vertex:
  - CODC equal to its ODC set.
  - $CODC_{x_1} = ODC_{x_1}$ .
- The second vertex:
  - CODC smaller than its ODC to be safe enough to allow transformations permitted by the first ODC.
  - $CODC_{x_2} = C_{x_1}(ODC_{x_2}) + ODC_{x_2}ODC'_{x_1}$
- Order dependence.

**Example**  
**first vertex  $v_y$**


© GDM

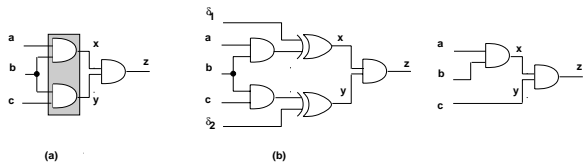

- $CODC_y = ODC_y = x' = b' + a'$
- $ODC_x = y' = b' + c'$
- $CODC_x = C_y(ODC_x) + ODC_x(ODC_y)' = C_y(y') + y'x = y'x = (b' + c')ab = abc'$ .

**Example (2)**

© GDM

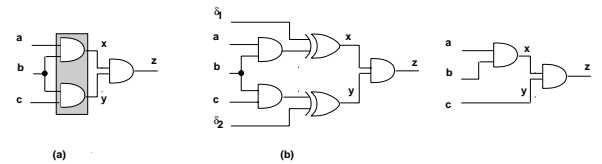

- Allowed perturbation:
  - $f_y = bc \rightarrow g_y = c$ .
  - $\delta_y = bc \oplus c = b'c \subseteq CODC_y = b' + a'$ .
- Disallowed perturbation:
  - $f_x = ab \rightarrow g_x = a$ .
  - $\delta_x = ab \oplus a = ab' \not\subseteq CODC_x = abc'$ .
- The converse holds if  $v_x$  is the first vertex.

## Multiple-vertex optimization compatible *don't cares*

© GDM

```
SIMPLIFY_MV(  $G_n(V, E)$  ){  
  repeat {  
     $U$  = selected vertex subset;  
    foreach vertex  $v_x \in U$   
      Compute  $COCD_x$  and the corresponding  
      local don't care subset  $\widetilde{DC}_x$ ;  
      Optimize simultaneously the functions at  $U$ ;  
    }until (no more reduction is possible);  
}
```

## Summary Boolean methods

© GDM

- Boolean methods exploit *don't care* sets and simplification of logic representations.
- *Don't care* set computation:
  - Controllability and observability.
- Single and multiple transformations.

## Synthesis and testability

© GDM

- Testability:
  - Ease of testing a circuit.
- Assumptions:
  - Combinational circuit.
  - Single or multiple *stuck-at* faults.
- Full testability:
  - Possible to generate test set for all faults.
  - Restrictive interpretation.

## Test for *stuck-ats*

© GDM

- Net  $y$  stuck-at 0.
  - Input pattern that sets  $y$  to true.
  - Observe output.
  - Output of faulty circuit differs.
- Net  $y$  stuck-at 1.
  - Same, but set  $y$  to false.
- Need *controllability* and *observability*.

## Test sets

*don't care interpretation*

© GDM

- Stuck-at 0 on net  $y$ .
  - $\{\mathbf{t} | y(\mathbf{t}) \cdot ODC'_y(\mathbf{t}) = 1\}$ .
- Stuck-at 1 on net  $y$ .
  - $\{\mathbf{t} | y'(\mathbf{t}) \cdot ODC'_y(\mathbf{t}) = 1\}$ .


## Using testing methods for synthesis

© GDM

- Redundancy removal.
  - Use TPG to search for untestable faults.
- If stuck-at 0 on net  $y$  is untestable:
  - Set  $y = 0$ .
  - Propagate constant.
- If stuck-at 1 on  $y$  is untestable:
  - Set  $y = 1$ .
  - Propagate constant.


## Example

© GDM

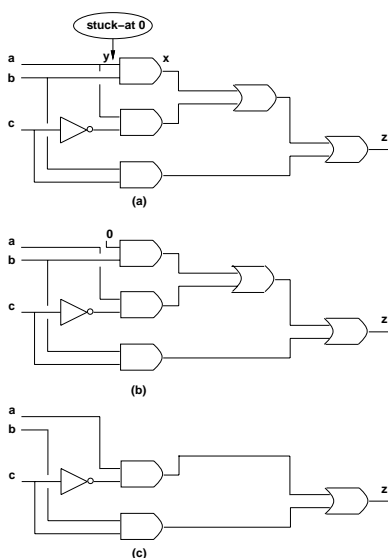

## Redundancy removal and perturbation analysis

© GDM

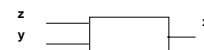

- Stuck-at 0 on  $y$ .
  - $y$  set to 0. Namely  $g_x = f_x|_{y=0}$ .
  - Perturbation:
    - \*  $\delta = f_x \oplus f_x|_{y=0} = y \cdot \partial f_x / \partial y$ .
- Perturbation is feasible  $\Leftrightarrow$  fault is untestable.
  - No input vector  $\mathbf{t}$  can make  $y(\mathbf{t}) \cdot ODC'_y(\mathbf{t})$  true.
  - No input vector can make  $y(\mathbf{t}) \cdot ODC'_x(\mathbf{t}) \cdot \partial f_x / \partial y$  true.
    - \* because  $ODC_y = ODC_x + (\partial f_x / \partial y)'$ .

## Redundancy removal and perturbation analysis

© GDM

- Assume untestable stuck-at 0 fault.
- $y \cdot ODC'_x \cdot \partial f_x / \partial y \subseteq SDC$ .
- Local *don't care* set:
  - $DC_x \supseteq ODC_x + y \cdot ODC'_x \cdot \partial f_x / \partial y$ .
  - $DC_x \supseteq ODC_x + y \cdot \partial f_x / \partial y$ .
- Perturbation  $\delta = y \cdot \partial f_x / \partial y$ .
  - Included in the local *don't care* set.

## Synthesis for testability

© GDM

- Synthesize networks that are fully testable.
  - Single stuck-at faults.
  - Multiple stuck-at faults.
- Two-level forms.
- Multiple-level networks.

## Two-level forms


© GDM

- Full testability for single stuck-at faults:
  - Prime and irredundant cover.
- Full testability for multiple stuck-at faults:
  - Prime and irredundant cover when:
    - \* Single-output function.
    - \* No product term sharing.
    - \* Each component is PI.

## Example

$$f = a'b' + b'c + ac + ab$$

© GDM

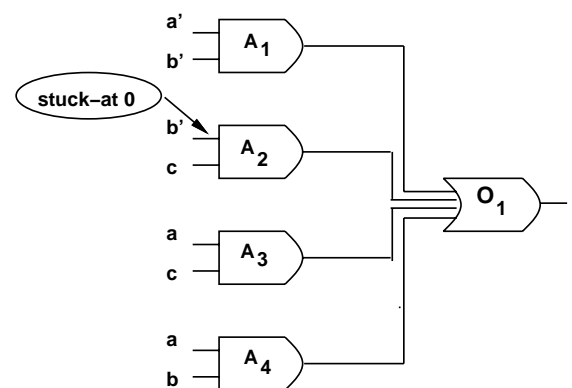

## Multiple-level networks Definitions

© GDM

- A logic network  $G_n(V, E)$ , with local functions in *sum of product* form.
- Prime and irredundant (PI):
  - No literal nor implicant of any local function can be dropped.
- Simultaneously prime and irredundant (SPI):
  - No subset of literals and/or implicants can be dropped.

## Multiple-level networks Theorems

© GDM

- A logic network is PI and only if:
  - its AND-OR implementation is fully testable for single stuck-at faults.
- A logic network is SPI if and only if:
  - its AND-OR implementation is fully testable for multiple stuck-at faults.

## Multiple-level networks Synthesis

© GDM

- Compute full local *don't care* sets.
  - Make all local functions PI w.r. to *don't care* sets.
- Pitfall:
  - *Don't cares* change as functions change.
- Solution:
  - Iteration (Espresso-MLD).
- If iteration converges, network is fully testable.

## Multiple-level networks Synthesis

© GDM

- Flatten to two-level form.
  - When possible – no size explosion.
- Make SPI by disjoint logic minimization.
- Reconstruct multiple-level network:
  - *Algebraic transformations preserve multifault testability.*

## Summary

---

© GDM

- Synergy between synthesis and testing.
- Testable networks correlate to small-area networks.
- *Don't care* conditions play a major role.