 


Functional Verification & Abstraction of Arithmetic Circuits




Maciej Ciesielski, Cunxi Yu

University of Massachusetts, Amherst
ciesiel@ecs.umass.edu

Arithmetic Verification

 - Functional verification
 - Does the circuit implement the required arithmetic function?
 - *What function* does this circuit implement ?
- Extracting arithmetic function from gate-level implementations
 - Avoid Boolean methods,
bit-blasting
 - Use Computer Algebra methods



Computer Algebra Approach

- Circuit specification F_{spec} and implementation B represented by pseudo-Boolean polynomials

- Check if implementation B satisfies specification F_{spec} by reducing F_{spec} modulo B

$$F_{spec} \xrightarrow{B} r$$


- If $r = 0$, the circuit is correct
 - If $r \neq 0$, circuit *may* still be correct but need canonical *Groebner basis* (*GB*) to determine if $r = 0$
 - Difficult to compute, computationally complex
 - *GB* must include polynomials $\langle x^2 - x \rangle$ (for all Boolean signals x)

- Methods differ in ways they accomplish reduction
 - Arithmetic Bit-level (ABL) representation [[Wienand'08, Pavlenko'11](#)]
 - Also applied to Galois Fields (GF) [[Kalla'14, TComp'15](#)]

Computer Algebra Approach: Example

□ Example: 2-bit adder

 
- $F_{spec} = a_0 + b_0 + 2a_1 + 2b_1 - 4r_2 - 2r_1 - r_0$
- B = list of polynomials describing gates
- Proof of functional correctness done by *polynomial division* (similar to our *forward rewriting*)



$$\left\{ \begin{array}{l} g_1 = r_0 - (a_0 + b_0 - 2a_0b_0) \\ g_2 = c - (a_0b_0) \\ g_3 = d - (a_1 + b_1 - 2a_1b_1) \\ g_4 = r_1 - (c + d - 2cd) \\ g_5 = f - (cd) \\ g_6 = e - (a_1b_1) \\ g_7 = r_2 - (e + f - ef) \end{array} \right.$$

Polynomial Division (1)

 - Divide polynomial $F_{spec} = a_0 + b_0 + 2a_1 + 2b_1 - 4r_2 - 2r_1 - r_0$




$$\begin{aligned}
 F_{spec} &= a_0 + b_0 + 2a_1 + 2b_1 - 4r_2 - 2r_1 - r_0 \\
 &= -(a_0 + b_0 - 2a_0b_0) + r_0 + b_0 + 2a_1 + 2b_1 - 4r_2 - 2r_1 - r_0 \\
 &= 2a_0b_0 + 2a_1 + 2b_1 - 4r_2 - 2r_1 \\
 &= -2(a_0b_0) + 2c + 2a_0b_0 + 2a_1 + 2b_1 - 4r_2 - 2r_1 \\
 &= 2c + 2a_1 + 2b_1 - 4r_2 - 2r_1 \\
 &= -2(a_1 + b_1 - 2a_1b_1) + 2d + 2c + 2a_1 + 2b_1 - 4r_2 - 2r_1 \\
 &= 4a_1b_1 + 2d + 2c - 4r_2 - 2r_1 \\
 &= -2(c + d - 2cd) + 2r_1 + 4a_1b_1 + 2d + 2c - 4r_2 - 2r_1 \\
 &= 4cd + 4a_1b_1 - 4r_2 \\
 &= -4(cd) + 4f + 2cd + 4a_1b_1 - 4r_2 \\
 &= 4f + 4a_1b_1 - 4r_2 \\
 &= -4(a_1b_1) + 4e + 4f + 4a_1b_1 - 4r_2 \\
 &= 4e + 4f - 4r_2 \\
 &= -4(e + f - ef) + 4r_2 + 4e + 4f - 4r_2 \\
 &= 4ef
 \end{aligned}$$

$$\left\{
 \begin{aligned}
 g_1 &= r_0 - (a_0 + b_0 - 2a_0b_0) \\
 g_2 &= c - (a_0b_0) \\
 g_3 &= d - (a_1 + b_1 - 2a_1b_1) \\
 g_4 &= r_1 - (c + d - 2cd) \\
 g_5 &= f - (cd) \\
 g_6 &= e - (a_1b_1) \\
 g_7 &= r_2 - (e + f - ef)
 \end{aligned}
 \right.$$

Non-zero residual ! Is circuit correct ?

Polynomial Division (2)

 - Continue dividing residual polynomial { 4ef }



$$\left\{ \begin{array}{l} g_1 = r_0 - (a_0 + b_0 - 2a_0b_0) \\ g_2 = c - (a_0b_0) \\ g_3 = d - (a_1 + b_1 - 2a_1b_1) \\ g_4 = r_1 - (c + d - 2cd) \\ g_5 = f - (cd) \\ g_6 = e - (a_1b_1) \\ g_7 = r_2 - (e + f - ef) \end{array} \right.$$

4ef

$$= 4e(cd)$$

$$= 4(a_1b_1)(cd)$$

$$= 4(a_1b_1)(a_0b_0)(a_1 + b_1 - 2a_1b_1)$$

$$= 4(a_1b_1)(a_1 + b_1 - 2a_1b_1)(a_0b_0)$$

$$= 4(a_1b_1a_1 + a_1b_1b_1 - 2a_1b_1a_1b_1)(a_0b_0)$$

$$= 4(0)(a_0b_0)$$

$$= 4ef = 0$$


- Hence $(F_{spec} \bmod B) = 0$, the circuit correctly implements a 2-bit adder.
- But many dividing steps are needed

Computer Algebra Approach - summary

- Another way of looking at the problem:

Instead of reducing F_{spec} modulo B , we can

 - Rewrite $\text{Sig}_{in} \rightarrow \text{Sig}_{out}$ (**forward rewriting**), or
- Rewrite $\text{Sig}_{out} \rightarrow \text{Sig}_{in}$ (**backward rewriting**)



Backward Rewriting


- Replace gate output by its equation
 - Backward *symbolic simulation*
 - No residual expression (r) !
 - But ... the expression can explode

$$f_3 = 4r_2 + 2r_1 + r_0$$

$$\begin{aligned} f_2 &= 4(f + e - ef) + 2r_1 + r_0 \\ &= 4f + 4e - 4ef + 2r_1 + r_0 \end{aligned}$$

$$\begin{aligned} f_1 &= 4e + 4(cd) - 4e(cd) + 2(c + d - 2cd) + r_0 \\ &= 4e + 2c + 2d + r_0 - 4ecd \end{aligned}$$
 
$$\begin{aligned} f_0 &= 4(a_1b_1) + 2(a_0b_0) + 2(a_1 + b_1 - 2a_1b_1) \\ &\quad + (a_0 + b_0 - 2a_0b_0) \\ &\quad - 4(a_1b_1)(a_0b_0)(a_1 + b_1 - 2a_1b_1) \\ &= 2a_1 + 2b_1 + a_0 + b_0 \end{aligned}$$



It matches the specification:
→ *circuit is correct*

Backward Rewriting - ordering

□ How efficient is it ?

- Simpler than forward rewriting (*no residual*)
- Cancellations happen during rewriting
- But expressions may explode

$$8z_3^{(1,2)} = 8x_1x_5$$

$$4z_2^{(1,2)} = 4x_1 + 4x_5 - 8x_1x_5$$

$$8z_3^{(3,4)} = 8x_1x_2x_3$$

$$4z_2^{(3,4)} = 4x_1 + 4x_2x_3 - 8x_1x_2x_3$$

$$8z_3^{(5,6)} = 8a_1b_1a_0b_0$$

$$4z_2^{(5,6)} = 4a_1b_1 + 4a_1a_0b_1b_0 - 8a_1a_0b_1b_0$$


$$F_{spec} = 8z_3 + 4z_2 + 2z_1 + z_0$$

$$F_{spec}^{(1,2)} = 4x_1 + 4x_5 + 2z_1 + z_0$$

$$F_{spec}^{(3,4)} = \dots$$




Still Linear !!

 


Backward Rewriting - Analysis

 - Example: 4-bit CSA-multiplier
 - Compare size of intermediate expressions
 - Individual bits vs. an entire expression ($Sig_{out} \rightarrow \dots \rightarrow Sig_{in}$)



Backward Rewriting - Summary

 
- ❑ No residual expression !
 - But the cut expression can explode (*fat belly issue*)
 - Choice and ordering of cuts during rewriting affects performance
- ❑ Issues:
 - Minimize the “fat belly”, the size of largest expression (memory)
 - Handling complex gates
 - Provide cuts in AOI gate



Backward Rewriting - Results


□ Performance for original & lightly synthesized designs

 - Synthesis performed by ABC “resyn”
- Verified designs
 - Multipliers, matrix multiplier, A^*B+C , squarer, etc.
 - Up-to 5 million gates
 - 256+ bit-widths
- ~Linear CPU time
- Memory : quadratic in # gates



Functional Abstraction – Spectral Method

 - Extract arithmetic functions with unknown boundaries
 - Assume that PO boundary is known but no boundary for PIs
 - Backward rewriting
- Spectral method
 - Examine distribution of weights (coefficients) of polynomial terms during rewriting
 - Determine arithmetic function corresponding to a sub-expression
 - based on its coefficients



Arithmetic Spectrum – Adder

□ n -bit adder

i = bit position of result
 $C(i) = 2^i$, coefficient a bit i
 $N(i) = \# \text{ terms with coeff } C(i)$


$$A = a_0 + 2a_1 + 4a_2$$

$$B = b_0 + 2b_1 + 4b_2$$

$$A + B = a_0 + 2a_1 + 4a_2 + b_0 + 2b_1 + 4b_2$$

$$N(i) = 2, i \in (0, 1, 2, \dots, n-1)$$

$+$	$i=3$	$i=2$	$i=1$	$i=0$
	2	2	2	2
	8	4	2	1

 

Arithmetic Spectrum – Linear Functions




- *n-bit word shifting*

$$N(i) = 1, i \in (0, 1, 2, \dots, n-2)$$

- *Multiplexer*


$$Z_{MUX} = W - 2s \cdot W$$
   
$$N_1(i) = 2, N_2(i) = 1, i \in (0, 1, 2, \dots, n-1)$$





Spectrum – Multiplier (*nonlinear*)


□ Multiplier

 
  
$$N_i = \begin{cases} i + 1 & \text{if } i \leq n/2 - 1 \\ n - i - 1 & \text{if } i \geq n/2 \end{cases}$$




Abstraction – Spectral Method

 

Other Arithmetic Spectra

 - Does the circuit structure affect the spectrum?
 - No, it affects rewriting performance, but *not* the spectrum
- Example: 3-bit *Booth multiplier* vs. CSA multiplier
 - Diagram: single-, double-, triple-variable terms (left to right)



$$F_{spec} = z_0 + 2z_1 + 4z_2 + 8z_3 + 16z_4 + 32z_5$$



Expression with 1-variable terms

Spectrum – Booth and CSA Multiplier



- 3-bit Mults

Rewriting progress

20 %

  

40 %

 
 


Spectrum – Booth and CSA Multiplier



□ 3-bit Mults

Rewriting progress

80 %

  

100 %

 
 


Non-linear
word
detected !

Spectrum – 3-operand Multiplier

□ Spectrum for *arbitrary* arithmetic function ?

  - 3-operand multiplier A^*B^*C
- *Addition, multiplication or combination*
 - Multiply-Accumulator (MAC)



$$\dots + 4x_1x_5 + 2x_1x_3 + x_3x_7 + 2x_5x_7 + \dots \\ = \dots + (2x_1 + x_7)(2x_5 + x_3) + \dots$$


□ Word abstraction from expression

- Pairing signals
- Need topological analysis

Arithmetic Spectrum - MAC



- Multiply Accumulator ($F = A * B + C$)
 - Can we identify the adder and the multiplier ?
 - Adder or multiplier may not exist after synthesis
 - We can tell that there is an *addition* and a *multiplication*
 - Identify the upper boundary of function F
 - What we cannot do: identify the adder or multiplier
 - Structural level
- Example : *MAC*
 - 2-bit multiplier following 4-bit adder

Initial step

 


Arithmetic Spectrum - MAC


□ MAC

  

Linear word!

 


Addition and multiplication detected

 

Functional Abstraction - Results

 - 8- to 128-bit MAC
- Limitations
 - Need to know *output bits*
 - Computing *spectrum* is expensive



size k	#.gates	pre-ordering	Addition	Multiplication	Total
8	529	0.01 s	0.01 s	0.22 s	0.24 s
16	2089	0.01 s	0.03 s	2.71 s	2.75 s
32	8281	0.03 s	0.11 s	50.7 s	51.00 s
64	32953	0.07 s	0.47 s	1028.9 s	1029 s
80	51432	0.12 s	0.76 s	3049.5 s	3050 s
96	74008	0.15 s	1.27 s	2.0 hrs	2.0 hrs
112	100681	0.21 s	1.62 s	3.7 hrs	3.7 hrs
128	131465	0.27 s	2.23 s	6.6 hrs	6.6 hrs

TABLE I. WORD-ABSTRACTION EVALUATION USING
MULTIPLY-ACCUMULATOR S = SECONDS, HRS = HOURS

Thank You !