## Logic Synthesis via Boolean Relations

Valentina Ciriani University of Milano

A. Bernasconi, V. Ciriani, G. Trucco, T. Villa, Using Flexibility in P-Circuits by Boolean Relations, IEEE Transanctions on Computers 64(12), 2015.



- Boolean relations
- Example: logic synthesis with critical signals
   Problem definition
- P-circuits
- Synthesis of P-circuits with Boolean relations
- Experimental results

## Incompletely specified Multioutput **Boolean function**

Incompletely specified *n*-input, *m*-output **Boolean function:** 

 $F: \{0,1\}^n \to \{0,1,-\}^m$ 

01

10

Example F(00) = 00,F(10) = -0 (i.e., F(10) = $\{00, 10\}$ F(01) = 01, F(11) = 1- (i.e., F(11) = {{0,11}) 00 00 00 00 01 01 01 01 01 10 10 10 10 10 11 **Incompletely specified** Some covering functions **Multioutput Boolean** 

EPFL Workshop on Logic Synthesis & Verification. December 10-11, 2015

function

## **Boolean Relations**

- Boolean relations are a generalization of incompletely specified logic functions
- A Boolean relation R: {0,1}<sup>n</sup> → {0,1}<sup>m</sup> is a one-to-many multi-output Boolean mapping
- Example
- $\begin{array}{ll} \mathsf{R}(00) = \{00\} & \mathsf{R}(10) = \{00, 11\} \\ \mathsf{R}(01) = \{00, 01, 10\} & \mathsf{R}(11) = \{10, 11\} = 1- \end{array}$







**Boolean relation** 

Covering functions (compatible functions)

## **Boolean Relations**

The set of multi-output functions compatible with a Boolean relation R is defined as

 $F(R) = \{ f \mid f \subseteq R \text{ and } f \text{ is a function} \}.$ 

◆ The solution of a Boolean relation R is a multioutput Boolean function f ∈ F(R)

The function f is an optimal solution of R according to a given cost function c, if

 $\forall f' \in F(R), c(f) \leq c(f')$ 

## **Example of Synthesis via Boolean Relations**

#### Scenario:

 Logic synthesis in presence of critical signals that should be moved toward the output

Application fields:

 for decreasing power consumption:
 \$signals with high switching activity
 for decreasing circuit delay:
 \$signals with high delay



Restructure (or synthesize) a circuit in order to move critical signals near to the output (decreasing the cone of influence):

- minimizing the circuit area
- keeping the number of levels bounded
  performing an efficient minimization

## Simple solution: Shannon

Shannon decomposition
x is the critical signal

$$f = x f_{x=1} + \overline{x} f_{x=0}$$

f<sub>x=0</sub> and f<sub>x=1</sub> do not depend on x
x is near to the output



## **Problem of Shannon approach**



# The idea

- try not to split the cubes
- Iet the critical signal x near to the output
- idea:

the crossing cubes that do not depend on x are not projected

Problem: how to identify the points that may form crossing cubes that do not depend on x?

They are in the intersection:  $I = f_{x=0} \cap f_{x\neq 0}$ 









#### **Decomposition with intersection**



 $\bigcirc$ 

 $\left( \right)$ 





# **P-representation of a completely specified Boolean function f**

$$\bullet \text{Let} \qquad I = f_{x=0} \cap f_{x \neq 0}$$

#### A P-representation P(f) (or P-circuit) is:

 $P(f \neq x f^{\neq} + \overline{x} f^{=} + f^{I}$ 

where

$$f_{x=0} \setminus I \subseteq f^{=} \subseteq f_{x=0}$$
$$f_{x\neq0} \setminus I \subseteq f^{\neq} \subseteq f_{x\neq0}$$
$$\emptyset \subseteq f^{I} \subseteq I$$
$$P(f) = f$$

#### Minimization of P-circuits using Boolean Relation

- P-circuit minimization:
  - find the sets f<sup>=</sup>, f<sup>≠</sup>, f<sup>⊥</sup> leading to a P-circuit of minimal cost
- Formalized and solved using Boolean relations

We define a relation R such that

 the set of all the compatible functions of R corresponds exactly to the set of all possible Pcircuits for f

an optimal solution of R is an optimal P-circuit for f

### Minimization of P-circuits using Boolean Relation

Input set for R<sub>f</sub>: all the variables but the critical signal x<sub>i</sub>

Output set for R<sub>f</sub>: triple of functions f<sup>=</sup>, f<sup>≠</sup>, f<sup>I</sup> defining a P-circuit for f

x <sub>1</sub> x <sub>i-1</sub> x <sub>i+1</sub> x <sub>n</sub>	R <sub>f</sub> (f <sup>=</sup> , f <sup>≠</sup> , f <sup>+</sup> )
Points in f <sub>xi=0</sub> \ I	100
Points in f <sub>xi≠0</sub> ∖ I	010
Points in I	{1, 11-} = {001, 011, 101, 111, 110}
All other points	000

#### Minimization of P-circuits using Boolean Relation

Theorem:

#### P-circuit minimization for f

## minimization of the Boolean relation R<sub>f</sub>

# **Incompletely Specified Functions**



#### P-circuit of an incompletely specified Boolean function f

 $\bigstar \text{Let } \mathbf{f} = \{\mathbf{f}^{on}, \mathbf{f}^{dc}\}, \text{ with } \mathbf{f}^{on} \cap \mathbf{f}^{dc} = \emptyset;$ 

 $\diamond \text{ Define } I = (f_{x=0}^{on} \cup f_{x=0}^{dc}) \cap (f_{x\neq 0}^{on} \cup f_{x\neq 0}^{dc})$ 

A P-circuit P(f) is:

$$P(f) = x f^{\neq} + \overline{x} f^{=} + f^{I}$$

where

 $f_{x=0}^{on} \setminus I \subseteq f^{=} \subseteq f_{x=0}^{on} \cup f_{x=0}^{dc}$   $f_{x\neq0}^{on} \setminus I \subseteq f^{=} \subseteq f_{x\neq0}^{on} \cup f_{x\neq0}^{dc}$   $\emptyset \subseteq f^{I} \subseteq I$   $f^{on} \subseteq P(f) \subseteq f^{on} \cup f^{dc}$ 

# **Experimental results**

- Linux Intel Core i7, 3.40 GHz CPU, 8GB RAM
- CUDD library for OBDDs for function representation
- BREL (Bañeres, Cortadella, and Kishinevsky, 2009) for the synthesis of Boolean relations
- Multioutput benchmarks have been synthesized minimizing each single output independently from the others

# **Experimental results**

### • $\mu_L$ and $\mu_{BDD}$ :

- refer to P-circuits synthesized with cost function µ<sub>L</sub> that minimizes the number of literals
- and µ<sub>BDD</sub> that minimizes the size of the BDDs used for representing the relations
- modeling the P-circuit minimization problem using Boolean relations pays significantly:
  - P-circuit µ<sub>L</sub> and P-circuit µ<sub>BDD</sub> turned out to be more compact than the corresponding P-circuits proposed BCVT2009 in about 92% and 78% of our experiments, respectively

# **Experimental results**

	<b>P-circuit</b> $\mu_L$			<b>P-circuit</b> $\mu_{BDD}$		
Average gain	Time	Area	Delay	Time	Area	Delay
w.r.t. S-circuit	-383%	37%	29%	95%	30%	25%
w.r.t. P-circuit [4]	-4214%	33%	24%	56%	25%	20%
w.r.t. SOP	-39412%	26%	19%	-304%	18%	14%

#### TABLE II

#### Average gain of P-circuits based on Boolean relations

	<b>P-circuit</b> $\mu_L$	<b>P-circuit</b> $\mu_{BDD}$
w.r.t. S-circuit	65%	61%
w.r.t. P-circuit [4]	13%	13%
w.r.t. SOP	44%	62%

#### TABLE III

COMPARISON OF POWER DISSIPATION



 Boolean relations can be useful for modeling Boolean hard optimization problems

 Boolean relations have been successfully used in logic synthesis

#### Future work:

- investigating the use of Boolean relations in other algorithmic contexts (i.e., data mining)
- trade-off quality of results vs. scalability



## www.di.unimi.it/ciriani