# LIBRARY BINDING

© Giovanni De Micheli

Stanford University

### Outline

C GDM

- Modeling and problem analysis.
- Rule-based systems for library binding.
- Algorithms for library binding:
  - Structural covering/matching.
  - Boolean covering/matching.
- Concurrent optimization and binding.

### Library binding

- Given an unbound logic network and a set of library cells:
  - Transform into an interconnection of instances of library cells.
  - Optimize area, (under delay constraints.)
  - Optimize *delay*, (under *area* constraints.)
  - Optimize *power*, (under *delay* constraints.)
- Called also *technology mapping*:
  - Method used for re-designing circuits in different technologies.

### Library models

C GDM

- Combinational elements:
  - Single-output functions:
    - \* e.g. AND, OR, AOI.
  - Compound cells: e.g. adders, encoders.
- Sequential elements:
  - Registers, counters.
- Miscellaneous:
  - Schmitt triggers.


### Major approaches

- Rule-based systems:
  - Mimic designer activity.
  - Handle all types of cells.
- Heuristic algorithms:
  - Restricted to single-output combinational cells.
- Most tools use a combination of both.
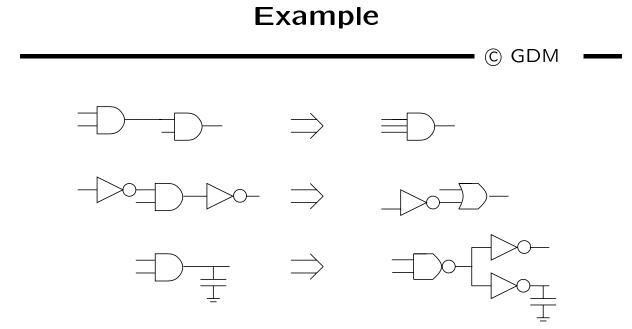
### **Rule-based library binding**

🗕 🛈 GDM

- Binding by stepwise transformations.
- Data-base:
  - Set of patterns associated with best implementation.
- Rules:
  - Select subnetwork to be mapped.
  - Handle high-fanout problems, buffering, etc.



#### **Strategies**

- © GDM

- Search for a sequence of transformations.
- Search space:
  - Breadth (options at each step).
  - Depth (look-ahead).
- *Meta-rules* determine dynamically breadth and depth.

### **Rule-based library binding**

C GDM

• Advantages:

- Applicable to all kinds of libraries.

- Disadvantages:
  - Large rule data-base:
    - \* Completeness issue.
    - \* Formal properties of bound network.
  - Data-base updates.

### Algorithms for library binding

\_\_\_\_\_ © GDM \_\_\_\_

- Mainly for single-output combinational cells.
- Fast and efficient:
  - Quality comparable to rule-based systems.
- Library description/update is simple:
  - Each cell modeled by its function or equivalent pattern.

#### **Problem analysis**


C GDM


- Matching:
  - A cell matches a sub-network
     if their terminal behavior is the same.
  - Input-variable *assignment* problem.
- Covering:
  - A cover of an unbound network
     is a partition into subnetworks
     which can be replaced by library cells.
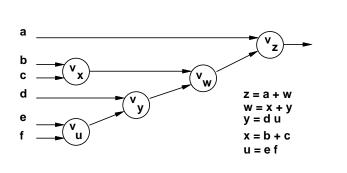
### Assumptions

- Network granularity is fine.
  - Decomposition into *base* functions.
    - \* 2-input AND, OR, NAND, NOR.
- Trivial binding:
  - Replacement of each vertex by base cell.







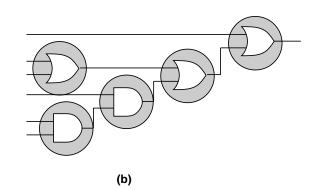

© GDM



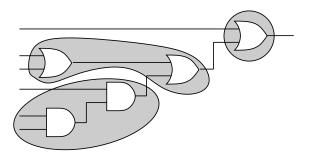

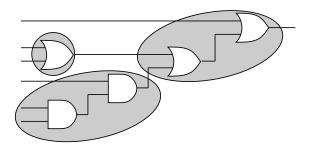


(c)

(d)

© GDM


\_

-

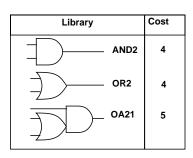







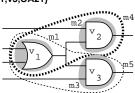




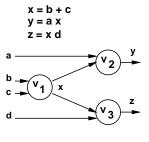

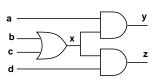


(c)

(b)

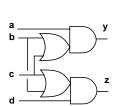



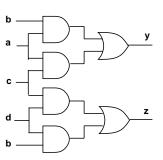

(f)

© GDM


- Vertex covering:
  - Covering  $v_1$ :  $(m_1 + m_4 + m_5)$ .
  - Covering  $v_2$ :  $(m_2 + m_4)$ .
  - Covering  $v_3$ :  $(m_3 + m_5)$ .
- Input compatibility:
  - Match  $m_2$  requires  $m_1$ :
    - \*  $(m'_2 + m_1)$ .
  - Match  $m_3$  requires  $m_1$ :
    - \*  $(m'_3 + m_1)$ .
- Overall *binate* clause:


 $- (m_1 + m_4 + m_5)(m_2 + m_4)(m_3 + m_5)(m'_2 + m_1)(m'_3 + m_1) = 1$ 

🗕 🔘 GDM


- Decomposition:
  - Cast network and library in standard form.
  - Decompose into *base functions*.
  - Example: NAND2 and INV.
- Partitioning:
  - Break network into cones.
  - Reduce to many multi-input single-output subnetworks.
- Covering:
  - Cover each subnetwork by library cells.

🗕 © GDM

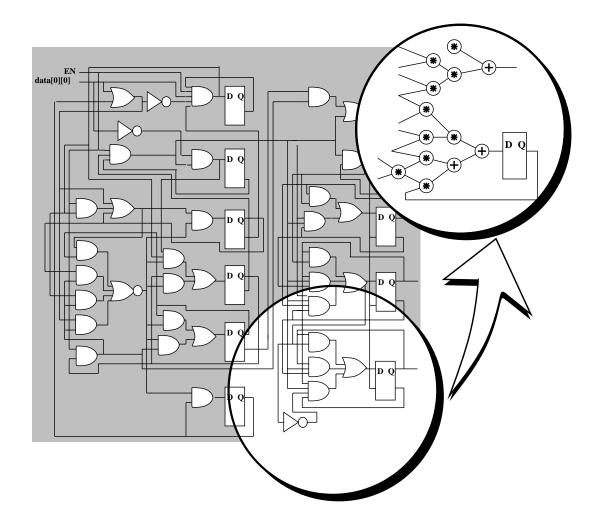

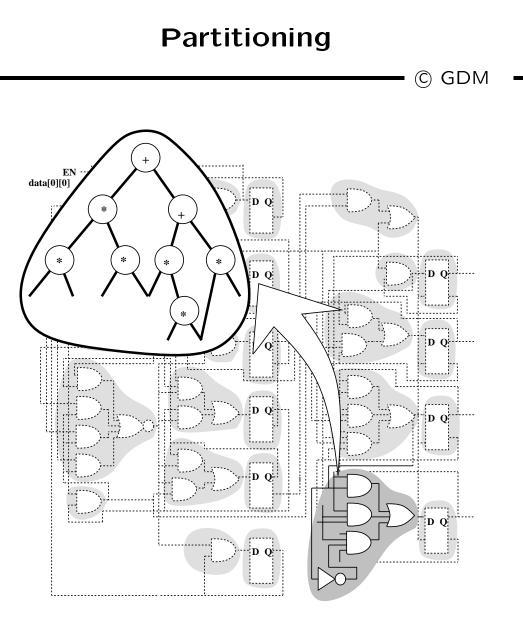



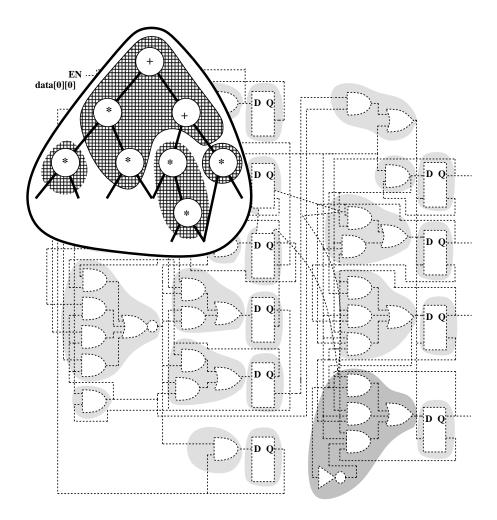


### Heuristic algorithms

- Structural approach:
  - Model functions by patterns.
    - \* Example: trees, dags.
  - Rely on *pattern matching* techniques.
- Boolean approach:
  - Use Boolean models.
  - Solve tautology problem.
  - More powerful.

## Example Boolean versus structural matching

© GDM

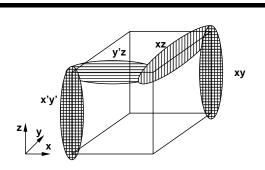

• f = xy + x'y' + y'z

• 
$$g = xy + x'y' + xz$$


• Function equality is a tautology:

- Boolean match.

• Patterns may be different:

- Structural match may not be found.
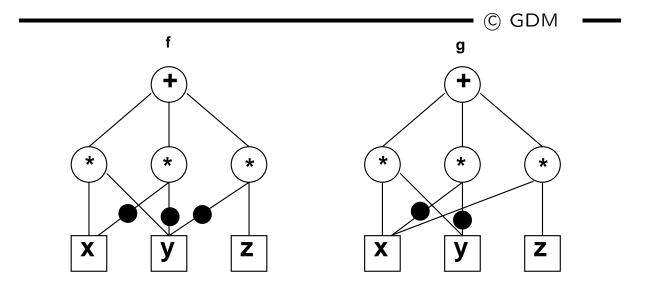
### Example Boolean versus structural matching



- f = xy + x'y' + y'z
- g = xy + x'y' + xz
- Patterns do not match.


### Structural matching and covering

– © GDM

• Expression patterns:

- Represented by dags.

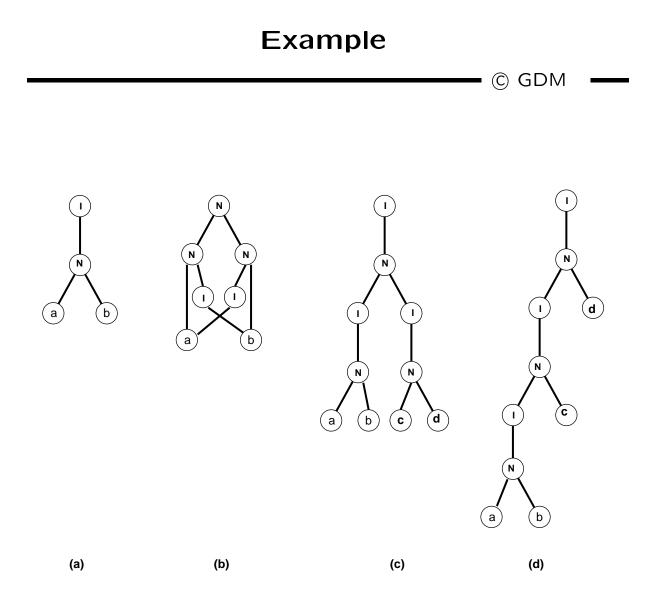
- Identify pattern dags in network:
  - Sub-graph isomorphism.
- Simplification:
  - Use tree patterns.


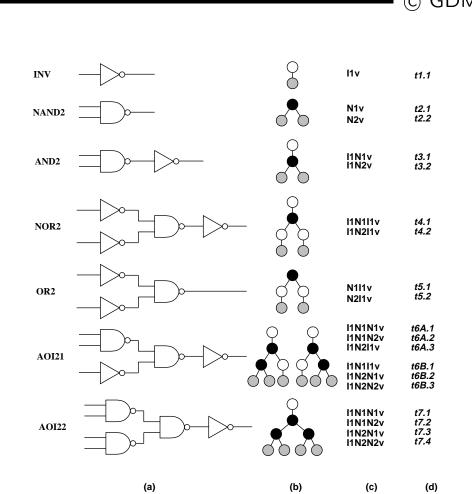
#### **Tree-based matching**

C GDM


- Network:
  - Partitioned and decomposed:
    - \* NOR2 (or NAND2) + INV.
    - \* Generic base functions.
  - Subject tree.
- Library:
  - Represented by trees.
  - Possibly more than one tree per cell.
- Pattern recognition:
  - Simple binary tree match.
  - Aho-Corasick automaton.




### Simple library
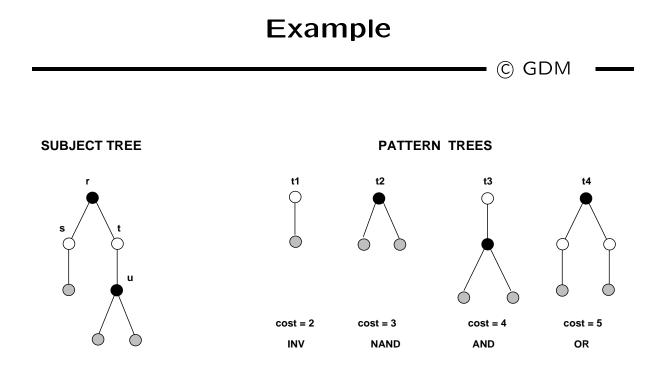
### Tree covering

- Dynamic programming:
  - Visit subject tree bottom-up.
- At each vertex:
  - Attempt to match:
    - \* Locally rooted subtree.
    - \* All library cells.
- Optimum solution, for the subtree.



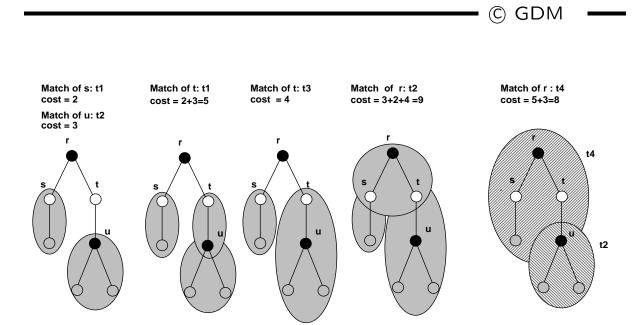

\_\_\_\_\_ © GDM \_\_\_\_

- Minimum-area cover.
- Area costs:
  - INV:2; NAND2:3; AND2:4; AOI21:6.
- Best choice:
  - AOI21 fed by a NAND2 gate.

- © GDM

Network	Subject graph	Vertex	Match	Gate	Cost
<b>0</b>		x	t2	NAND2(b,c)	3
		У	t1	INV(a)	2
		z	t2	NAND2(x,d)	2* 3 = 6
		W	t2	NAND2(y,z)	3 * 3 + 2 = 11
		0	t1	INV(w)	3 * 3 + 2 * 2 = 13
a x d	v N <sup>1</sup> 2		t3	AND2(y,z)	2 * 3 + 4 + 2 = 12
			t6B	AOI21(x,d,a)	3 + 6 = 9
b c	v d				

### Minimum delay cover

- Dynamic programming approach.
- Cost related to gate delay.
- Delay modeling:
  - Constant gate delay.
    - \* Straightforward.
  - Load-dependent delay:
    - \* Load fanout unknown.
    - \* Binning techniques.

### Minimum delay cover constant delays

© GDM

• The cell pattern tree and the rooted subtree are isomorphic.

- The vertex is labeled with the cell delay.

- The cell tree is isomorphic to a subtree with leaves *L*.
  - The vertex is labeled with the cell cost plus the maximum of the labels of L.

© GDM

- Inputs data-ready times are 0 except for  $t_d = 6$ .
- Constant delays:

- INV:2; NAND2:4; AND2:5; AOI21:10.

• Compute *data-ready* times bottom-up:

 $-t_x = 4, t_y = 2; t_z = 10t_w = 14.$ 

• Best choice:

- AND2, two NAND2 and an INV gate.

- © GDM

Network	Subject graph	Vertex	Match	Gate	Cost
• ×		х	t2	NAND2(b,c)	4
w y z a x d	$ \begin{array}{c}     1 \\     1 \\     1 \\     1 \\     2 \\     1 \\     V \\     N \\     V \\     N \\     1 \\     2 \\     1 \\     2 \\     1 \\     2 \\     1 \\     2 \\     2 \\     1 \\     2 $	у	t1	INV(a)	2
		Z	t2	NAND2(x,d)	6 + 4 = 10
		W	t2	NAND2(y,z)	10 + 4 = 14
		0	t1	INV(w)	14 + 2 = 16
			t3	AND2(y,z)	10 + 5 = 15
	$ \begin{array}{c c} & & & & & v \\ 0 & 1 & 2 & 6 \end{array} $		t6B	AOI21(x,d,a)	10 + 6 = 16
b c	v d dv				
	0 0				

### Minimum delay cover load-dependent delays

- Model:
  - Assume a finite set of load values.
- Dynamic programming approach:
  - Compute an array of solutions for each possible load.
  - For each input to a matching cell the best match for any load is selected.
- Optimum solution, when all possible loads are considered.

- Inputs data-ready times are 0 except for  $t_d = 6$ .
- Load-dependent delays:
  - INV:1+I; NAND2:3+I; AND2:4+I; AOI21:9+I.
- Loads:
  - INV:1; NAND2:1; AND2:1; AOI21:1.
- Same solution as before.

- Inputs data-ready times are 0 except for  $t_d = 6$ .
- Load-dependent delays:
  - INV:1+I; NAND2:3+I; AND2:4+I; AOI21:9+I; SINV:1+0.5I;.
- Loads:
  - INV:1; NAND2:1; AND2:1; AOI21:1; SINV:2.
- Assume output load is 1:
  - Same solution as before.
- Assume output load is 5:
  - Solution uses SINV cell.

C GDM

-

					Cost		
Network	Subject graph	Vertex	Match	Gate	Load=1	Load=2	Load=5
v v z a x d	$ \begin{array}{c}                                     $	х	t2	NAND2(b,c)	4	5	8
		у	t1	INV(a)	2	3	6
		Z	t2	NAND2(x,d)	10	11	14
		W	t2	NAND2(y,z)	14	15	18
		0	t1	INV(w)			20
			t3	AND2(y,z)			19
			t6B	AOI21(x,d,a)			20
b c	v d dv			SINV(w)			18.5
	0 0						

# Library binding and polarity assignment


– © GDM

- Search for lower cost solution by not constraining the signal polarities.
- Most circuit allow us to choose the input/output signal polarities.
- Approaches:
  - Structural covering.
  - Boolean covering.
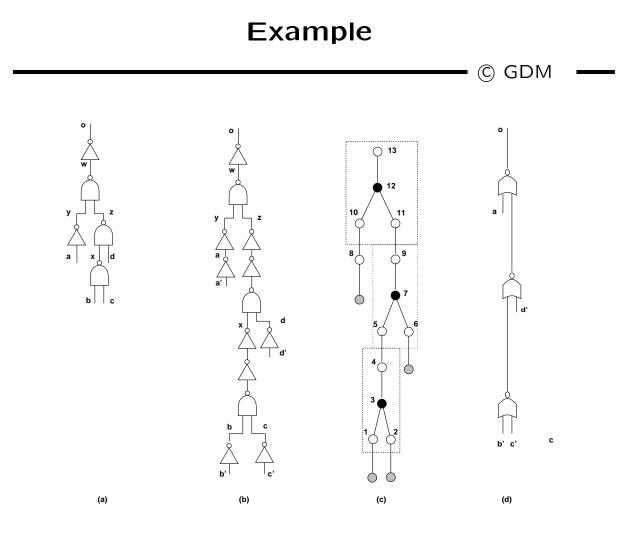
## Structural covering and polarity assignment

🗕 🔘 GDM

- Pre-process subject network:
  - Add inverter pairs between NANDs.
  - Provide signals with both polarity.
- Add inverter-pair cell to the library:
  - To eliminate unneeded pairs.
  - Cell corresponds to a connection with zero cost.




### **Boolean covering**

© GDM

- Decompose network into base functions.
- When considering vertex  $v_i$ :
  - Construct *clusters* by local elimination.
  - Several functions associated with  $v_i$ .
- Limit size and depth of clusters.

© GDM

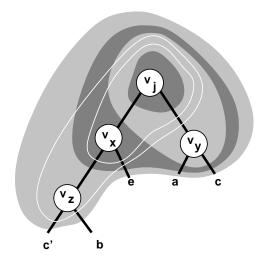

$$f_{j,1} = xy;$$
  

$$f_{j,2} = x(a+c);$$
  

$$f_{j,3} = (e+z)y;$$
  

$$f_{j,4} = (e+z)(a+c);$$
  

$$f_{j,5} = (e+c'+d)y;$$
  

$$f_{j,6} = (e+c'+d)(a+c);$$

\_\_\_\_ © GDM \_\_\_\_

- Cluster function  $f(\mathbf{x})$ : sub-network behavior.
- Pattern function  $g(\mathbf{y})$ : cell behavior.
- *P*-equivalence:
  - Exists a permutation operator  $\mathcal{P}$ , such that  $f(\mathbf{x}) = g(\mathcal{P} \mathbf{x})$  is a tautology?
- Approaches:
  - Tautology check over all input permutations.
  - Multi-rooted pattern ROBDD capturing all permutations.

## Input/output polarity assignment

© GDM

- Allow for reassignment of input/output polarity.
- $\mathcal{NPN}$  classification of Boolean functions.
- $\mathcal{NPN}$ -equivalence:
  - Exists a permutation matrix  $\mathcal{P}$ , and complementation operators  $\mathcal{N}_i, \mathcal{N}_o$ such that  $f(\mathbf{x}) = \mathcal{N}_o \ g(\mathcal{P} \ \mathcal{N}_i \ \mathbf{x})$ is a tautology?
- Variations:

-  $\mathcal{N}$ -equivalence,  $\mathcal{PN}$ -equivalence

#### **Boolean matching**

\_\_\_\_\_ © GDM \_\_\_\_

- *Pin assignment* problem.
  - Map cluster variables x to pattern vars y.
  - Characteristic equation:  $A(\mathbf{x}, \mathbf{y}) = 1$ .
- Pattern function under variable assignment:

$$-g_{\mathcal{A}}(\mathbf{x}) = \mathcal{S}_{\mathbf{y}}\mathcal{A}(\mathbf{x}, \mathbf{y}) g(\mathbf{y})$$

• Tautology problem.

 $-f(\mathbf{x}) \oplus g_{\mathcal{A}}(\mathbf{x})$ 

 $- \forall_{\mathbf{X}}(f(\mathbf{x}) \oplus \mathcal{S}_{\mathbf{y}} (\mathcal{A}(\mathbf{x}, \mathbf{y}) g(\mathbf{y})))$ 

\_\_\_\_\_ © GDM \_\_\_\_

- Assign  $x_1$  to  $y'_2$  and  $x_2$  to  $y_1$ .
- Characteristic equation:

 $-A(x_1, x_2, y_1, y_2) = (x_1 \oplus y_2)(x_2 \oplus y_1)$ 

• AND pattern function:

 $-g = y_1 y_2$ 

• Pattern function under assignment:

$$- \mathcal{S}_{y_1,y_2}\mathcal{A}g = \\= \mathcal{S}_{y_1,y_2}(x_1 \oplus y_2)(x_2 \overline{\oplus} y_1)y_1y_2 = x_2x_1'$$

- Capture some properties of Boolean functions.
- If signatures do not match, there is no match.
- Used as filters to reduce computation.
- Signatures:
  - Unateness.
  - Symmetries.
  - Co-factor sizes.
  - Spectra.

# Filters based on unateness and symmetries

- Any pin assignment must associate
  - unate (binate) variables in  $f(\mathbf{x})$ with unate (binate) variables in  $g(\mathbf{y})$ .
- Variables or groups of variables
  - that are interchangeable in  $f(\mathbf{x})$ must be interchangeable in  $g(\mathbf{y})$ .

C GDM

• Cluster function: f = abc.


- Symmetries:  $\{(a, b, c)\}$  - unate.

• Pattern functions:

-  $g_1 = a + b + c$ \* Symmetries: {(a, b, c)} - unate. -  $g_2 = ab + c$ \* Symmetries: {(a, b)(c)} - unate. -  $g_3 = abc' + a'b'c$ \* Symmetries: {(a, b, c)} - binate.
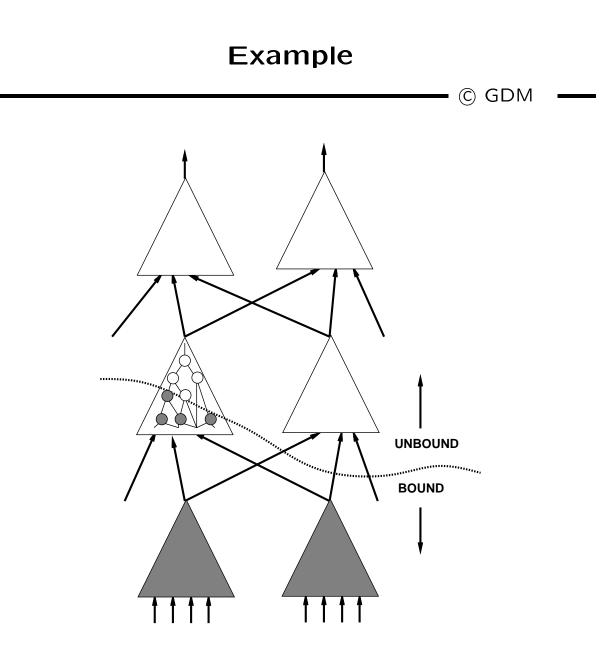
# Concurrent optimization and library binding

- Motivation:
  - Logic simplification is usually done prior to binding.
  - Logic simplification/substitution can be combined with binding.
- Mechanism:
  - Binding induces some *don't care* conditions.
  - Exploit *don't cares* as degrees of freedom in matching.




# Boolean matching with *don't care* conditions


— © GDM


- Given  $f(\mathbf{x}), f_{DC}(\mathbf{x})$  and  $g(\mathbf{y})$ :
  - g matches f if g is equivalent to  $\widetilde{f}$  where  $f \cdot f'_{DC} \leq \widetilde{f} \leq f + f_{DC}$
- Matching condition:

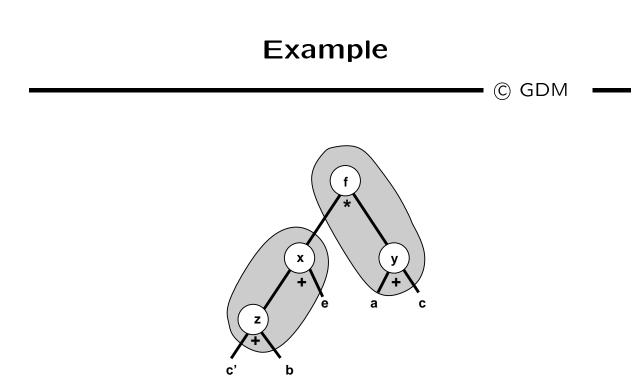 $- \forall_{\mathbf{X}} (f_{DC}(\mathbf{x}) + f(\mathbf{x}) \oplus \mathcal{S}_{\mathbf{y}} (\mathcal{A}(\mathbf{x}, \mathbf{y}) g(\mathbf{y})))$ 



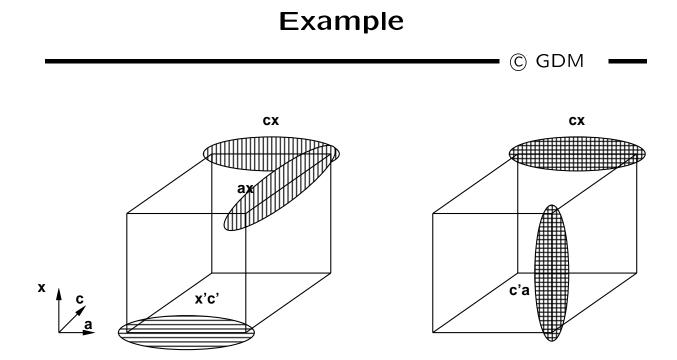- Assume  $v_x$  is bound to OR3(c', b, e).
- Don't care set includes  $x \oplus (c' + b + e)$ .
- Consider  $f_j = x(a+c)$  with CDC = x'c'.
- No simplification. Mapping into AOI gate.
- Matching with DC. Mapping into MUX gate.



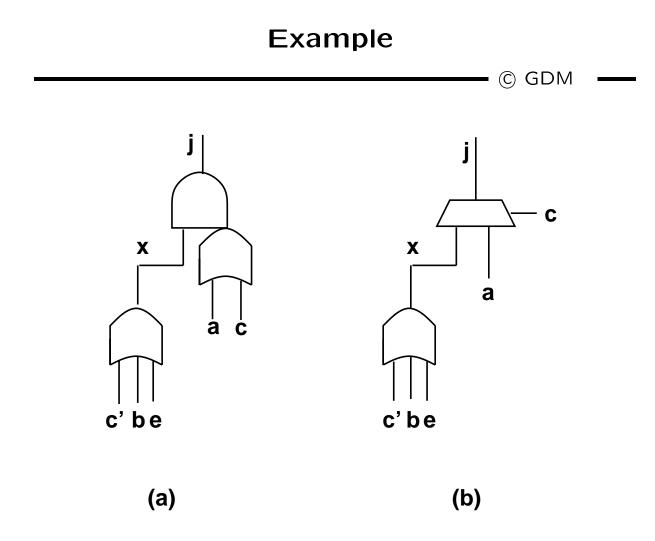

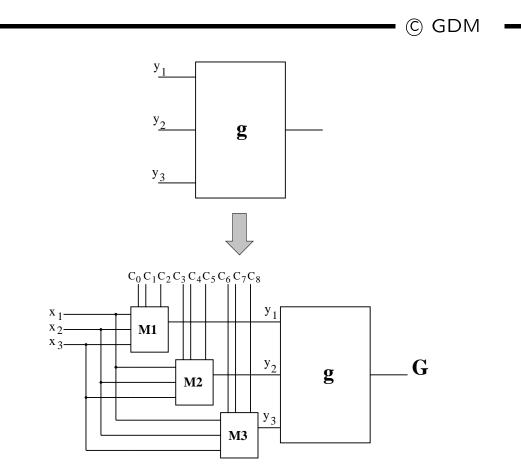
## Extended matching

© GDM

- Augment pattern function with mux function.
  - Each cell input can be routed to any cluster input (or voltage rail).
  - Input polarity can be changed.
  - Cell and cluster may differ input size.
- Define composite function  $G(\mathbf{x}, \mathbf{c})$ :
  - Pin assignment is determining **c**.
- Matching formula:  $M(\mathbf{c}) = \forall_{\mathbf{X}} [G(\mathbf{x}, \mathbf{c}) \oplus f(\mathbf{x})]$






- $g = y_1 + y_2 y'_3$
- $y_1(\mathbf{c}, \mathbf{x}) = (c_0 c_1 x_1 + c_0 c'_1 x_2 + c'_0 c_1 x_3) \oplus c_2$
- $G = y_1(\mathbf{c}, \mathbf{x}) + y_2(\mathbf{c}, \mathbf{x}) \ y_3(\mathbf{c}, \mathbf{x})'$
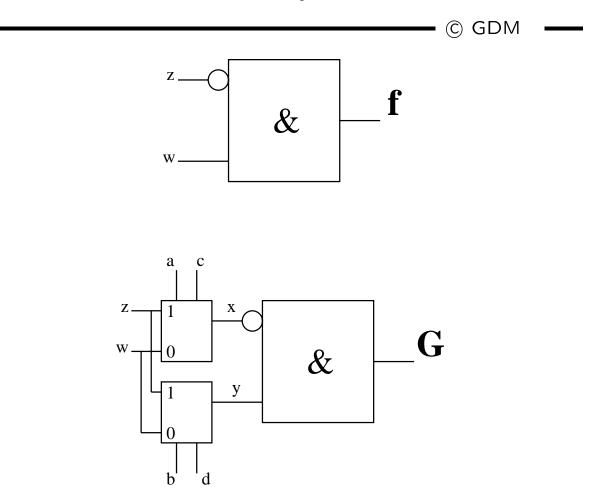
## Extended matching modeling

© GDM

- Model composite functions by ROBDDs.
  - Assume: n-input cluster and m-input cell.
  - For each cell input:
    - \*  $\lceil log_2 n \rceil$  variables for pin permutation.
    - \* One variable for input polarity.
  - Total size of **c**:  $m(\lceil \log_2 n \rceil + 1)$ .
- A match exists if there is at least one value of **c** satisfying  $M(\mathbf{c}) = \forall_{\mathbf{X}} [G(\mathbf{x}, \mathbf{c}) \oplus f(\mathbf{x})].$



- g = x'y, f = wz'
- $G(a, b, c, d, w, z) = (c \oplus (za + wa'))'(d \oplus (zb + wb'))$
- $f \overline{\oplus} G = (wz') \overline{\oplus} ((c \oplus (za + wa'))'(d \oplus (zb + wb')))$
- M(a, b, c, d) = ab'c'd' + a'bcd

----- © GDM -

- Captures implicitly all possible matches.
- No extra burden when exploiting *don't care* sets.

$$- M(\mathbf{c}) = \forall_{\mathbf{X}} \left[ G(\mathbf{x}, \mathbf{c}) \ \overline{\oplus} \ f(\mathbf{x}) + f_{DC}(\mathbf{x}) \right]$$

- Efficient BDD-based representation.
- Extensions to support multiple-output matching

#### Summary

\_\_\_\_ © GDM

- Library binding is very important.
- Rule-based approach:

- General, sometimes inefficient.

- Algorithmic approach:
  - Pattern-based: fast, but limited.
  - Boolean: more general and efficient.