



Ambipolar Logic Circuit Design and Synthesis

I. O'Connor, K. Jabeur, S. Le Beux, D. Navarro

*Lyon Institute of Nanotechnology
Ecole Centrale de Lyon, France*

ian.oconnor@ec-lyon.fr



Ambipolar nanofabrics

- At nanoscale, only regular fabrics are viable for systematic variability (e.g. OPC) and for self-assembly
- Still random variability – need device-level tuning and system-level reconfigurability
- Multi-gate devices can offer this level of flexibility
- Ambipolar double gate devices in regular nanofabrics could offer a means to solve many problems at the same time
- This work: based on CNT fabric
- Techniques also applicable to SiNW, GNR ...

Nanograin architecture

- Layer of aligned semiconducting CNTs
- CMOS-type interconnect layers
- Fine-grain reconfigurable cells
- Fixed intra-matrix interconnect
- Reconfigurable inter-matrix interconnect



leti


inl

ims




Device and model data

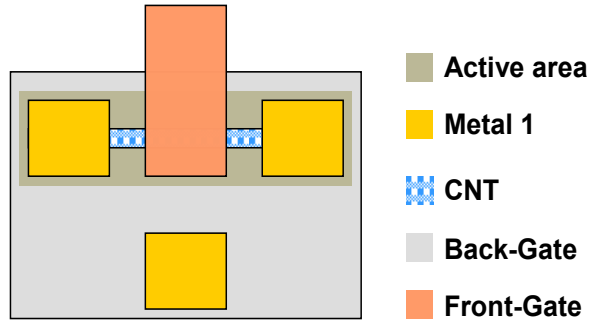M. H. Ben Jamaa et al, ECS Transactions, 34 (1) 1005-1010 (2011)




DG-CNTFET: top view

Parameters	DG CNFET	PTM 16nm LP
Drain access channel length	50nm	0
Source access channel length	50nm	0
Inner channel	20nm	16nm
Width	50nm	56nm(n-type)/80nm(p-type)
Chirality (n,m)	(11, 0)	-
Nb of nanotubes	12	-
Diameter of 1 nanotube	0.86nm	-
Supply voltage	0.9 V	0.9 V

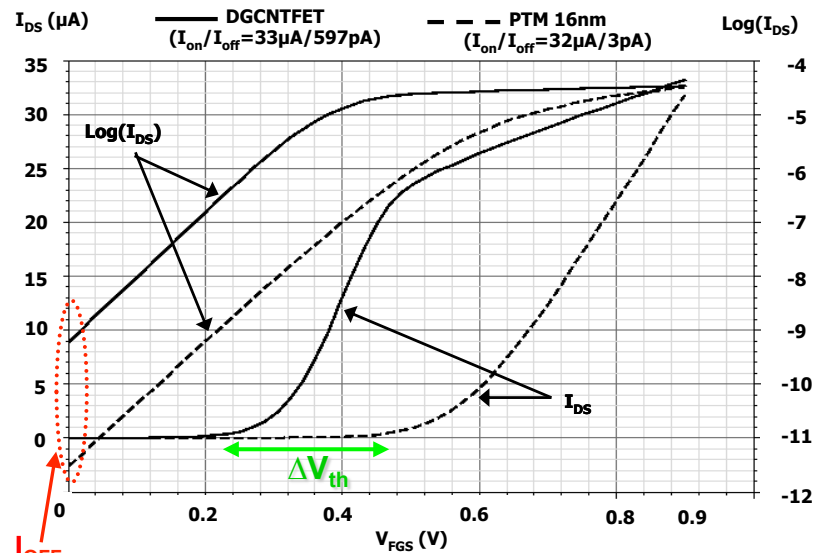

 I_{DS}/V_{FGS} characteristics of the n-branch
($V_{BG}-V_S = +V = +0.9V$)




I_{DS}/V_{FGS} characteristics of the p-branch
($V_{BG}-V_S = -V = -0.9V$)

Agenda


- Compact ambipolar logic
 - TTS structure primitive
 - Double-Gate static logic: principle and evaluation
 - Double-Gate dynamic logic: principle and evaluation
- Reconfigurable logic gates
 - Am-ICDGFET transmission gate primitive
 - x-function logic cell synthesis methodology
 - Performance comparison
- Conclusion

Compact ambipolar logic

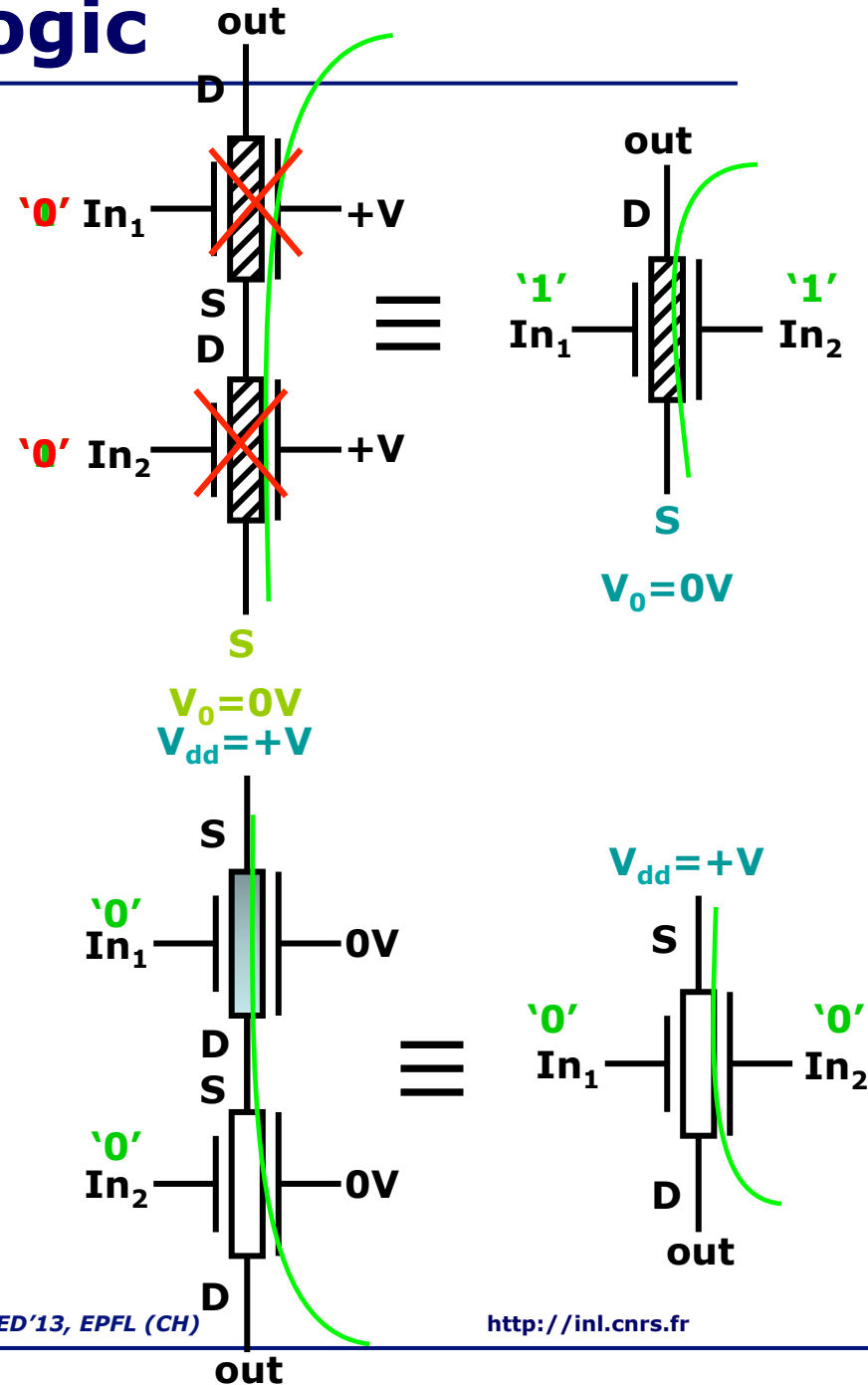- Basic idea: use Am-ICDGFET device to replace two transistors in series (TTS) structures
- critical for path resistance and gate capacitance optimization, with consequent impact on delay, power and area





Static Logic structures

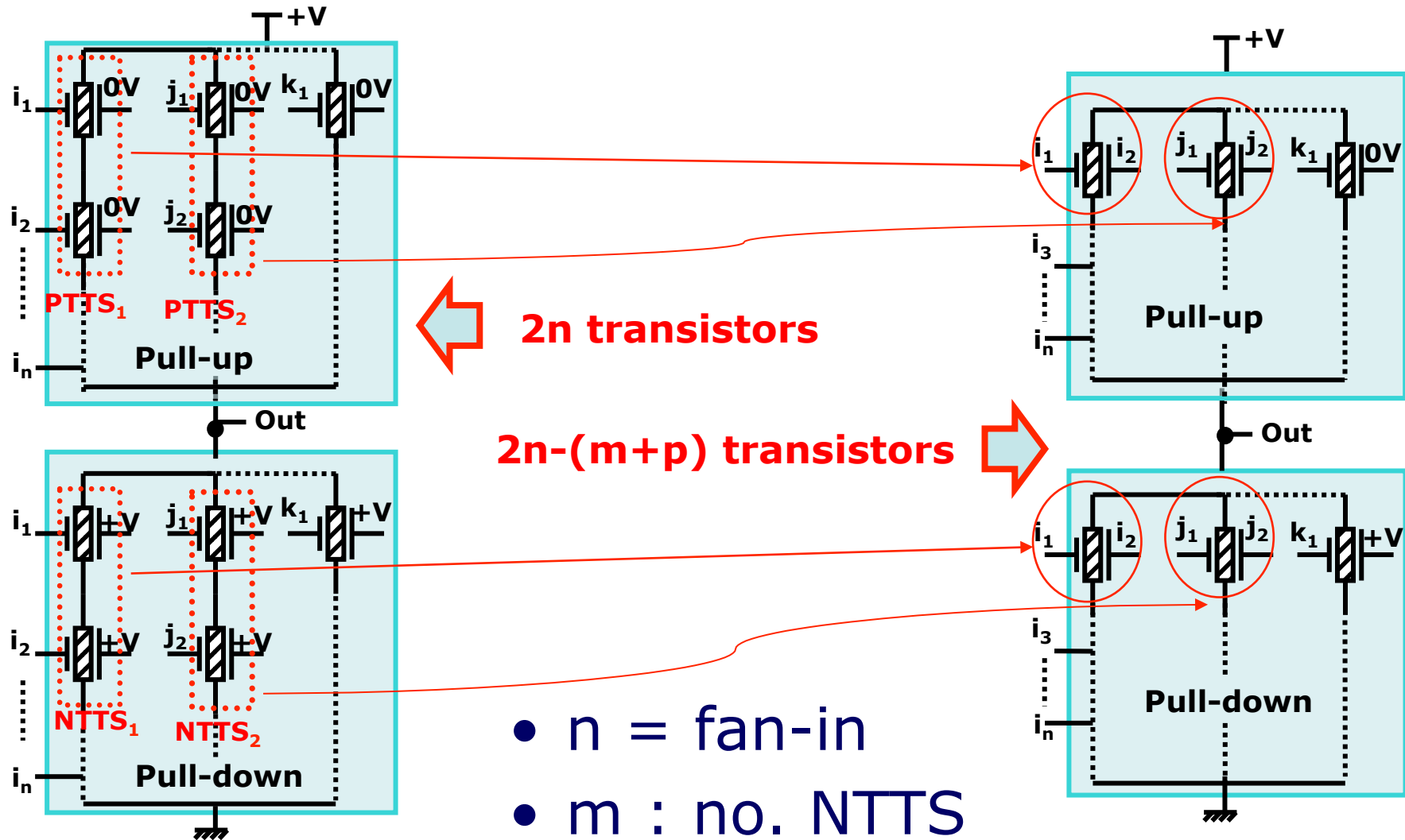


- $n = \text{fan-in}$
- m : no. NTTS
- P : no. PTTS

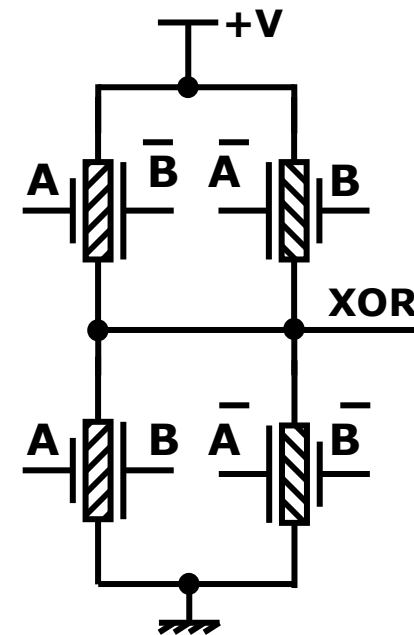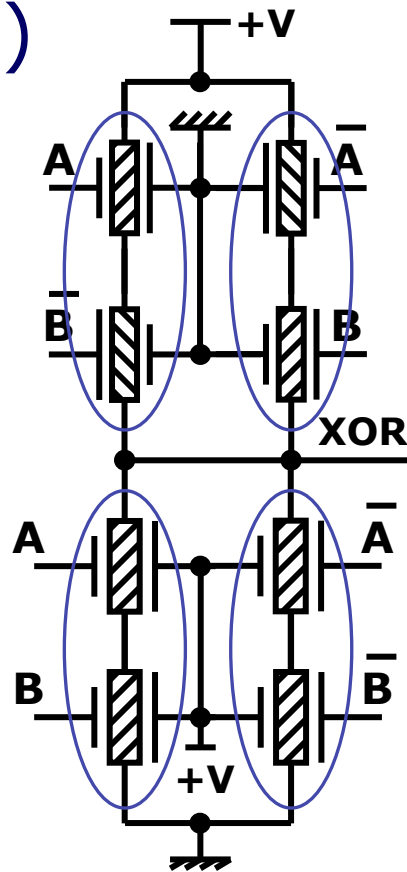Example: XOR


- Applicable to any complementary static logic gate containing TTS structures
- efficient with complex gates (XOR/XNOR, MUXs...)







Example: 2:1 and 4:1 MUX

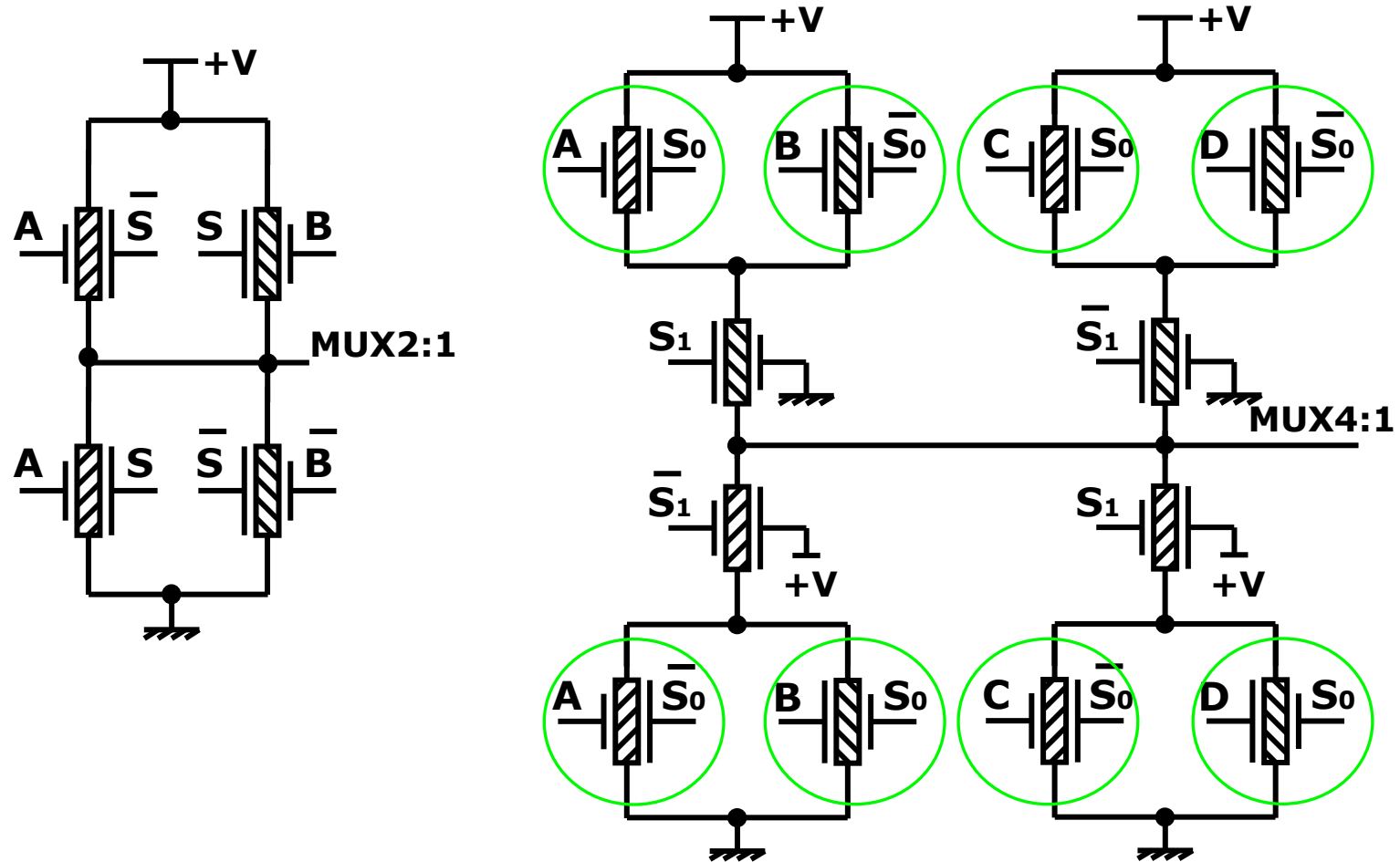



Dynamic Logic structures: 3 approaches

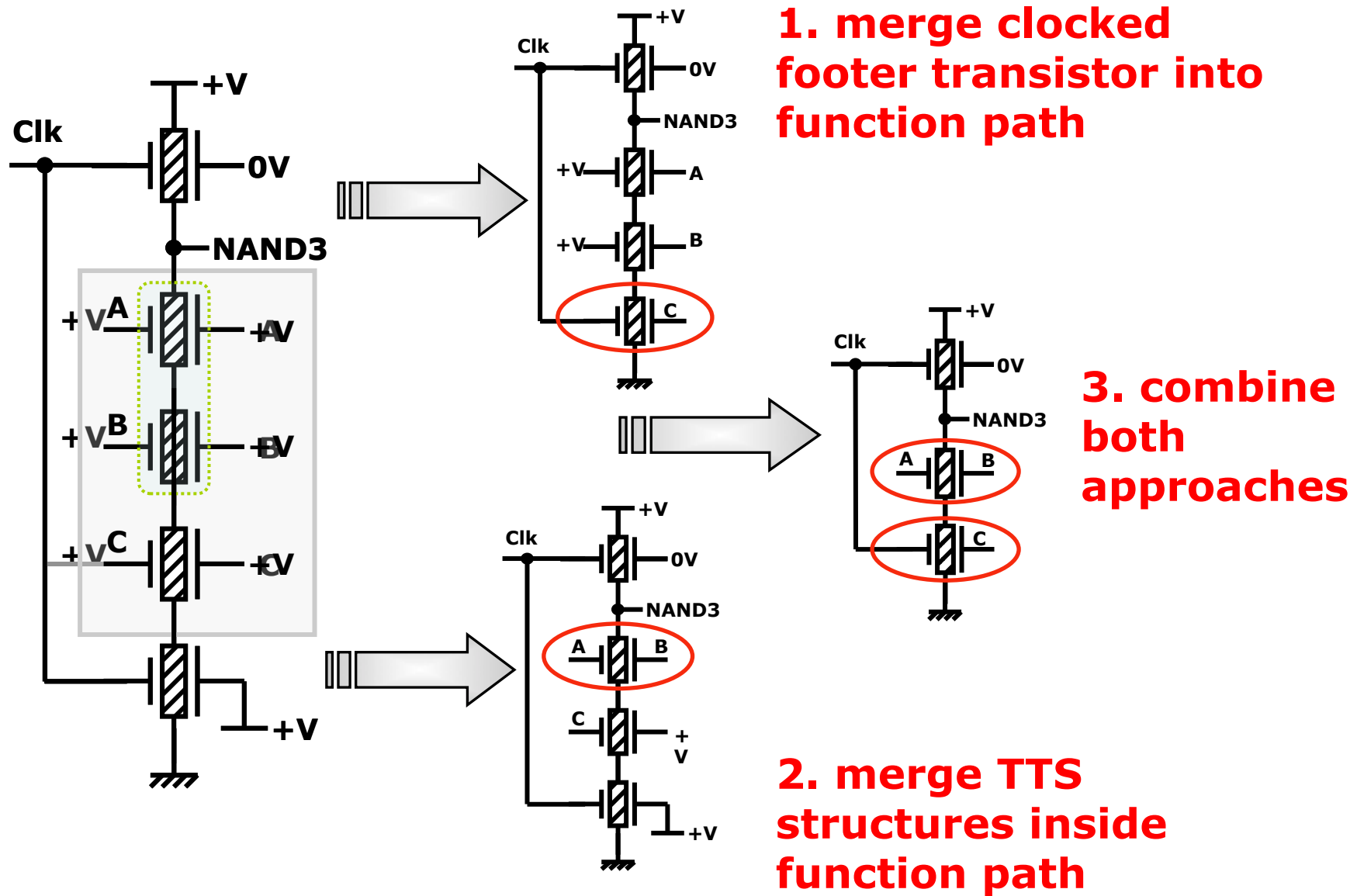

Examples

    

1.
n+1 transistors

  


2.
n+2-m transistors

$\neg ((A \wedge C) \wedge D) \vee B$
3.
n+1-m transistors

$\neg ((A \wedge B) \vee (C \wedge D)) \wedge E$

Performance Comparison

 

$f_{\text{clk}} = 1\text{GHz}$
 $t_r = t_f = 20\text{ps}$
 $C_L = C_{\text{inv}4}$



SiSL: 16nm conventional static logic
 CSL: CNT conventional static logic
 DGSL: CNT DG static logic

Figures averaged over:
 XOR
 XNOR
 2:1 MUX
 4:1 MUX
<http://inl.cnrs.fr>

  
- **1.7X power consumption**
- **0.4X time delay**
- **0.7X PDP**
- **0.5X area**

Reconfigurable logic gates

- Basic idea: configure switching properties of logic networks with back gate voltages
- Requires transmission gates to propagate logic levels with no degradation and for a wide range of data and control voltage combinations
- Also requires gate synthesis methodology for tunable functionality



Reconfigurable logic cell CNT-DR7T

 

- boolean data inputs A and B (logic level at $V_{ss}=0V$ and $V_{dd}=1V$) + circuit output Y
- four-phase non-overlapping clock signals
 - two pre-charge inputs PC_1, PC_2
 - two evaluation inputs EV_1, EV_2
- control inputs $V_{bgA}, V_{bgB}, V_{bgC}$ to configure circuit to 1 of 14 functions (back-gate bias -1V / p-type and +1V / n-type)

V_{bgA}	V_{bgB}	V_{bgC}	Y
+V	+V	+V	$\overline{A+B}$
+V	+V	-V	A+B
+V	-V	+V	$\overline{A.B}$
+V	-V	-V	$\overline{A+B}$
-V	+V	+V	$\overline{A.B}$
-V	+V	-V	$\overline{A+B}$
-V	-V	+V	A.B
-V	-V	-V	$\overline{A.B}$
+V	0	+V	\overline{A}
+V	0	-V	A
0	+V	+V	\overline{B}
0	+V	-V	B
0	0	0	1
0	0	-V	0


I. O'Connor et al., IEEE TCAS, 2007

Am-BDD design technique

1. Define output functions
2. Map their BDDs in a common Am-BDD
3. Label every edge connecting two different nodes
4. Trace the configuration table and identify correlations
5. Pass-transistor logic circuit implementation


$$F_1 = \neg(A+B+C)$$

$$F_2 = \neg(A.B.C)$$

 

F	a	b	c	d	e	f
$F_1 = \neg(A+B+C)$	0V	0V	V/2	V/2	+V	+V
$F_2 = \neg(A.B.C)$	+V	+V	0V	0V	V/2	V/2

X Y Z

 

16-function (complete operator set)

 
 



TABLE II. 16-FUNCTIONS CONFIGURATION TABLE

a	b	c	d	e	f	g	h	i	j	k	l	F
0	0	0	-V	0	0	+V	0	-V	0	0	+V	$\overline{A+B}$
0	+V	0	0	-V	0	0	0	0	-V	+V	0	$A+B$
0	-V	0	0	+V	0	0	0	0	-V	+V	0	$\overline{A+B}$
0	0	0	+V	0	0	-V	0	-V	0	0	+V	$A \bullet \overline{B}$
0	+V	0	-V	0	0	0	0	-V	0	0	+V	$A+B$
0	0	0	0	-V	0	+V	0	0	-V	+V	0	$B \bullet \overline{A}$
-V	0	0	0	0	0	0	0	0	0	0	0	T
0	0	0	0	0	0	0	+V	0	0	0	0	\perp
0	0	0	0	+V	0	-V	0	0	-V	+V	0	$A \bullet B$
0	-V	0	+V	0	0	0	0	-V	0	0	+V	$\overline{A \bullet B}$
0	+V	0	0	0	0	-V	0	0	0	0	0	A
0	-V	0	0	0	0	+V	0	0	0	0	0	\overline{A}
0	0	+V	0	0	0	0	0	-V	0	0	+V	\overline{B}
0	0	0	0	0	+V	0	0	0	-V	+V	0	B
0	0	0	-V	+V	0	0	0	-V	-V	+V	+V	$\overline{A \oplus B}$
0	0	0	+V	-V	0	0	0	-V	-V	+V	+V	$A \oplus B$

12 configuration signals!

12-function

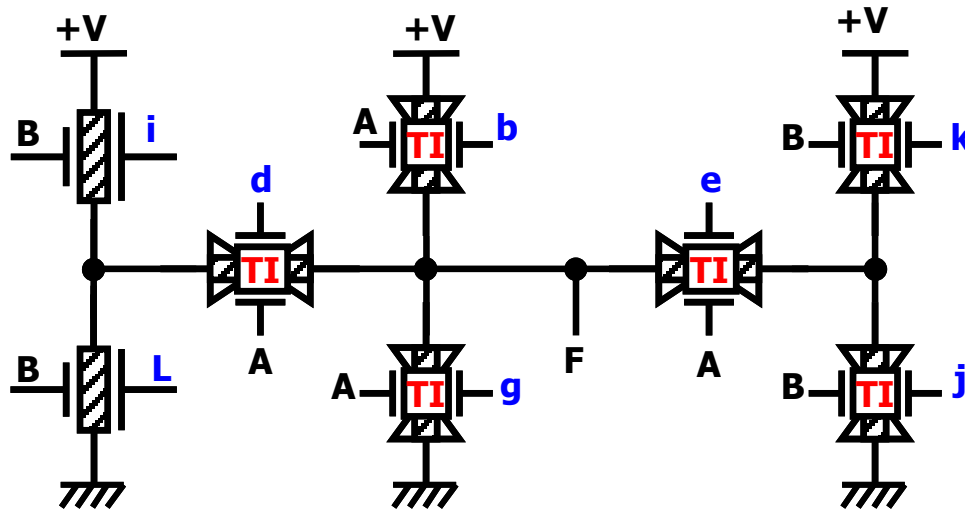
- Tune the functionality
- Remove T, ⊥, B, !B



b	d	e	g	i	j	k	l	F
V/2	0V	V/2	+V	0V	V/2	V/2	+V	$\overline{A+B}$
+V	V/2	0V	V/2	V/2	0V	+V	V/2	$A+B$
0V	V/2	+V	V/2	V/2	0V	+V	V/2	$\overline{A+B}$
V/2	+V	V/2	0V	0V	V/2	V/2	+V	$A \cdot \overline{B}$
+V	0V	V/2	V/2	0V	V/2	V/2	+V	$A + \overline{B}$
V/2	V/2	0V	+V	V/2	0V	+V	V/2	$B \cdot \overline{A}$
V/2	V/2	+V	0V	V/2	0V	+V	V/2	$A \cdot B$
0V	+V	V/2	V/2	0V	V/2	V/2	+V	$\overline{A \cdot B}$
+V	V/2	V/2	0V	V/2	V/2	V/2	V/2	A
0V	V/2	V/2	+V	V/2	V/2	V/2	V/2	\overline{A}
V/2	0V	+V	V/2	0V	0V	+V	+V	$\overline{A \oplus B}$
V/2	+V	0V	V/2	0V	0V	+V	+V	$A \oplus B$


6-function

- Strip down to NAND, NOR, INV, BUF

 


b	d	g	i	l	F
V/2	0V	+V	0V	+V	$\overline{A+B}$
V/2	+V	0V	0V	+V	$A \bullet \overline{B}$
+V	0V	V/2	0V	+V	$A + \overline{B}$
0V	+V	V/2	0V	+V	$\overline{A \bullet B}$
+V	V/2	0V	V/2	V/2	A
0V	V/2	+V	V/2	V/2	\overline{A}

Performance comparison

 

• 16F-AmBDD vs 2-LUT:

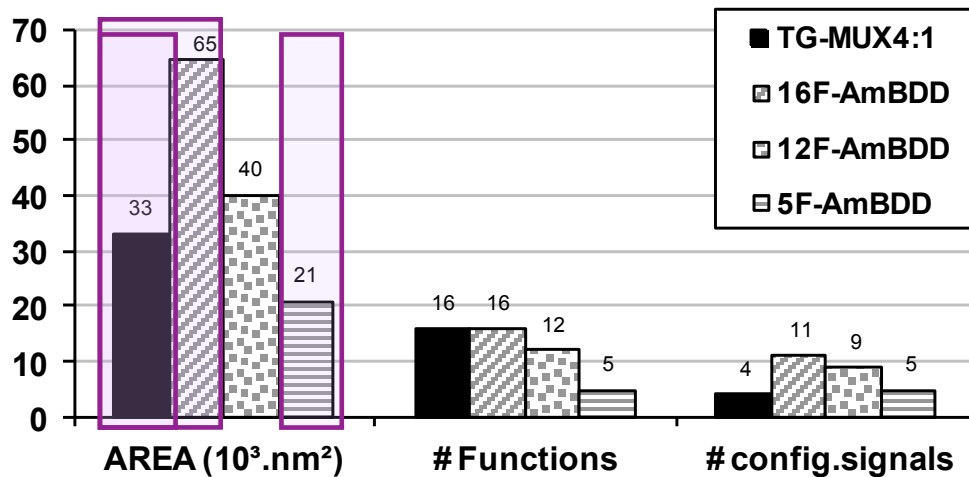- 1X functionality
- 1.6X PDP
- 2X area
- 2.8X config



• 6F-AmBDD vs 2-LUT:

- 0.4X functionality
- 0.3X PDP
- 0.6X area
- 1.3x config

Conclusion and perspectives

- Compact logic gates:
 - Merge TTS structures in function path (+footer) using back gate
 - Fewer transistors : $2n-(m+p)$ or $n+2-m$
 - Improved time delay : low V_{TH} , low branch resistance
 - Increased power consumption : low V_{TH}
- Reconfigurable logic gates
 - Am-BDD logic synthesis method
 - Full 16F functionality has worse PDP and area
 - Better results achieved for basic 6F cell
- Towards synthesis flows for reduced functionality cells and static interconnect