

The fascinating properties of majority

Mathias Soeken

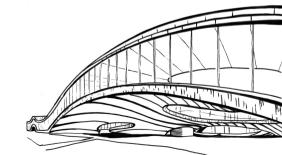Integrated Systems Laboratory, EPFL, Switzerland



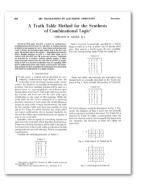




[S.B. Akers Jr., IRE Trans. EC-10 (1961), 604-615]




Before leaving this section on synthesis, several comments seem appropriate. The reader's first reaction to the foregoing may well be that the one thing which the general area of switching circuit theory does *not* need is *another* method for synthesizing combinational logic. However, this method does offer several features which may make it more desirable in certain applications:

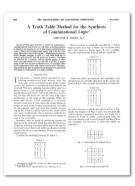[S.B. Akers Jr., IRE Trans. EC-10 (1961), 604-615]






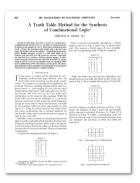[C. Schensted, Letter to Martin Gardner, Dec 9, 1978]






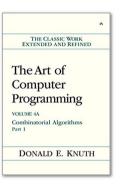


[D.E. Knuth, The Art of Computer Programming 4A (2011)]



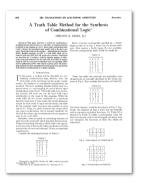[D.E. Knuth, The Art of Computer Programming 4A (2011)]





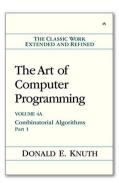



[L.G. Amarù, P.-E. Gaillardon, and G. De Micheli, DAC 51 (2014), 194:1-194:6]

 $\langle x_1x_2x_3\rangle$

$$\langle x_1x_2x_3\rangle=(x_1\vee x_2)(x_1\vee x_3)(x_2\vee x_3)$$

$$\langle x_1 x_2 x_3 \rangle = (x_1 \lor x_2)(x_1 \lor x_3)(x_2 \lor x_3)$$

= $x_1 x_2 \lor x_1 x_3 \lor x_2 x_3$

$$\langle x_1 x_2 x_3 \rangle = (x_1 \vee x_2)(x_1 \vee x_3)(x_2 \vee x_3) \qquad \langle x_1 \dots x_n \rangle = [x_1 + \dots + x_n > \frac{n}{2}]$$

$$= x_1 x_2 \vee x_1 x_3 \vee x_2 x_3$$

$$\langle x_1 x_2 x_3 \rangle = (x_1 \vee x_2)(x_1 \vee x_3)(x_2 \vee x_3) \qquad \langle x_1 \dots x_n \rangle = [x_1 + \dots + x_n > \frac{n}{2}]$$

$$= x_1 x_2 \vee x_1 x_3 \vee x_2 x_3$$

Majority rule

$$\langle x_1 x_1 x_2 \rangle = x_1$$

$$\langle x_1\bar{x}_1x_2\rangle=x_2$$

$$\langle x_1 x_2 x_3 \rangle = (x_1 \vee x_2)(x_1 \vee x_3)(x_2 \vee x_3) \qquad \langle x_1 \dots x_n \rangle = [x_1 + \dots + x_n > \frac{n}{2}]$$

$$= x_1 x_2 \vee x_1 x_3 \vee x_2 x_3$$

Majority rule

$$\begin{split} \langle x_1 x_1 x_2 \rangle &= x_1 \\ \langle x_1 \overline{x}_1 x_2 \rangle &= x_2 \end{split} \qquad \begin{aligned} \langle x_1 \ldots x_1 x_2 \ldots x_{\lceil \frac{n}{2} \rceil} \rangle &= x_1 \\ \langle x_1 \overline{x}_1 x_2 \ldots x_{n-1} \rangle &= \langle x_2 \ldots x_{n-1} \rangle \end{aligned}$$

$$\langle x_1 x_2 x_3 \rangle = (x_1 \vee x_2)(x_1 \vee x_3)(x_2 \vee x_3) \qquad \langle x_1 \dots x_n \rangle = [x_1 + \dots + x_n > \frac{n}{2}]$$

$$= x_1 x_2 \vee x_1 x_3 \vee x_2 x_3$$

Majority rule

$$\langle x_1 x_1 x_2 \rangle = x_1$$

$$\langle x_1 x_1 x_2 \dots x_{\lceil \frac{n}{2} \rceil} \rangle = x_1$$

$$\langle x_1 \overline{x}_1 x_2 \rangle = x_2$$

$$\langle x_1 \overline{x}_1 x_2 \dots x_{n-1} \rangle = \langle x_2 \dots x_{n-1} \rangle$$

Containment of AND and OR

$$\langle x_1 0 x_2 \rangle = x_1 \wedge x_2$$
$$\langle x_1 1 x_2 \rangle = x_1 \vee x_2$$

$$\langle x_1 x_2 x_3 \rangle = (x_1 \vee x_2)(x_1 \vee x_3)(x_2 \vee x_3) \qquad \langle x_1 \dots x_n \rangle = [x_1 + \dots + x_n > \frac{n}{2}]$$

$$= x_1 x_2 \vee x_1 x_3 \vee x_2 x_3$$

Majority rule

$$\begin{aligned} \langle x_1 x_1 x_2 \rangle &= x_1 \\ \langle x_1 \bar{x}_1 x_2 \rangle &= x_2 \end{aligned} \qquad \begin{aligned} \langle x_1 \ldots x_1 x_2 \ldots x_{\lceil \frac{n}{2} \rceil} \rangle &= x_1 \\ \langle x_1 \bar{x}_1 x_2 \ldots x_{n-1} \rangle &= \langle x_2 \ldots x_{n-1} \rangle \end{aligned}$$

Containment of AND and OR

$$\begin{aligned} \langle x_1 0 x_2 \rangle &= x_1 \wedge x_2 \\ \langle x_1 1 x_2 \rangle &= x_1 \vee x_2 \end{aligned} \qquad \begin{aligned} \langle x_1 \dots x_{\lceil \frac{n}{2} \rceil} 0 \dots 0 \rangle &= x_1 \wedge \dots \wedge x_{\lceil \frac{n}{2} \rceil} \\ \langle x_1 \dots x_{\lceil \frac{n}{2} \rceil} 1 \dots 1 \rangle &= x_1 \vee \dots \vee x_{\lceil \frac{n}{2} \rceil} \end{aligned}$$

Commutativity rule

$$\langle xyz\rangle = \langle yzx\rangle = \langle zxy\rangle$$

Commutativity rule

$$\langle xyz \rangle = \langle yzx \rangle = \langle zxy \rangle$$

Associativity rule

$$\langle x \mathbf{u} \langle y \mathbf{u} z \rangle \rangle = \langle \langle x \mathbf{u} y \rangle \mathbf{u} z \rangle$$

Mnemonic: $(x \circ (y \circ z)) = ((x \circ y) \circ z)$

Commutativity rule

$$\langle xyz \rangle = \langle yzx \rangle = \langle zxy \rangle$$

Associativity rule

$$\langle x \mathbf{u} \langle y \mathbf{u} z \rangle \rangle = \langle \langle x \mathbf{u} y \rangle \mathbf{u} z \rangle$$

Mnemonic: $(x \circ (y \circ z)) = ((x \circ y) \circ z)$

Distributivity rule

$$\langle xu\langle yvz\rangle\rangle = \langle \langle xuy\rangle v\langle xuz\rangle\rangle$$

Mnemonic: $(x \circ (y \times z)) = ((x \circ y) \times (x \circ z))$

Commutativity rule

$$\langle xyz\rangle = \langle yzx\rangle = \langle zxy\rangle$$

Associativity rule

$$\langle x \mathbf{u} \langle y \mathbf{u} z \rangle \rangle = \langle \langle x \mathbf{u} y \rangle \mathbf{u} z \rangle$$

Mnemonic: $(x \circ (y \circ z)) = ((x \circ y) \circ z)$

Distributivity rule

$$\langle xu\langle yvz\rangle \rangle = \langle \langle xuy\rangle v\langle xuz\rangle \rangle$$

Mnemonic: $(x \circ (y \times z)) = ((x \circ y) \times (x \circ z))$

Inverter propagation rule

$$\langle \bar{x}\bar{y}\bar{z}\rangle = \overline{\langle xyz\rangle}$$

▶ NC¹ contains families of Boolean circuits with logarithmic depth, and a polynomial number of 2-input gates, and inverters

- ▶ NC¹ contains families of Boolean circuits with logarithmic depth, and a polynomial number of 2-input gates, and inverters
- ► AC⁰ contains families of Boolean circuits with constant depth, a polynomial number of AND and OR gates with unbounded fan-in, and inverters

- ▶ NC¹ contains families of Boolean circuits with logarithmic depth, and a polynomial number of 2-input gates, and inverters
- ► AC⁰ contains families of Boolean circuits with constant depth, a polynomial number of AND and OR gates with unbounded fan-in, and inverters
- ► TC⁰ contains families of Boolean circuits with constant depth, a polynomial number of MAJ gates with unbounded fan-in, and inverters

- ▶ NC¹ contains families of Boolean circuits with logarithmic depth, and a polynomial number of 2-input gates, and inverters
- ► AC⁰ contains families of Boolean circuits with constant depth, a polynomial number of AND and OR gates with unbounded fan-in, and inverters
- ► TC⁰ contains families of Boolean circuits with constant depth, a polynomial number of MAJ gates with unbounded fan-in, and inverters
- ▶ Relationship: $AC^0 \subsetneq TC^0 \subseteq NC^1$

- ▶ NC¹ contains families of Boolean circuits with logarithmic depth, and a polynomial number of 2-input gates, and inverters
- ► AC⁰ contains families of Boolean circuits with constant depth, a polynomial number of AND and OR gates with unbounded fan-in, and inverters
- ► TC⁰ contains families of Boolean circuits with constant depth, a polynomial number of MAJ gates with unbounded fan-in, and inverters
- ▶ Relationship: $AC^0 \subsetneq TC^0 \subseteq NC^1$
- ► Examples: integer division and integer multiplication are in TC⁰, but not in AC⁰

One "fascinating" property of AND and OR

One "fascinating" property of AND and OR

$$x_1 \wedge x_2 \wedge \cdots \wedge x_{n-1} \wedge x_n = (x_1 \wedge (x_2 \wedge (\cdots (x_{n-1} \wedge x_n) \cdots)))$$

$$x_1 \vee x_2 \vee \cdots \vee x_{n-1} \vee x_n = (x_1 \vee (x_2 \vee (\cdots (x_{n-1} \vee x_n) \cdots)))$$

One "fascinating" property of AND and OR

$$x_1 \wedge x_2 \wedge \dots \wedge x_{n-1} \wedge x_n = (x_1 \wedge (x_2 \wedge (\dots (x_{n-1} \wedge x_n) \dots)))$$

$$x_1 \vee x_2 \vee \dots \vee x_{n-1} \vee x_n = (x_1 \vee (x_2 \vee (\dots (x_{n-1} \vee x_n) \dots)))$$

Not so easy with majority

One "fascinating" property of AND and OR

$$x_1 \wedge x_2 \wedge \cdots \wedge x_{n-1} \wedge x_n = (x_1 \wedge (x_2 \wedge (\cdots (x_{n-1} \wedge x_n) \cdots)))$$

$$x_1 \vee x_2 \vee \cdots \vee x_{n-1} \vee x_n = (x_1 \vee (x_2 \vee (\cdots (x_{n-1} \vee x_n) \cdots)))$$

Not so easy with majority

$$\langle x_1 x_2 x_3 x_4 x_5 \rangle = \langle x_1 \langle x_2 x_3 x_4 \rangle \langle x_5 x_4 \langle x_3 x_2 x_1 \rangle \rangle \rangle$$

One "fascinating" property of AND and OR

$$x_1 \wedge x_2 \wedge \cdots \wedge x_{n-1} \wedge x_n = (x_1 \wedge (x_2 \wedge (\cdots (x_{n-1} \wedge x_n) \cdots)))$$

$$x_1 \vee x_2 \vee \cdots \vee x_{n-1} \vee x_n = (x_1 \vee (x_2 \vee (\cdots (x_{n-1} \vee x_n) \cdots)))$$

Not so easy with majority

$$\begin{split} \langle x_1 x_2 x_3 x_4 x_5 \rangle &= \langle x_1 \langle x_2 x_3 x_4 \rangle \langle x_5 x_4 \langle x_3 x_2 x_1 \rangle \rangle \rangle \\ \langle x_1 x_2 x_3 x_4 x_5 x_6 x_7 \rangle &= \langle x_7 \langle x_3 \langle x_4 x_5 x_6 \rangle \langle x_1 x_2 \langle x_4 x_5 x_6 \rangle \rangle \rangle \langle x_6 \langle x_1 x_2 x_3 \rangle \langle x_4 x_5 \langle x_1 x_2 x_3 \rangle \rangle \rangle \end{split}$$

One "fascinating" property of AND and OR

$$x_1 \wedge x_2 \wedge \cdots \wedge x_{n-1} \wedge x_n = (x_1 \wedge (x_2 \wedge (\cdots (x_{n-1} \wedge x_n) \cdots)))$$

$$x_1 \vee x_2 \vee \cdots \vee x_{n-1} \vee x_n = (x_1 \vee (x_2 \vee (\cdots (x_{n-1} \vee x_n) \cdots)))$$

Not so easy with majority

$$\begin{split} \langle x_1 x_2 x_3 x_4 x_5 \rangle &= \langle x_1 \langle x_2 x_3 x_4 \rangle \langle x_5 x_4 \langle x_3 x_2 x_1 \rangle \rangle \rangle \\ \langle x_1 x_2 x_3 x_4 x_5 x_6 x_7 \rangle &= \langle x_7 \langle x_3 \langle x_4 x_5 x_6 \rangle \langle x_1 x_2 \langle x_4 x_5 x_6 \rangle \rangle \rangle \langle x_6 \langle x_1 x_2 x_3 \rangle \langle x_4 x_5 \langle x_1 x_2 x_3 \rangle \rangle \rangle \end{split}$$

Open problem: What are the optimum majority-3 networks to realize majority-n?

Montone functions

A Boolean function $f(x_1, ..., x_n)$ is monotone if $f_{\bar{x}_i} \to f_{x_i}$ for $1 \leqslant i \leqslant n$.

Montone functions

A Boolean function $f(x_1, ..., x_n)$ is monotone if $f_{\bar{x}_i} \to f_{x_i}$ for $1 \leqslant i \leqslant n$.

Schensted decomposition

If $f(x_1, x_2, x_3, ..., x_n)$ is monotone, then

$$f(x_1, x_2, x_3, ..., x_n) = \langle f(x_1, x_1, x_3, ..., x_n) f(x_1, x_2, x_2, ..., x_n) f(x_3, x_2, x_3, ..., x_n) \rangle$$

► Since majority-n is monotone, we can use Schensted decomposition to map majority-n into majority-3

Montone functions

A Boolean function $f(x_1,\ldots,x_n)$ is monotone if $f_{\bar{x}_i}\to f_{x_i}$ for $1\leqslant i\leqslant n$.

Schensted decomposition

If $f(x_1, x_2, x_3, ..., x_n)$ is monotone, then

$$f(x_1, x_2, x_3, ..., x_n) = \langle f(x_1, x_1, x_3, ..., x_n) f(x_1, x_2, x_2, ..., x_n) f(x_3, x_2, x_3, ..., x_n) \rangle$$

- ► Since majority-n is monotone, we can use Schensted decomposition to map majority-n into majority-3
- ightharpoonup Inner subfunctions remain monotone ightarrow recursive application

Montone functions

A Boolean function $f(x_1, ..., x_n)$ is monotone if $f_{\bar{x}_i} \to f_{x_i}$ for $1 \leqslant i \leqslant n$.

Schensted decomposition

If $f(x_1, x_2, x_3, ..., x_n)$ is monotone, then

$$f(x_1, x_2, x_3, ..., x_n) = \langle f(x_1, x_1, x_3, ..., x_n) f(x_1, x_2, x_2, ..., x_n) f(x_3, x_2, x_3, ..., x_n) \rangle$$

- ▶ Since majority-n is monotone, we can use Schensted decomposition to map majority-n into majority-3
- ightharpoonup Inner subfunctions remain monotone ightarrow recursive application
- But: Upper bound is exponential!

Majority-n from sorter networks

▶ Idee: Sort all input bits and pick the middle one from the sorted list

Majority-n from sorter networks


- ▶ Idee: Sort all input bits and pick the middle one from the sorted list
- ➤ Sorter networks consist only of comparators, which in the Boolean case can be implemented in terms of AND and OR:

Majority-n from sorter networks

- ▶ Idee: Sort all input bits and pick the middle one from the sorted list
- ➤ Sorter networks consist only of comparators, which in the Boolean case can be implemented in terms of AND and OR:

$$\begin{array}{ccc}
 x & \downarrow & x \land y = \langle x0y \rangle \\
 y & \downarrow & x \lor y = \langle x1y \rangle
 \end{array}$$

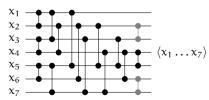Example: Sorter networks for 7 bits requires 16 comparisons (optimal), we can drop $2 \rightarrow 28$ majority gates




Majority-n from sorter networks

- ▶ Idee: Sort all input bits and pick the middle one from the sorted list
- ➤ Sorter networks consist only of comparators, which in the Boolean case can be implemented in terms of AND and OR:

$$\begin{array}{ccc}
 x & \downarrow & x \land y = \langle x0y \rangle \\
 y & \downarrow & x \lor y = \langle x1y \rangle
 \end{array}$$

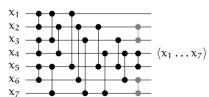Example: Sorter networks for 7 bits requires 16 comparisons (optimal), we can drop $2 \rightarrow 28$ majority gates



Complexity: $O(n \log n)$

Median selection: An algorithm that finds the median of given values $\{a_1, \ldots, a_n\}$ using O(n) comparisons (it does not sort *all* elements)

- Median selection: An algorithm that finds the median of given values $\{\alpha_1, \ldots, \alpha_n\}$ using O(n) comparisons (it does not sort *all* elements)
- $\langle x_1 \dots x_n \rangle = [\text{median of } \{x_1, \dots, x_n\}]$

- Median selection: An algorithm that finds the median of given values $\{a_1, \ldots, a_n\}$ using O(n) comparisons (it does not sort *all* elements)
- $\langle x_1 \dots x_n \rangle = [\text{median of } \{x_1, \dots, x_n\}]$
- ▶ Good asymptotic upper bound, but the construction is quite complex

- Median selection: An algorithm that finds the median of given values $\{a_1, \ldots, a_n\}$ using O(n) comparisons (it does not sort *all* elements)
- $\langle x_1 \dots x_n \rangle = [\text{median of } \{x_1, \dots, x_n\}]$
- ▶ Good asymptotic upper bound, but the construction is quite complex
- ▶ Majority-7 based on median selection construction has at least 42 majority gates

Shannon decomposition and majority decomposition

Shannon decomposition

For any Boolean function $f(x_1, ..., x_n)$ we have

$$f=x_{\mathfrak{i}} \ ? \ f_{x_{\mathfrak{i}}} : f_{\bar{x}_{\mathfrak{i}}}=x_{\mathfrak{i}}f_{x_{\mathfrak{i}}} \oplus \bar{x}_{\mathfrak{i}}f_{\bar{x}_{\mathfrak{i}}}$$

Shannon decomposition and majority decomposition

Shannon decomposition

For any Boolean function $f(x_1,...,x_n)$ we have


$$f=x_{\mathfrak{i}} \ ? \ f_{x_{\mathfrak{i}}} : f_{\bar{x}_{\mathfrak{i}}}=x_{\mathfrak{i}}f_{x_{\mathfrak{i}}} \oplus \bar{x}_{\mathfrak{i}}f_{\bar{x}_{\mathfrak{i}}}$$

Majority decomposition [S.B. Akers Jr., 1961]

For a monotone Boolean function $f(x_1, \ldots, x_n)$ we have


$$f = \langle x_{\mathfrak{i}} f_{x_{\mathfrak{i}}} f_{\bar{x}_{\mathfrak{i}}} \rangle = x_{\mathfrak{i}} f_{x_{\mathfrak{i}}} \oplus x_{\mathfrak{i}} f_{\bar{x}_{\mathfrak{i}}} \oplus f_{x_{\mathfrak{i}}} f_{\bar{x}_{\mathfrak{i}}}$$

From BDDs to majority graphs

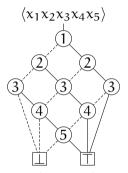


Binary decision diagram

From BDDs to majority graphs

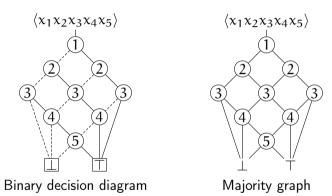


From BDDs to majority graphs

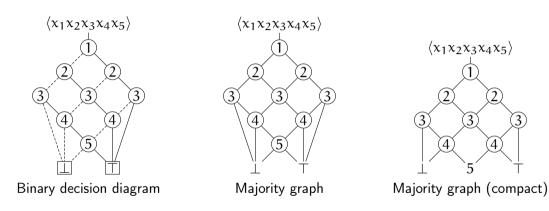

Upper bounds for majority-n decomposition


n	3	5	7	9	11	13	15	17
Optimum	1	4	7					
BDDs	3	8	15	24	35	48	63	80
Sorter networks	6	18	32	50	70	90	112	142
Median selection*	18	30	42	53	65	77	89	101

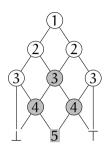^{*}optimistic: takes only into account number of comparators




Apply distributivity rule
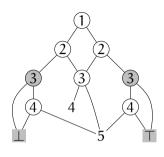
$$\langle\langle x_4x_50\rangle x_3\langle x_4x_51\rangle\rangle = \langle x_4x_5\langle 0x_31\rangle\rangle = \langle x_4x_3x_5\rangle$$



Apply relevance rule

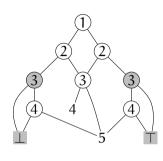
$$\langle xyz \rangle = \langle xyz_{x/\bar{y}} \rangle$$



Apply relevance rule

$$\langle xyz \rangle = \langle xyz_{x/\bar{y}} \rangle$$
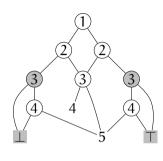
$$\langle 0x_3 \langle 0x_4x_5 \rangle \rangle = \langle 0x_3 \langle 0x_4x_5 \rangle_{0/\bar{x}_3} \rangle = \langle 0x_3 \langle \bar{x}_3x_4x_5 \rangle \rangle$$




Apply relevance rule

$$\langle xyz \rangle = \langle xyz_{x/\bar{y}} \rangle$$


$$\langle 0x_3 \langle 0x_4x_5 \rangle \rangle = \langle 0x_3 \langle 0x_4x_5 \rangle_{0/\bar{x}_3} \rangle = \langle 0x_3 \langle \bar{x}_3x_4x_5 \rangle \rangle$$
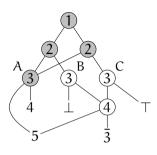
$$\langle 1x_3\langle 1x_4x_5\rangle\rangle = \langle 1x_3\langle 1x_4x_5\rangle_{1/\bar{x}_3}\rangle = \langle 1x_3\langle \bar{x}_3x_4x_5\rangle\rangle$$




Apply distributivity rule

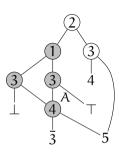
$$\langle \langle \mathbf{x}_2 \mathbf{A} \mathbf{B} \rangle \mathbf{x}_1 \langle \mathbf{x}_2 \mathbf{A} \mathbf{C} \rangle \rangle = \langle \mathbf{x}_2 \mathbf{A} \langle \mathbf{B} \mathbf{x}_1 \mathbf{C} \rangle \rangle$$



Apply distributivity rule

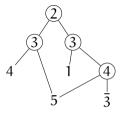
$$\langle\langle x_3 A 0 \rangle x_1 \langle x_3 A 1 \rangle\rangle = \langle x_3 A \langle 0 x_1 1 \rangle\rangle = \langle x_3 A x_1 \rangle$$



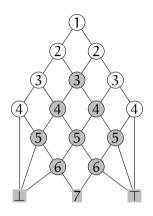


Identify majority-5

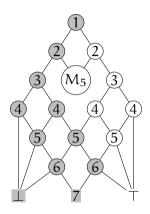
There are actually four majority-5 subnetworks in the graph



Consider left branch

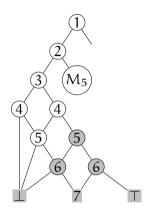


Identify majority-3

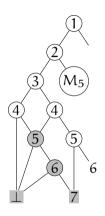


Relevance


Changes constants into primary inputs

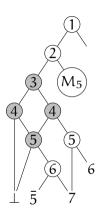


Distributivity

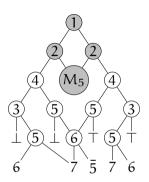

Distributivity

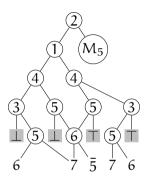

Remove \perp and \top

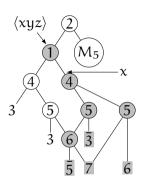


Replacement rule


We have

$$\langle xyz \rangle = \langle wyz \rangle$$

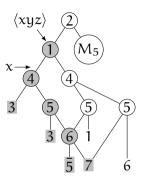
if and only if $(y \oplus z)(w \oplus x) = 0$.



Replacement rule

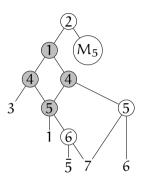

Distributivity $+ M_5$ optimum

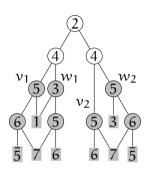


Swapping rule


Let v_1, v_2, w_1, w_2 not depend on x and y. We have

$$\langle \mathbf{x} \langle \mathbf{y} \mathbf{v}_1 \mathbf{w}_1 \rangle \langle \mathbf{y} \mathbf{v}_2 \mathbf{w}_2 \rangle \rangle = \langle \mathbf{x} \langle \mathbf{y} \mathbf{v}_2 \mathbf{w}_1 \rangle \langle \mathbf{y} \mathbf{v}_1 \mathbf{w}_2 \rangle \rangle,$$

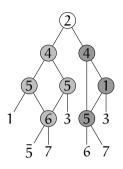if
$$(v_1 \oplus v_2)(w_1 \oplus w_2) = 0$$
.



Distributivity and relevance

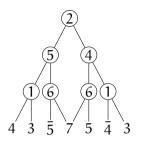

Optimum result

► Research question: How many majority-3 operations do we need to realize majority-n (precisely)?

- ► Research question: How many majority-3 operations do we need to realize majority-n (precisely)?
- ► Constructions that were used to show good asymptotic upper bounds are not helpful for small n

- ► Research question: How many majority-3 operations do we need to realize majority-n (precisely)?
- Constructions that were used to show good asymptotic upper bounds are not helpful for small n
- Proposed construction method based on BDDs by exploiting decomposition property for monotone functions

- ▶ Research question: How many majority-3 operations do we need to realize majority-n (precisely)?
- Constructions that were used to show good asymptotic upper bounds are not helpful for small n
- Proposed construction method based on BDDs by exploiting decomposition property for monotone functions
- ▶ Next: Majority-9 and more insight into analytical derivations

The fascinating properties of majority

Mathias Soeken

Integrated Systems Laboratory, EPFL, Switzerland

