

Progressive Decomposition: A Heuristic to Structure Arithmetic Circuits

Ajay K. Verma, Philip Brisk and Paolo Ienne



Processor Architecture Laboratory (LAP)
& Centre for Advanced Digital Systems (CSDA)



Ecole Polytechnique Fédérale de Lausanne (EPFL)

Logic Synthesis: Unable to Impose Hierarchy and Structure


- Logic synthesis tools
 - Local optimization via Boolean minimization
 - Lacking for arithmetic circuits

$$ab(a + b) + ca + \bar{c} \longrightarrow a + \bar{c}$$

- Architectural transformation
 - Not with logic synthesis

Our contribution

 Ripple-Carry Adder \longrightarrow Carry-Lookahead Adder




Leading Zero Detector (LZD)

- Finds the position of the most significant non-zero bit

$$x_i = \overline{a_{15}}\overline{a_{14}} \dots \overline{a_{15-(i-2)}}\overline{a_{15-(i-1)}}a_{15-i}$$

x_i is TRUE if $(i+1)^{\text{th}}$ most-significant bit is the leading non-zero bit


Large fan-in dependencies

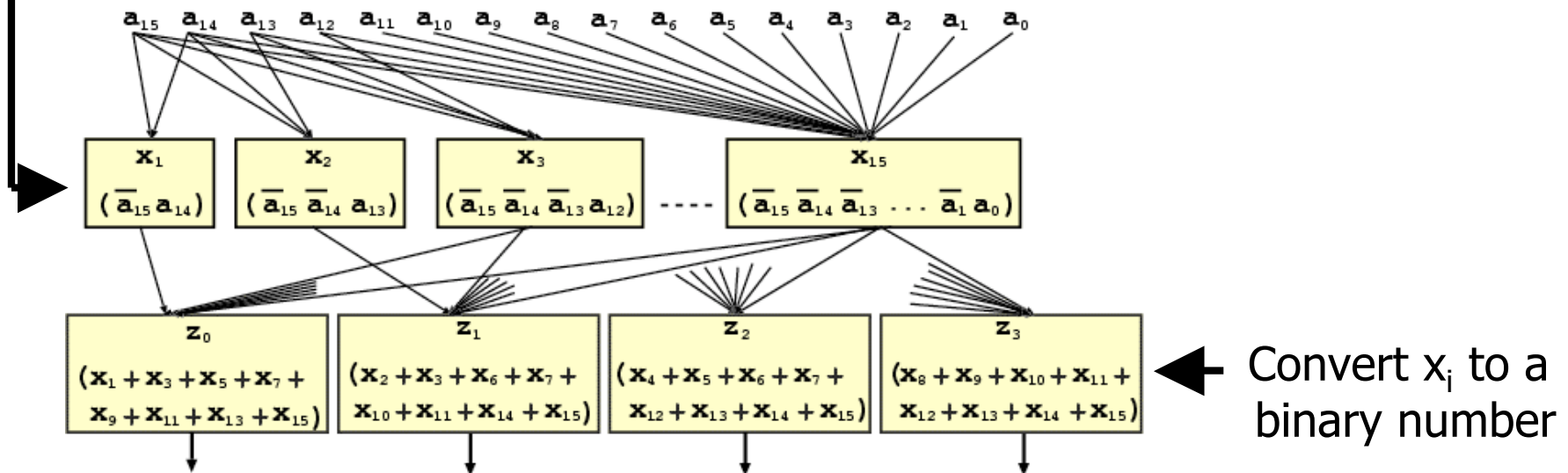

LZD: A Better Implementation [Oklobdzija94]


- Divide 16 bits into 4 blocks
 - For each block compute the following:
 - Position of the most significant non-zero bit
 - Control bit V_i is TRUE if at least one bit in this block is one

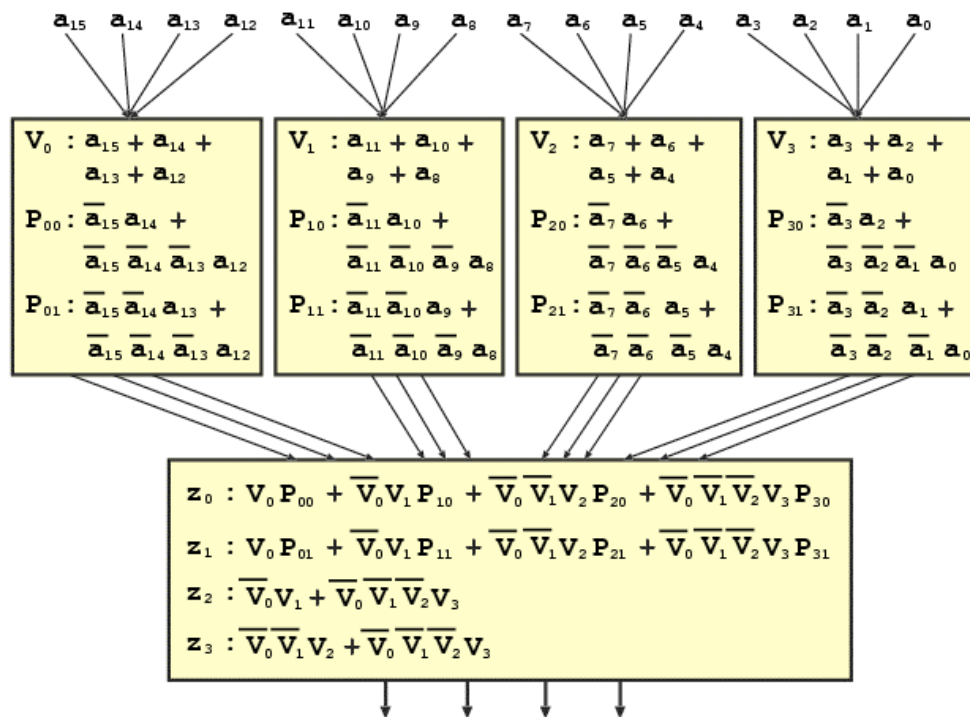- Similar in principle to carry-lookahead addition




Reduced fan-in dependencies

What is the Bottom Line?

 

0.36 ns
(426.8 μm^2)

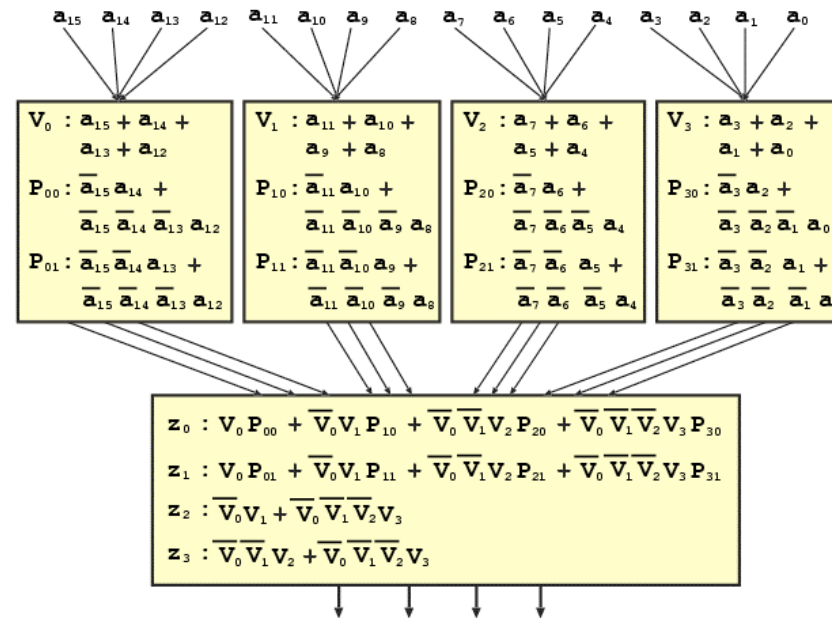

Outline

- Related Work
- Architectural optimization
 - How to impose hierarchy?
- Properties of Algebra
 - Ring structure of Boolean expressions
- Progressive Decomposition Algorithm
- Results
- Conclusions


Related Work

- Manual approaches for optimizing circuits of interest
 - The entire field of computer arithmetic
 - Great ideas by really smart people!
- Algorithmic approaches for a particular class of circuits
 - Variable group size CLA adder [Lee91]
 - Irregular partial product compressors [Stelling98]
- Heuristics to optimize general classes of circuits
 - Kernel and co-kernel extraction [Brayton82]
 - Architecture exploration via exhaustive search [Verma06]

Input Condensation


Leader expressions:

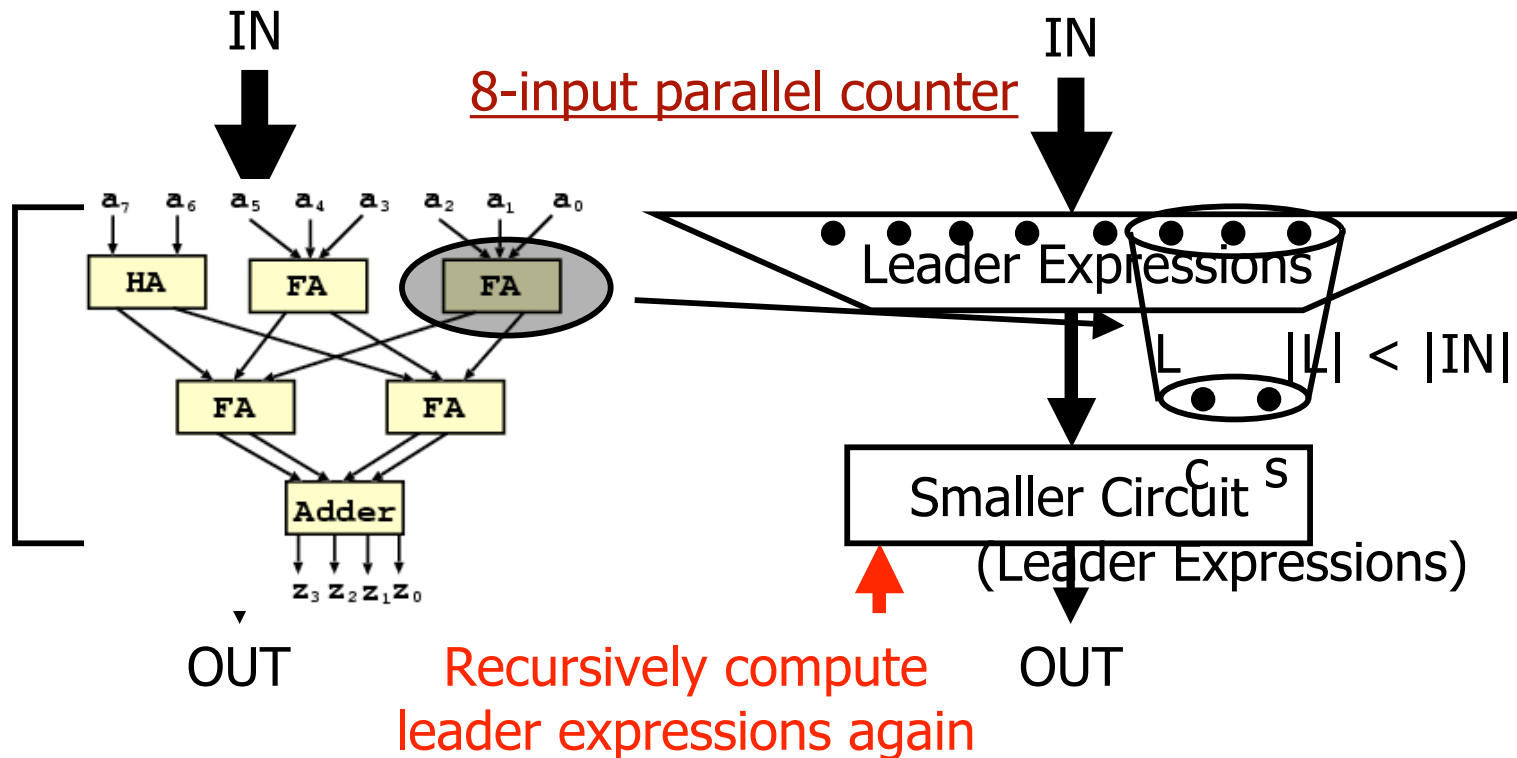- Sufficient to evaluate the whole of an expression
- Once you evaluate them, you can discard the input bits



Compute all leader expressions in parallel

Hierarchical Circuit Construction

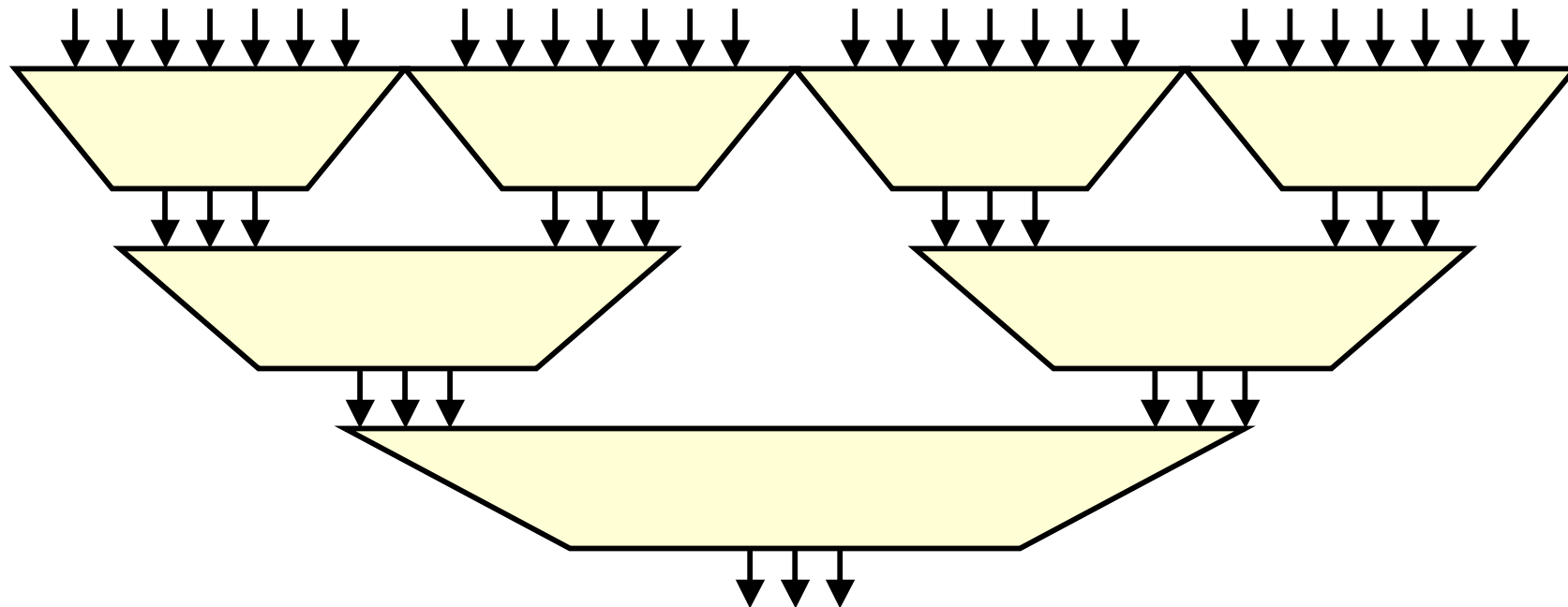

Theorem: This approach always generalizes to circuits that have an "effective compose hierarchy"

Reed-Muller Form

- XOR-of-Product Form
 - Better suits arithmetic circuits
 - Forms a ring under the operations XOR and AND
 - Boolean properties exploited by our algorithm
 - Identities
 - Null Spaces
 - Linear Dependence


- Before

$$X = [a_1b_1 + (a_1 + b_1)a_0b_0] \\ \oplus [(a_1 \oplus b_1 \oplus a_0b_0)c_1 + c_0(a_0 \oplus b_0)(c_1 + (a_1 \oplus b_1 \oplus a_0b_0))]$$

- After

$$X = a_1b_1 \oplus a_0a_1b_0 \oplus a_0b_0b_1 \oplus a_1c_1 \oplus b_1c_1 \oplus a_0b_0c_1 \oplus a_0c_0c_1 \oplus a_0a_1c_0 \\ \oplus a_0b_1c_0 \oplus a_0b_0c_0 \oplus b_0c_0c_1 \oplus a_1b_0c_0 \oplus b_0b_1c_0$$

 Progressive Decomposition: Algorithm Overview



- Find leader expressions
- Choose a subset of input bits
 - Optimize via Boolean ring properties
 - How many bits?
 - Find identities
- Rewrite circuit in terms of leader expressions
 - Many can be dependent expressions

Finding Leader Expressions

- Similar to kernel extraction in algebraic factorization

$$X = ad \oplus aef \oplus bcd \oplus abe \oplus ace \oplus bcef$$

$$X = (a \oplus bc)d \oplus (a \oplus bc)ef \oplus (ab \oplus ac)e$$

$$X = (a \oplus bc)(d \oplus ef) \oplus (ab \oplus ac)e$$

$$\{(a, d), (a, ef), (bc, d), (ab, e), (ac, e), (bc, ef)\}$$

$$\{(a \oplus bc, d), (a \oplus bc, ef), (ab \oplus ac, e)\}$$

$$\{(a \oplus bc, d \oplus ef), (ab \oplus ac, e)\}$$

$$L(X, \{a, b, c\}) = ?$$

Leader expression of X
using inputs {a, b, c}

$$\alpha\beta \oplus \beta\gamma \rightarrow (\alpha \oplus \beta)\gamma$$

Separate expression terms: $(\text{chosen}, \text{not chosen}) \rightarrow (\alpha \oplus \beta)$ input bits

Hierarchy and Circuit Structure


$$X = ad \oplus aef \oplus bcd \oplus abe \oplus ace \oplus bcef$$

$$L(X, \{a, b, c\}) = \{a \oplus bc, ab \oplus ac\}$$

$$s_1 = a \oplus bc$$

$$s_2 = ab \oplus ac$$

$$X = s_1(d \oplus ef) \oplus s_2e$$

 

Example: Ternary Adder (3rd Output)


$$X = [a_1 b_1 + (a_1 + b_1) a_0 b_0] \oplus [(a_1 \oplus b_1 \oplus a_0 b_0) c_1 + c_0 (a_0 \oplus b_0) (c_1 + (a_1 \oplus b_1 \oplus a_0 b_0))]$$

$$L(X, \{a_1, b_1, c_1\}) = \{ \underbrace{a_1 \oplus b_1 \oplus c_1}_{\text{sum}}, \quad \underbrace{a_1 b_1 \oplus b_1 c_1 \oplus a_1 c_1}_{\text{carry}} \}$$

sum

carry

Carry-save adder

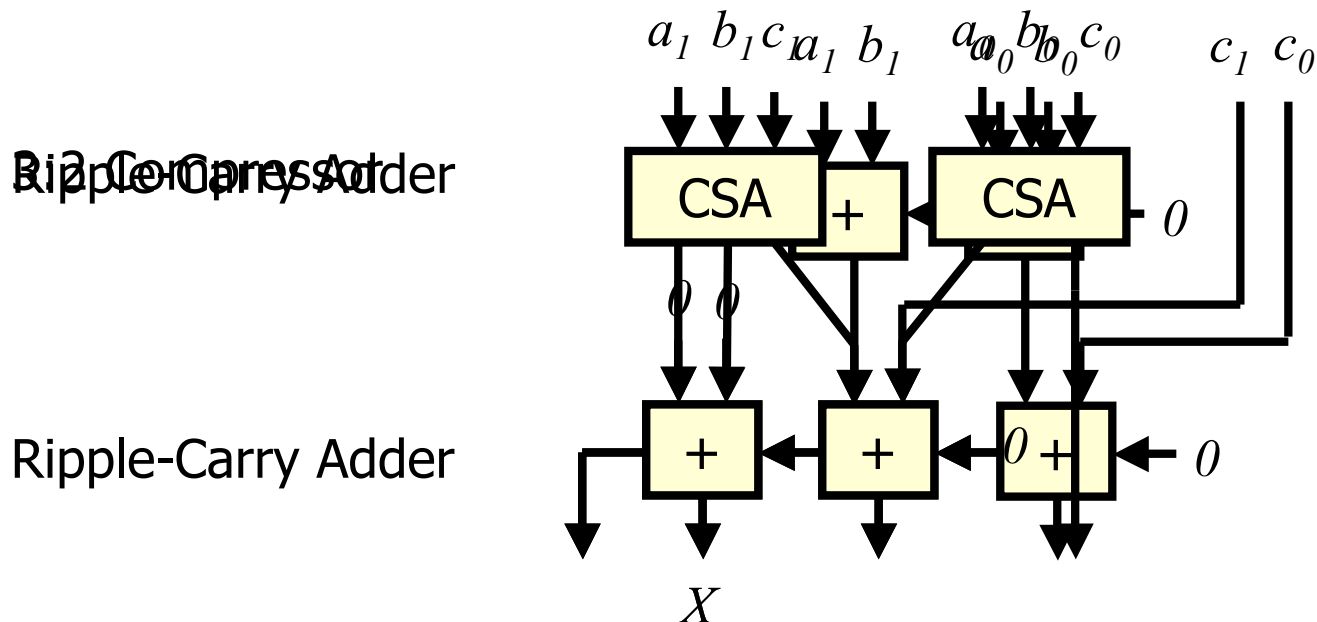

Exploiting the Null Space

- Null space of P, N(P):
 - All expressions that satisfy $PX = 0$

$$X = s_1(c \oplus d) \oplus s_2(a \oplus b) \oplus e \oplus de \oplus de$$

$$L(X, \{s_1, s_2\}) = \{s_1(c \oplus d) \oplus s_2(a \oplus b) \oplus e\}$$

$$X = (c \oplus d)(s_1 \oplus s_2) \oplus a s_2 \oplus b s_2 \oplus e s_1 \oplus b$$

$$L(X, \{s_2, t_2\}) = \{c d, s_1 \oplus d\}$$

$$L(X, \{s_2, t_2\}) = ? \quad t_1 = cd \quad t_2 = c \oplus d$$

$$\longrightarrow s_1 \in N(s_2)$$

$$\longrightarrow t_1 \in N(t_2)$$

$$\{(s_2, t_1 \oplus e), (t_2, s_1 \oplus e)\}$$

$$\{(s_2, s_1 \oplus t_1 \oplus e), (t_2, s_1 \oplus t_1 \oplus e)\}$$



$$\{(s_2 \oplus t_2, s_1 \oplus t_1 \oplus e)\}$$

Combine expressions: $\{(\alpha, \gamma), (\beta, \gamma)\} \rightarrow \{(\alpha \oplus \beta, \gamma)\}$

Linear Independence

- Linear dependence
 - Between leader expressions
 - Or between their corresponding coefficients
 - Rewrite some elements in terms of others

$$\{a \oplus b, b \oplus c, \cancel{c \oplus a}\} \longrightarrow \{a \oplus b, b \oplus c\}$$
$$c \oplus a = (a \oplus b) \oplus (b \oplus c)$$

- LZD
 - Initial basis: $\{V_0, P_{00}, P_{01}, V_0 \oplus P_{00}, V_0 \oplus P_{01}\}$
 - Reduces to: $\{V_0, P_{00}, P_{01}\}$

7-bit Majority Function

- Returns 1 if at least 4 bits are 1; 0 otherwise


$$L(X, \{a_1, a_2, a_3, a_4\}) = \{s_1, s_2, s_3, s_4\}$$

$$s_1 = a_1 \oplus a_2 \oplus a_3 \oplus a_4$$

$$s_2 = a_1a_2 \oplus a_1a_3 \oplus a_1a_4 \oplus a_2a_3 \oplus a_2a_4 \oplus a_3a_4$$

$$s_3 = a_1a_2a_3 \oplus a_1a_2a_4 \oplus a_1a_3a_4 \oplus a_2a_3a_4$$
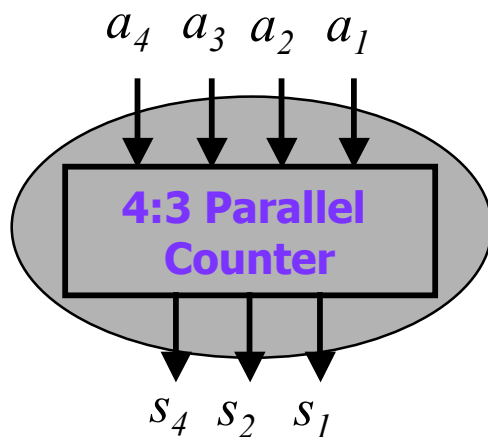
$$s_4 = a_1a_2a_3a_4 \quad s_4 \in N(s_1) \quad s_4 \in N(s_2)$$




$$s_3 = s_1s_2$$

$a_4a_3a_2a_1$	s_4	s_3	s_2	s_1
0000	0	0	0	0
0001	0	0	0	1
0010	0	0	1	0
0011	0	0	1	1
0100	0	0	0	1
0101	0	0	1	0
0110	0	0	1	0
0111	0	1	1	1
1000	0	0	0	1
1001	0	0	1	0
1010	0	0	1	0
1011	0	1	1	1
1100	0	0	1	0
1101	0	1	1	1
1110	0	1	1	1
1111	1	0	0	0

Propagation of Null Space Information

$$X = ap \oplus bp \oplus cp \oplus ax \oplus ay \oplus by \oplus bz \oplus cx \oplus cz \quad \{az = 0, bx = 0, cy = 0\}$$

$$L(X, \{a, b, c\}) = ?$$

 


$$X = (a \oplus b \oplus c)(p \oplus x \oplus y \oplus z)$$


$$L(X, \{a, b, c\}) = \{a \oplus b \oplus c\}$$

Combine expressions: $\{(\alpha, \gamma), (\beta, \gamma)\} \rightarrow \{(\alpha \oplus \beta, \gamma)\}$

Experimental Setup

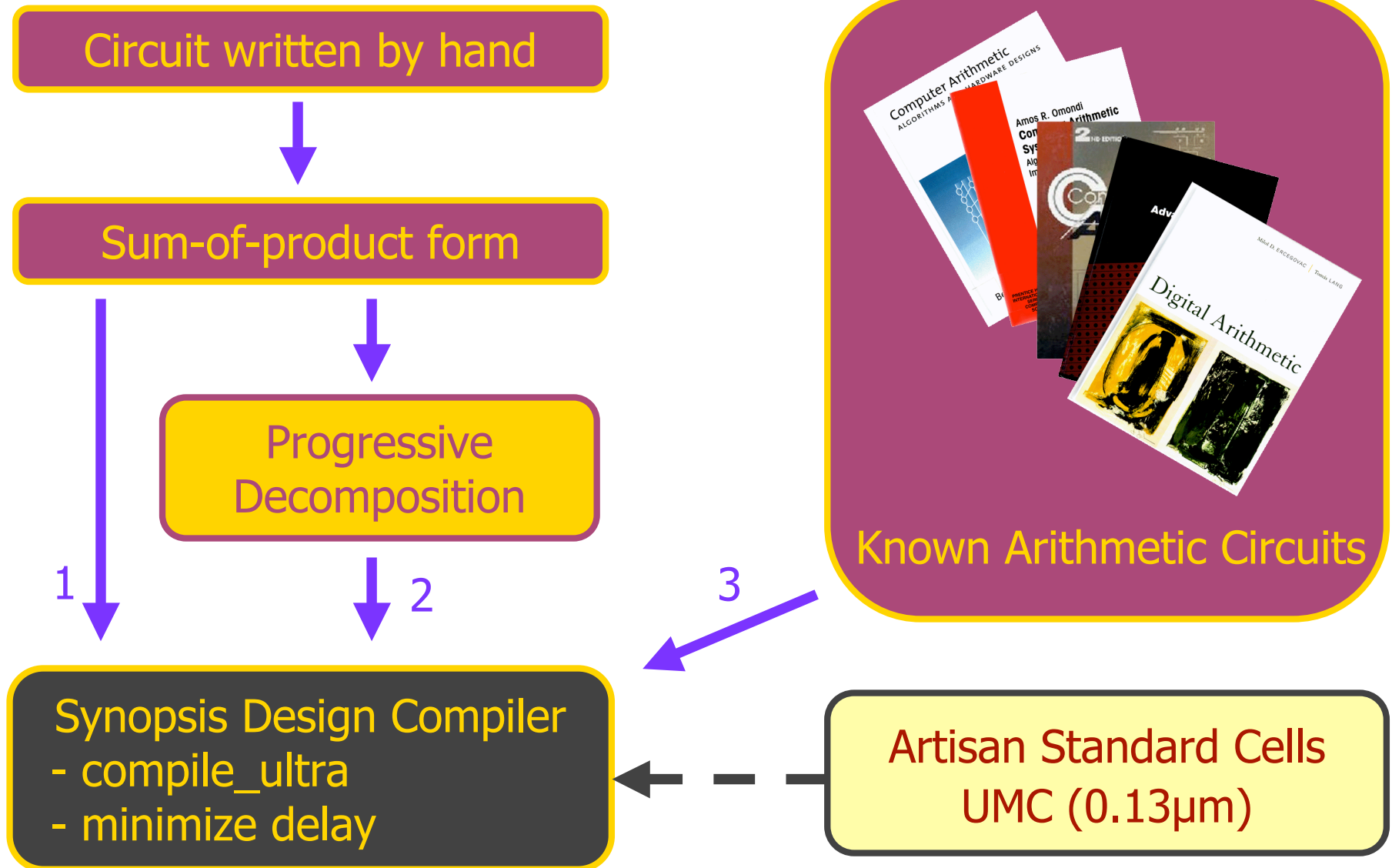

Results

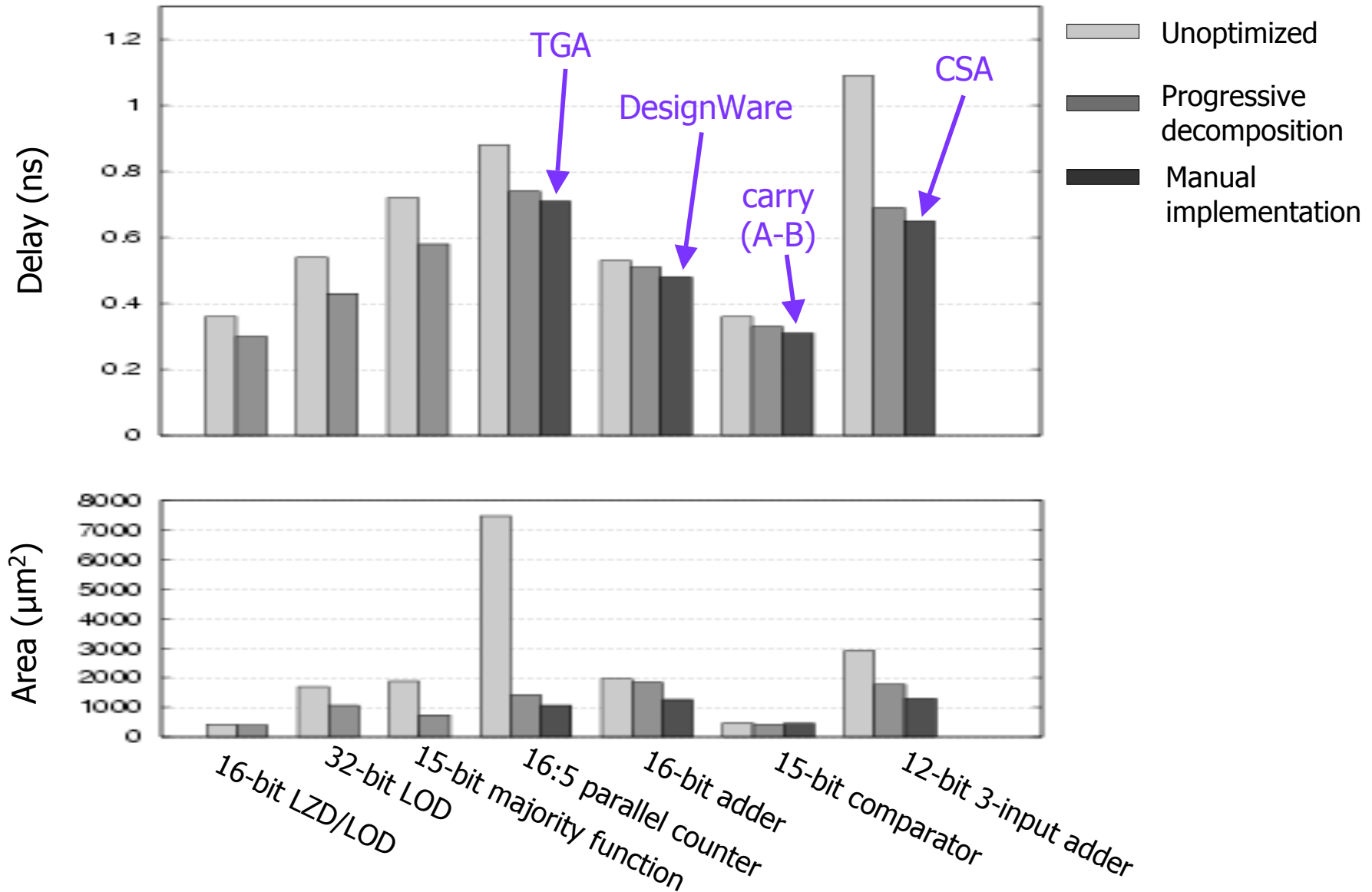

Conclusion

- Progressive Decomposition Algorithm
 - Arithmetic circuits
 - Previously, hard to optimize
 - Expert ideas can be generalized and automated
 - Automatically infers successful circuit designs from the literature
 - Carry-lookahead adder
 - Structured LZD circuit
 - Carry-save addition
 - Parallel counters
- Long-term goal
 - Replace manual circuit design with automated tools